

Electric Charge and electric Current

i = current

q = charge

A = Ampere

$$i = 1A$$


$$1A = \frac{1C}{S}$$

Coulomb
Second


$$i(t) = \frac{dq(t)}{dt} = \frac{\text{Charged Particles}}{\text{unit of time}}$$

$$q(t) = \int_{-\infty}^t i(x) dx$$

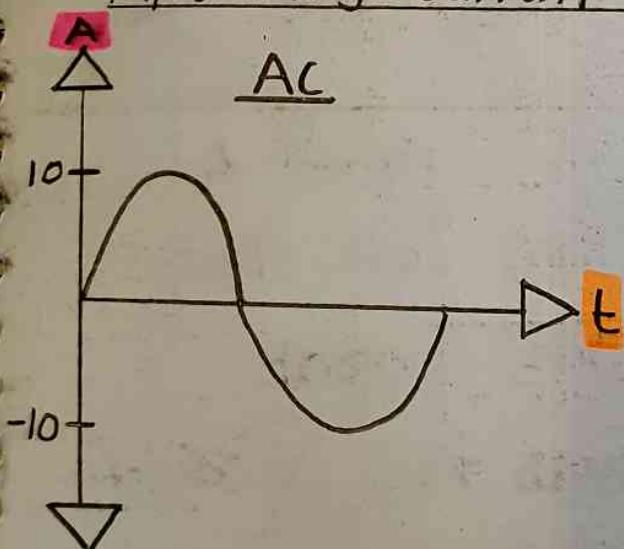Alternating Current (AC) vs. Direct Current (DC)



$$i_{ac} = 10 \sin(t) A$$

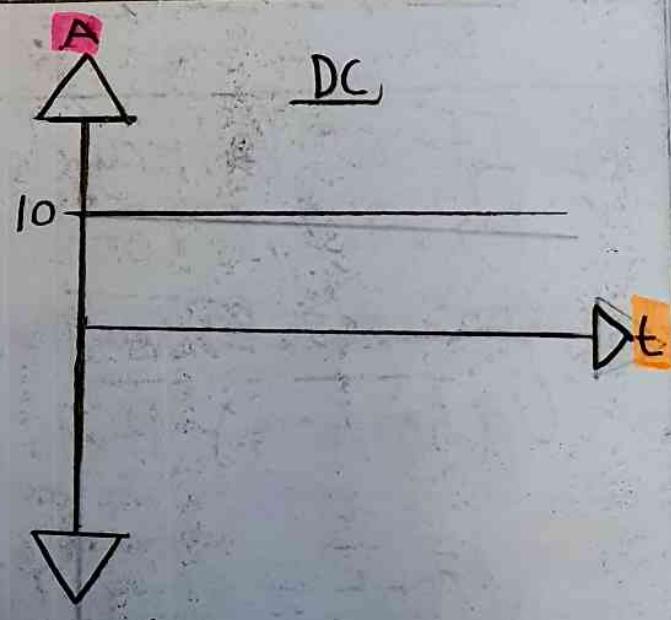


$$i_{dc} = 10A$$

A = Amps

t = time

Definition of Voltage

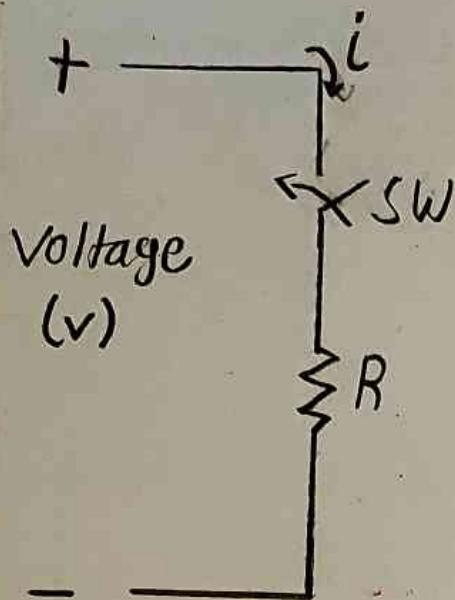

Coulomb = unit of charge

J = Joule

W = Watt

Current = watts / volts





$$1V = 1J/C$$

$$1W = \frac{1J}{S} = 1V(1A)$$






Q1. If a battery with a voltage equal to 100 volts is connected to a light bulb that consumes 60 watts, what is the current (in Amperes) that flow through the circuit?

$$\begin{aligned}\text{Current} &= 60W / 100V \\ &= 0.6 \text{ Amps}\end{aligned}$$


Independant Sources

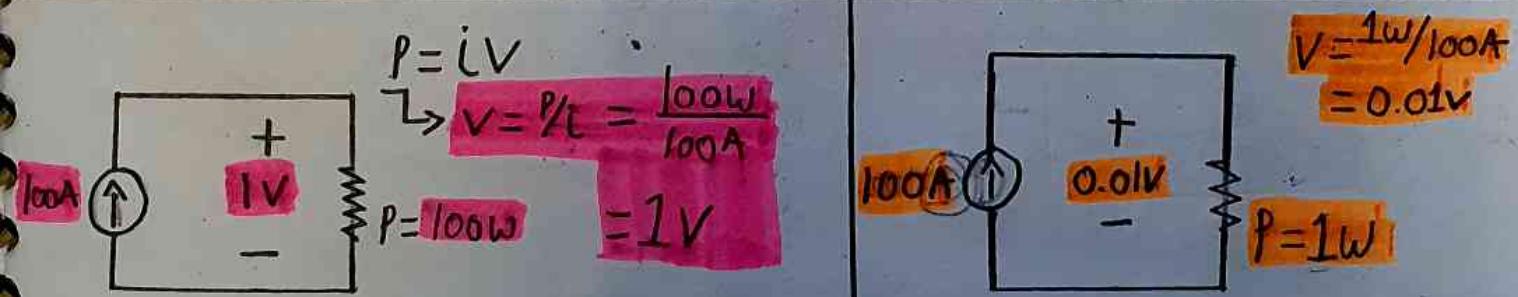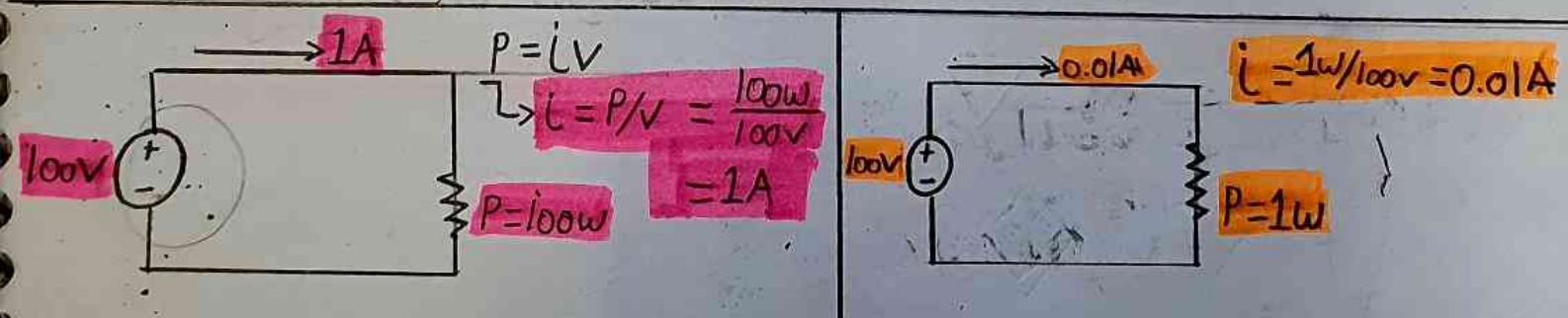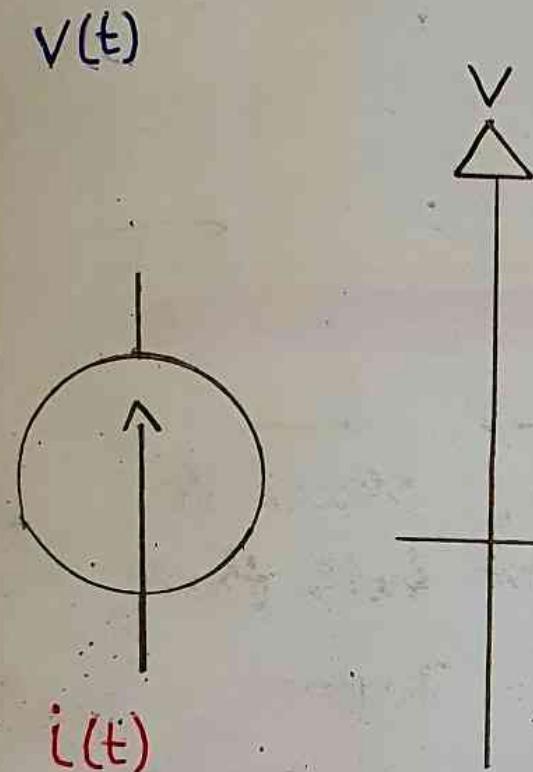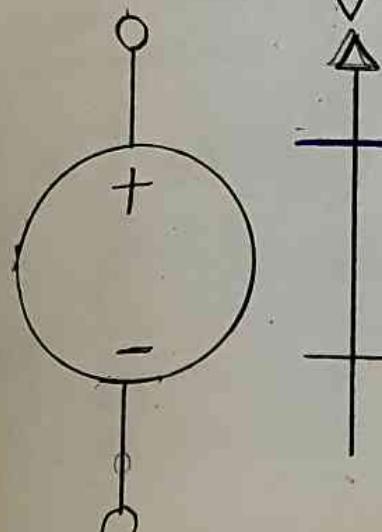

Dependant Sources

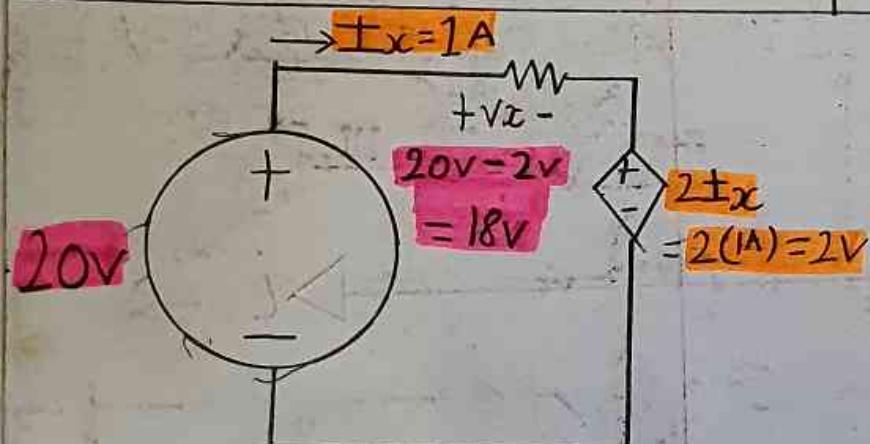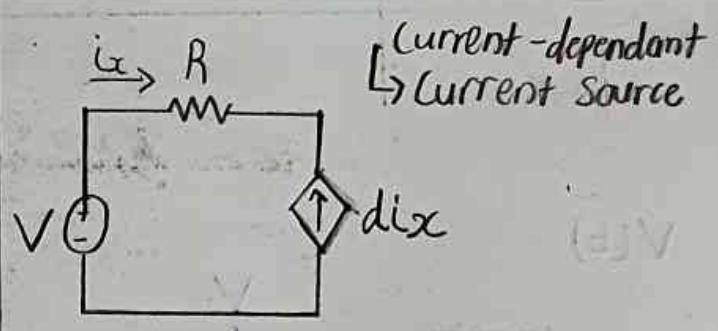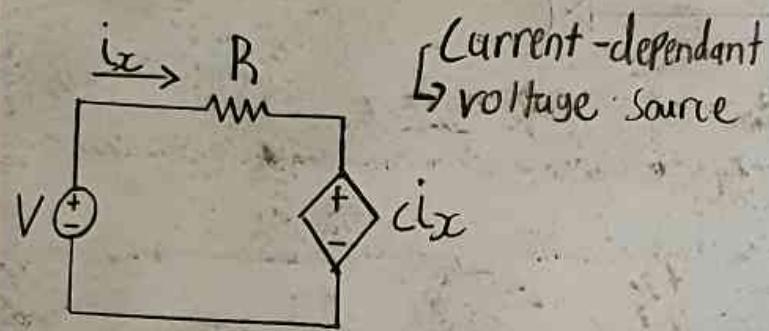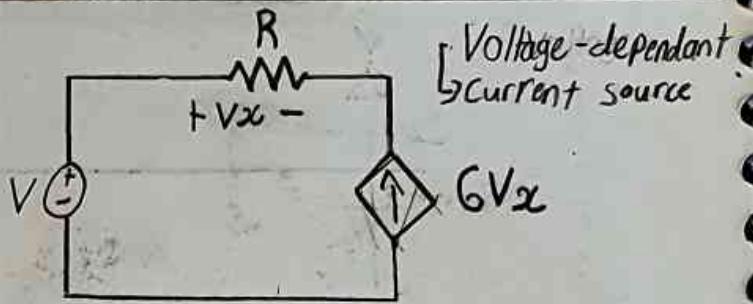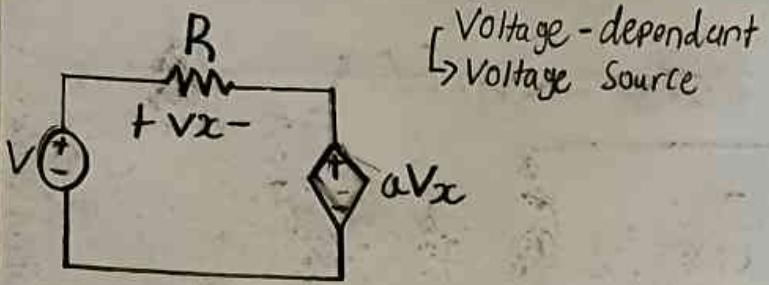


$$P = iV = 1A(18V) = 18W$$

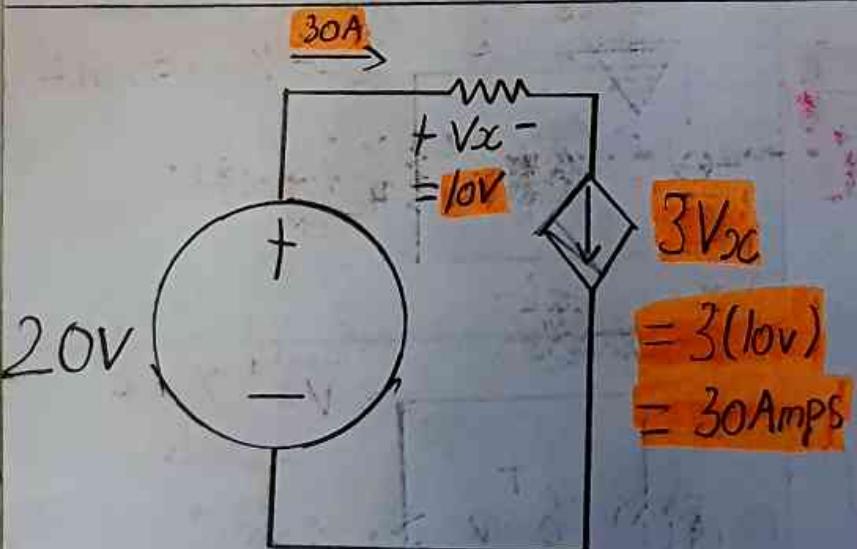

$$P = 30A(10V) = 300W$$

Ohm's Law

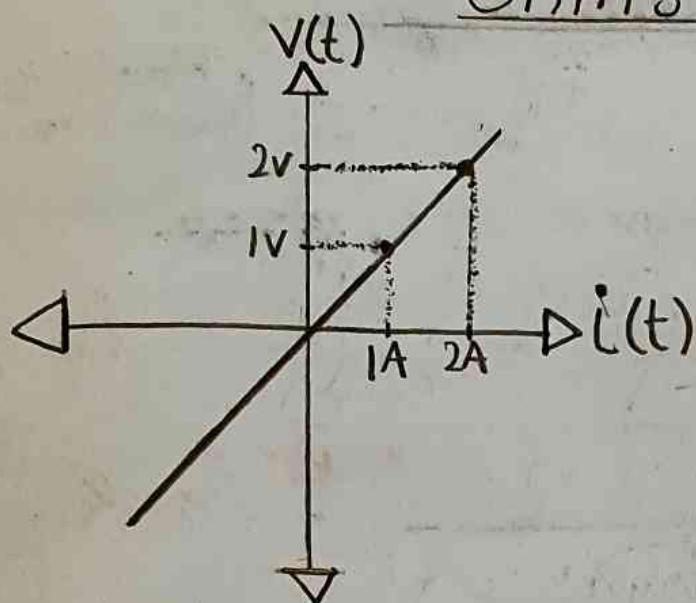


$$P = iV \rightarrow P = i(Ri) = i^2 R$$

$$P = \frac{V}{R} (V) \rightarrow P = \frac{V^2}{R}$$

$$R = \frac{V}{i} \rightarrow 1\Omega = \frac{1V}{1A}$$

$$V(t) = Ri(t)$$

$$G = 1/R \rightarrow 1/\Omega = 15$$

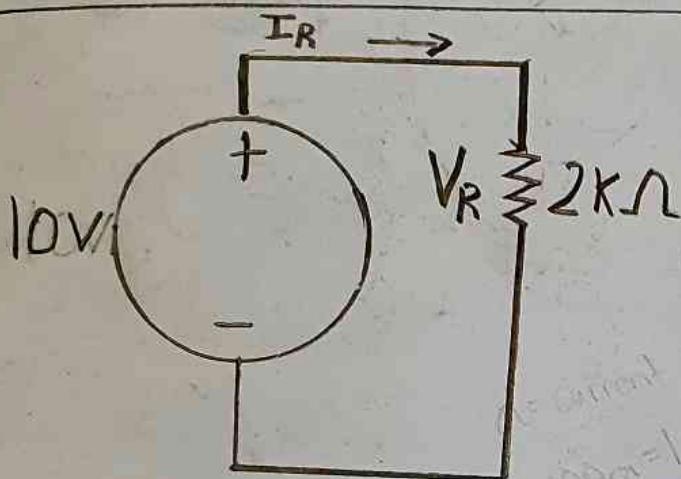


$$V = iR \rightarrow i = V_R = 10V / 2k\Omega = 5mA$$

$$P = \frac{V^2}{R} = \frac{10V^2}{2k\Omega} = 0.05W$$

$$P = i^2(R) = (5 \times 10^{-3})^2 (2k\Omega) = 0.05W$$
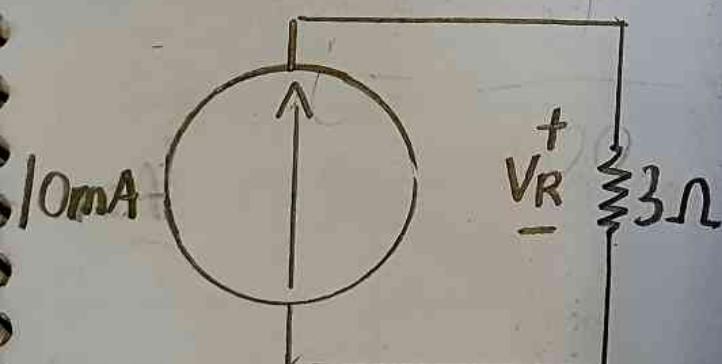
$$P = iV = (5 \times 10^{-3})(10V) = 0.05W$$



$$V = iR = (10 \times 10^{-3}) \times 3\Omega = 0.03V$$

$$P = \frac{V^2}{R} = \frac{0.03}{3} = 0.3mW$$


$$P = i^2R = (10 \times 10^{-3})^2 \times (3\Omega) = 0.3mW$$

$$P = iV = (10 \times 10^{-3}) \times 0.03V = 0.3mW$$

$$10mA = 10 \times 10^{-3} = 0.01A$$


Circuit terminology

- Nodes
- Loops
- Branch

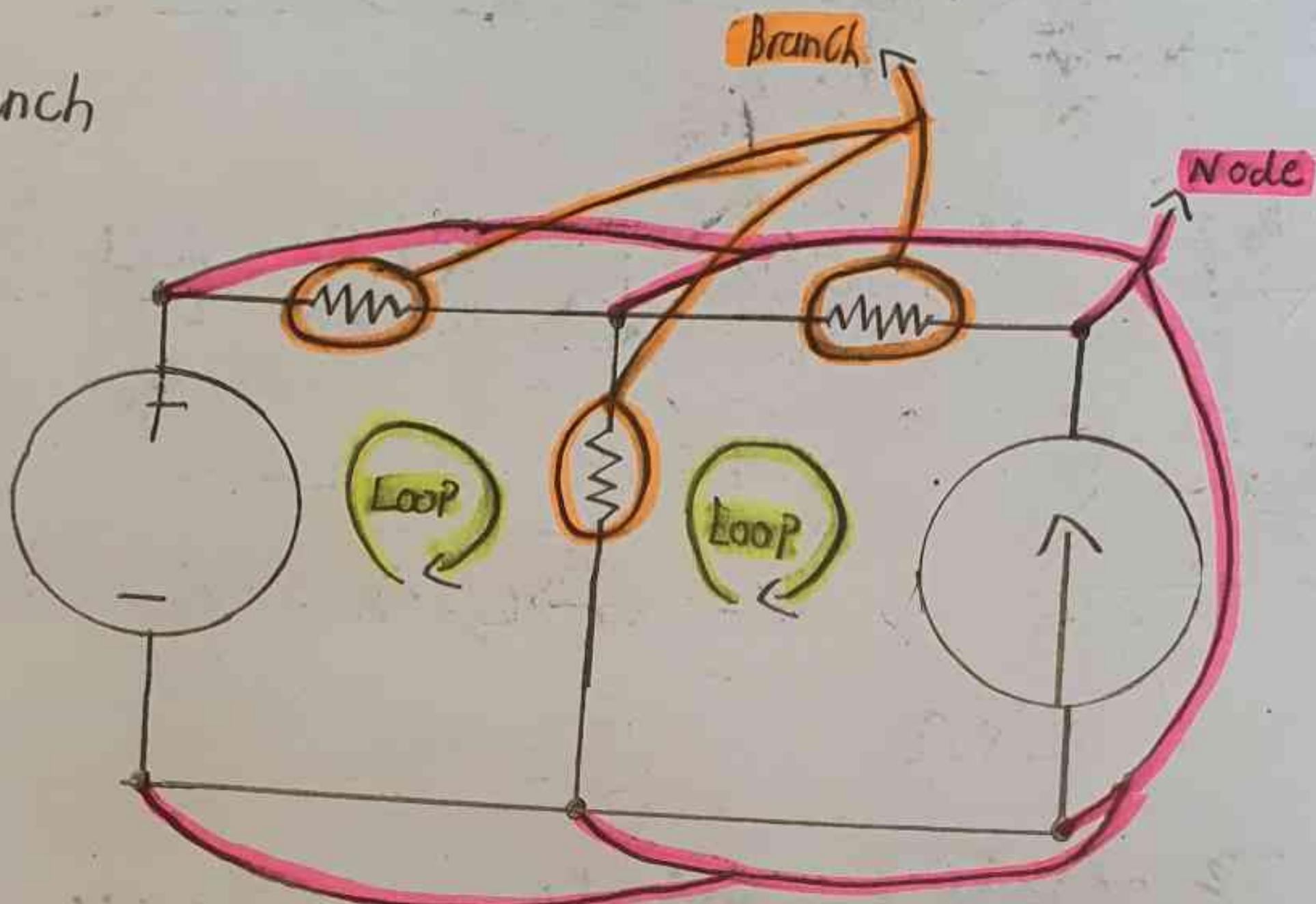


Kirchhoff's Current Law

Equation: $\sum_{j=1}^n i_j(t) = 0$

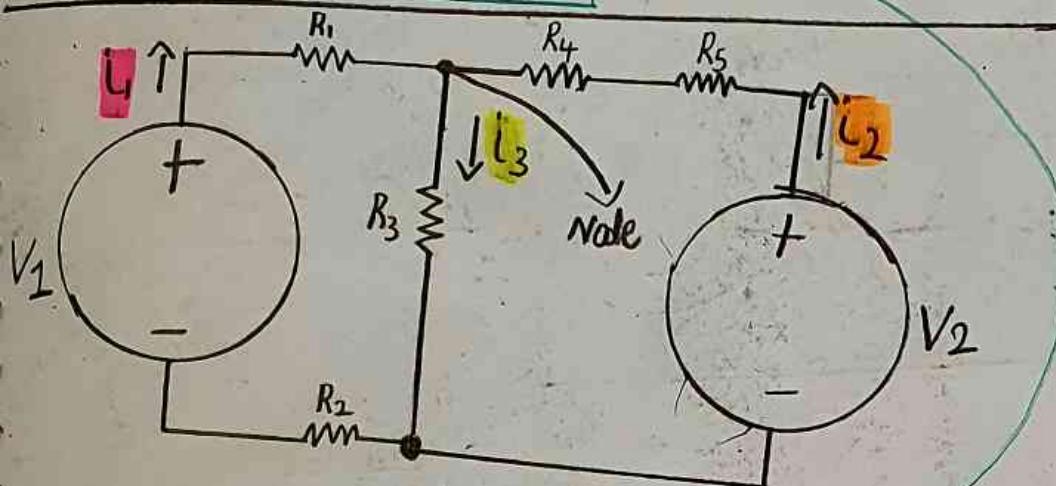

$$i_1 + i_2 - i_3 = 0$$

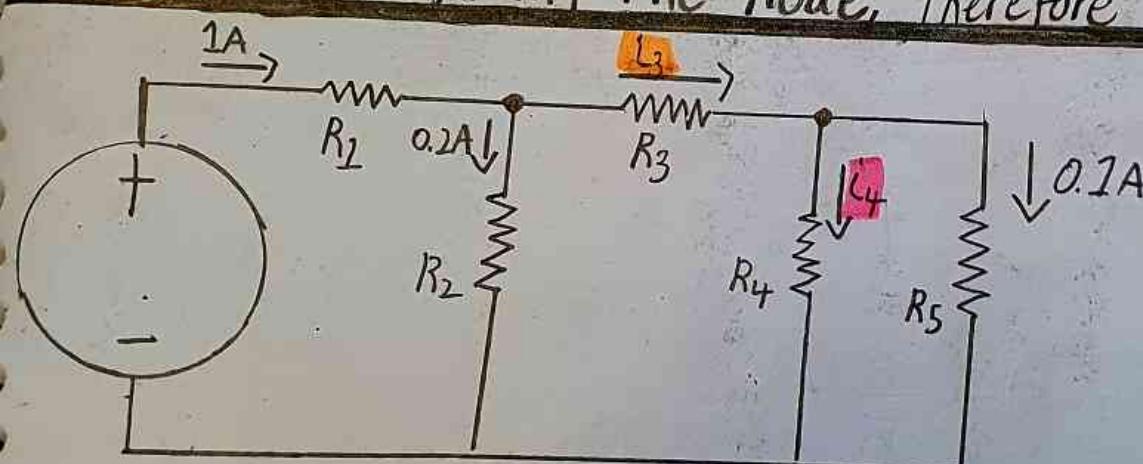i_1 and i_2 are entering the node so it's Positive
while i_3 is exiting the node, therefore it's negative.




$$1A - 0.2A - i_3 = 0 \rightarrow i_3 = 1A - 0.2A = 0.8A$$


$$0.8A - i_4 - 0.1A = 0 \rightarrow i_4 = 0.8A - 0.1A = 0.7A$$

Kirchhoff's Voltage Law

Equation: $\sum_{j=1}^n V_j(t) = 0$

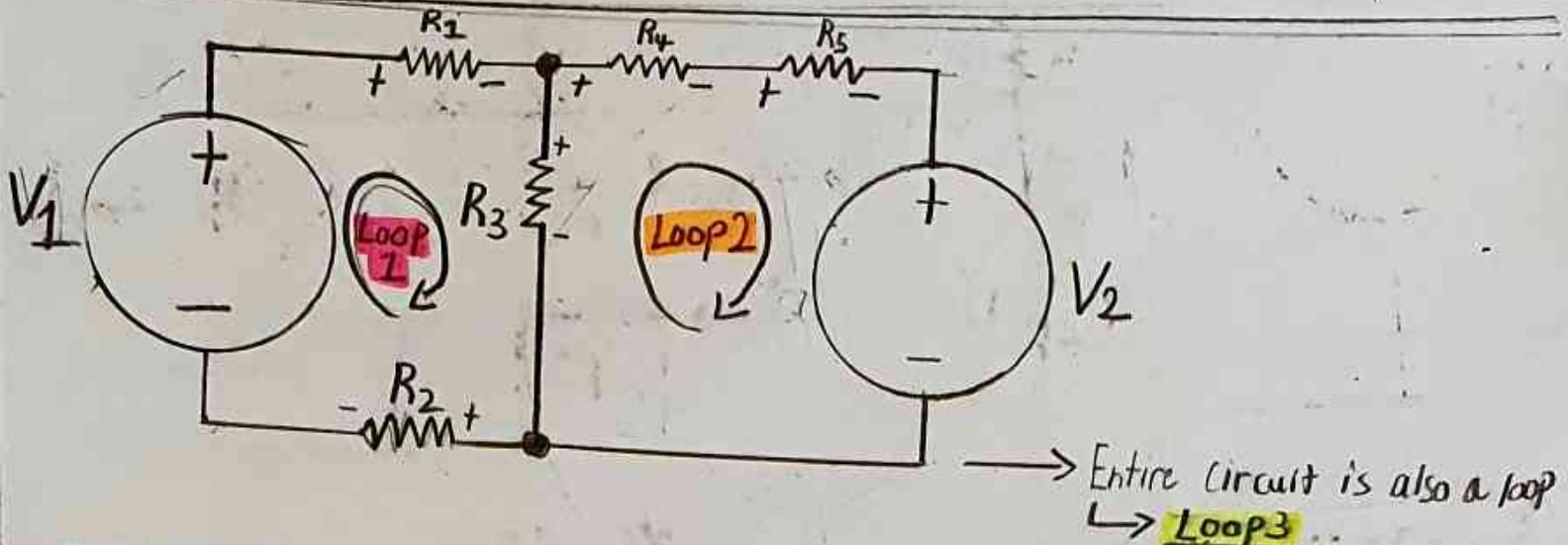


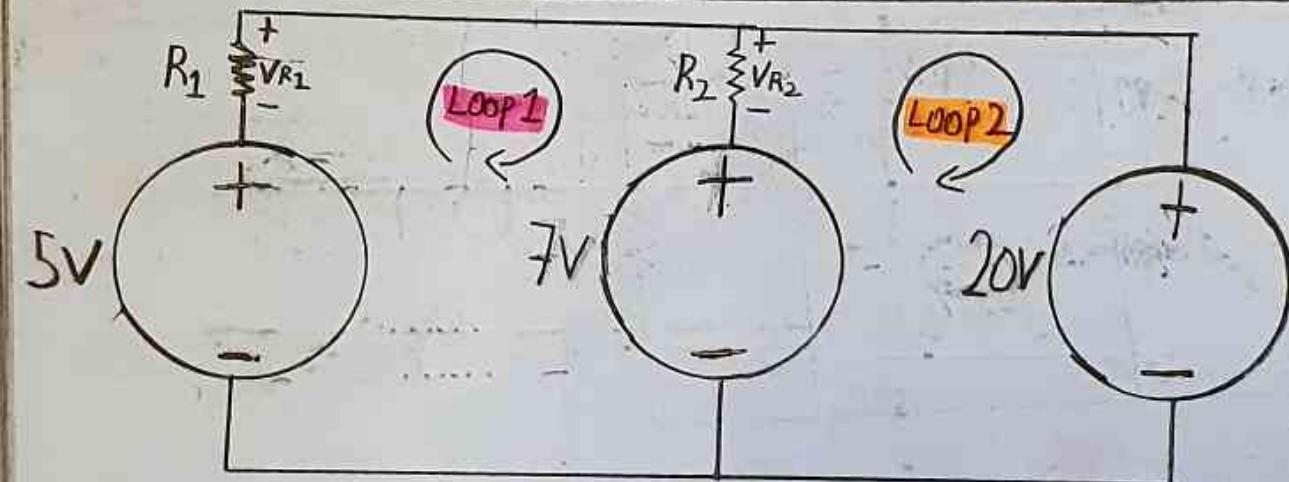- Loop 1: $-V_1 + V_{R1} + V_{R3} + V_{R2} = 0$
- Loop 2: $V_2 - V_{R3} + V_{R4} + V_{R5} = 0$
- Loop 3: $-V_1 + V_{R1} + V_{R4} + V_{R5} + V + V_{R2} = 0$



- Loop 1: $-5V - V_{R1} + V_{R2} + 7V = 0 \rightarrow V_{R1} = 15V$
- Loop 2: $-7V - V_{R2} + 20V = 0 \rightarrow V_{R2} = 13V$

Voltage Division

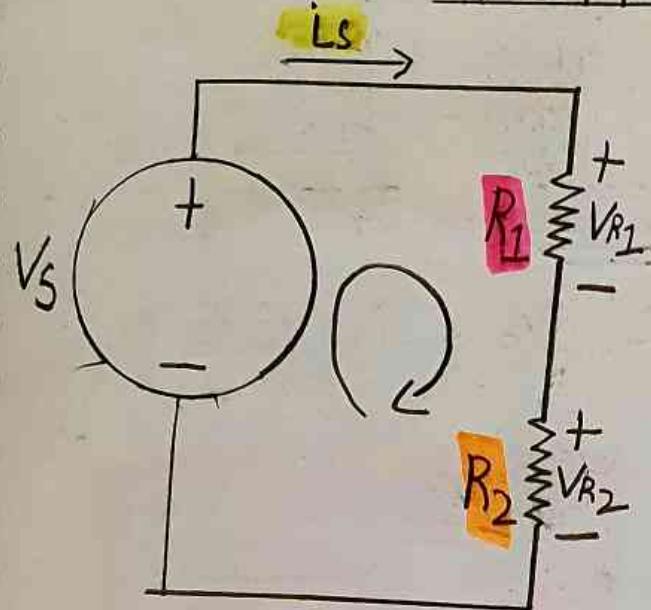

$$-V_s + V_{R1} + V_{R2} = 0 \rightarrow V_s = V_{R1} + V_{R2}$$

$$V = iR$$


$$V_s = i_s R_1 + i_s R_2 = i_s (R_1 + R_2)$$

$$\therefore i_s = \frac{V_s}{R_1 + R_2}$$

$$V_R = \frac{V_s R}{R_{\text{total}}}$$

$$V_{R1} = \frac{V_s}{R_1 + R_2} (R_1)$$

$$V_{R2} = \frac{V_s}{R_1 + R_2} (R_2)$$

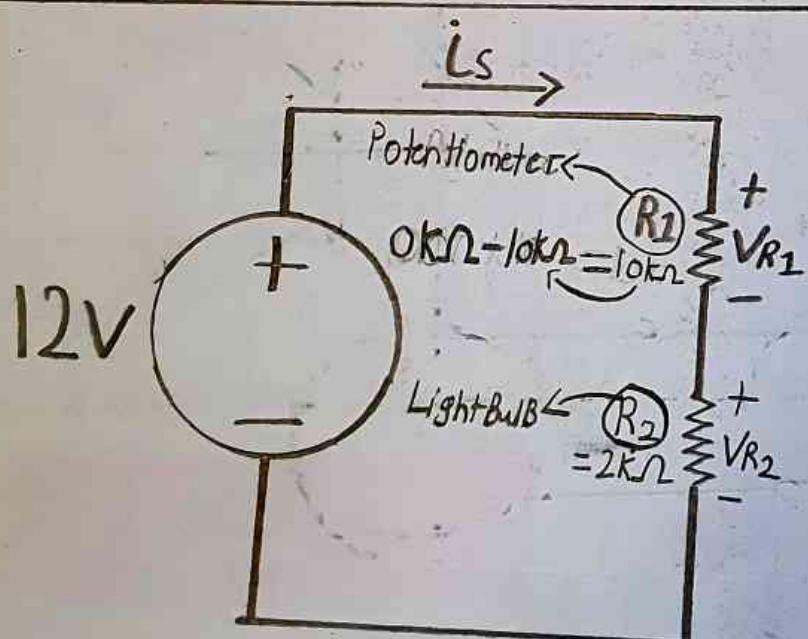

$$R_1 = 1k\Omega$$

$$V_{R2} = \frac{12V(2k\Omega)}{1k\Omega + 2k\Omega} = 8V$$


$$P = \frac{V^2}{R} = \frac{(8V)^2}{2k\Omega} = 32mW$$

$$R_1 = 10k\Omega$$

$$V_{R2} = \frac{12V(2k\Omega)}{10k\Omega + 2k\Omega} = 2V$$

$$P = \frac{V^2}{R} = \frac{(2V)^2}{2k\Omega} = 2mW$$

Current Division

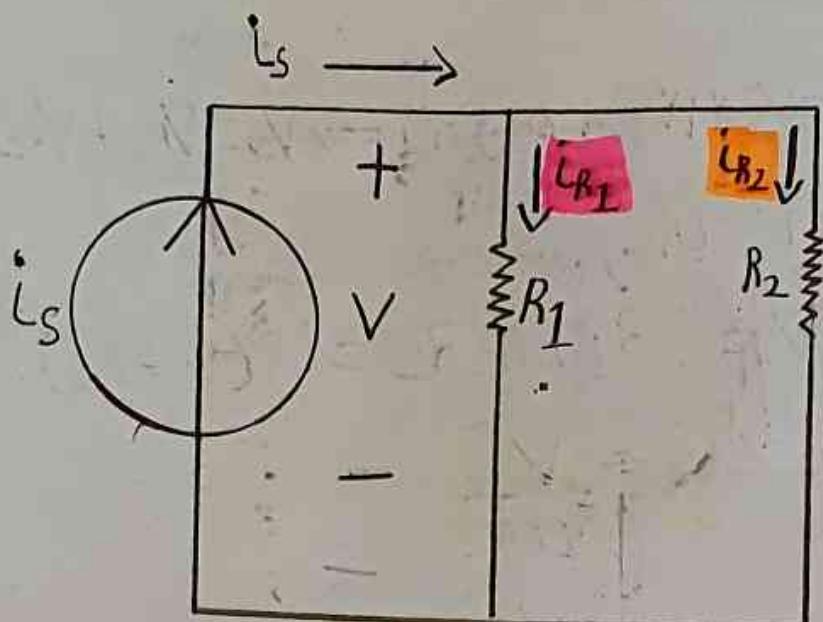



$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

Resistor Parallel

$$V = iR = i_s \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\begin{aligned} i_{R1} &= V/R_1 = i_s \left(\frac{R_1 R_2}{R_1 + R_2} \right) / R_1 \\ &= \frac{i_s R_2}{R_1 + R_2} \end{aligned}$$
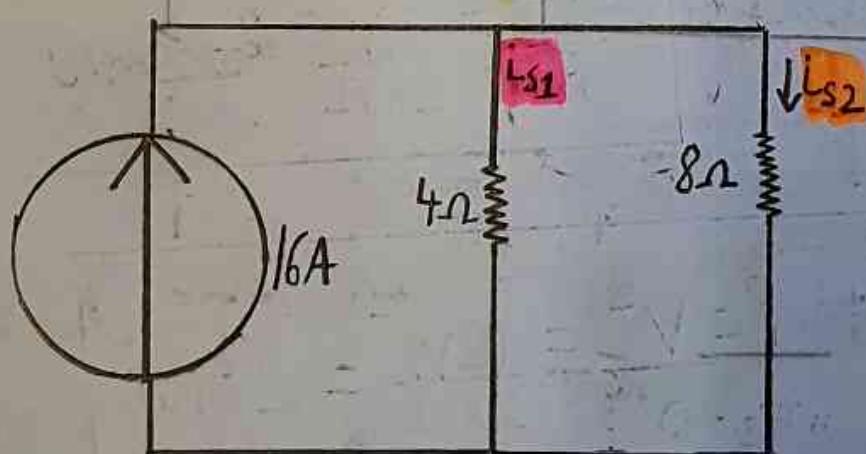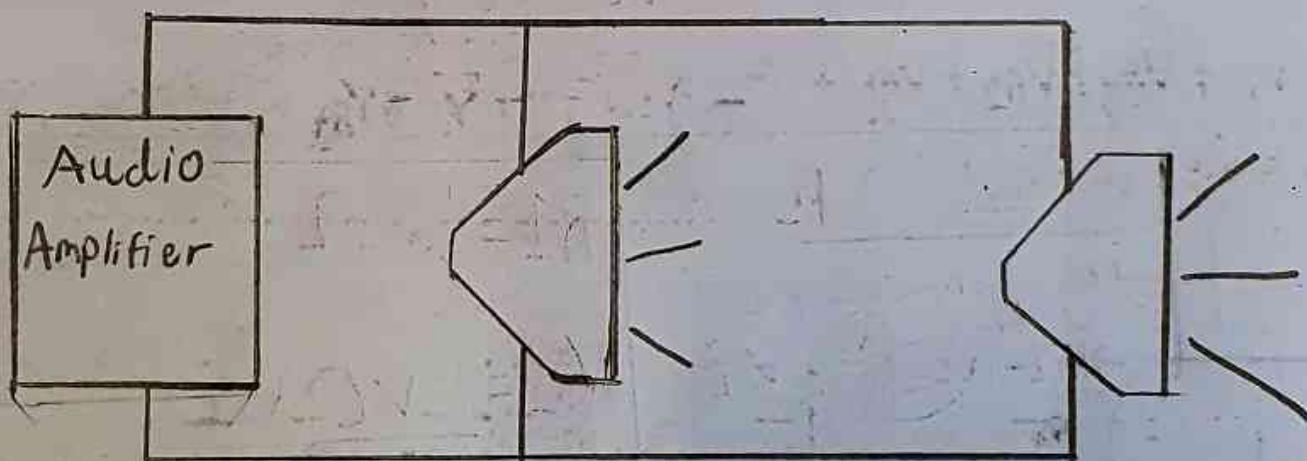
$$i_{R2} = i_s \left(\frac{R_1 R_2}{R_1 + R_2} \right) = \frac{i_s R_1}{R_1 + R_2}$$



$$i_{S1} = \frac{16A(8\Omega)}{4\Omega + 8\Omega} = 10.67A$$

$$i_{S2} = \frac{16A(4\Omega)}{4\Omega + 8\Omega} = 5.33A$$


$$\begin{aligned} P &= i^2 R = (10.67A)^2 (4\Omega) \\ &= 455.40W \end{aligned}$$

$$R_p = \frac{R_1 R_2}{R_1 + R_2} = \frac{4\Omega (8\Omega)}{4\Omega + 8\Omega} = 2.67\Omega$$

$$\begin{aligned} P_{total} &= 16^2 (2.67) \\ &\equiv 683.52W \end{aligned}$$

$$P = i^2 R = (5.33A)^2 (8\Omega) = 227.17W$$

Series Resistors

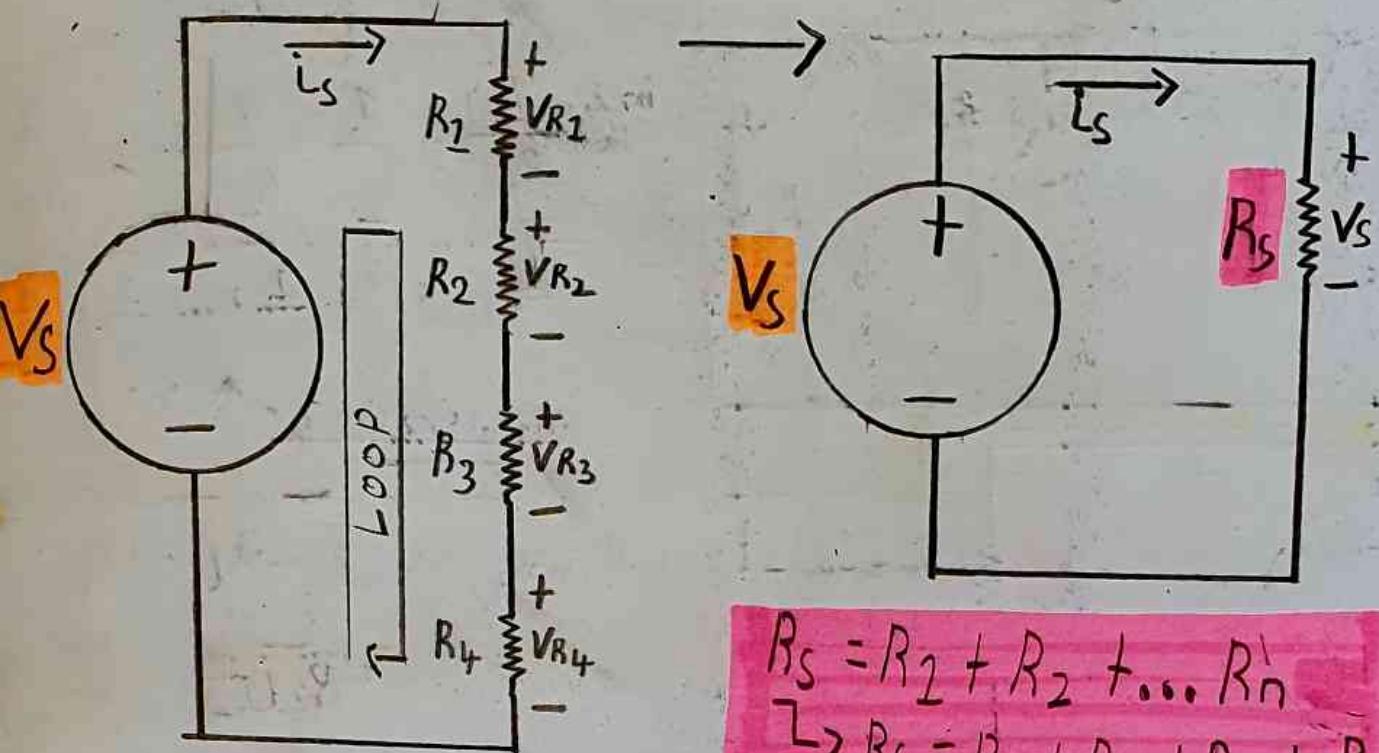

$$R_s = R_1 + R_2 + \dots + R_n$$


$$\Rightarrow R_s = R_1 + R_2 + R_3 + R_4$$

$$V = i_s R_1 + i_s R_2 + i_s R_3 + i_s R_4$$

$$\Rightarrow -V_s + V_{R1} + V_{R2} + V_{R3} + V_{R4} = 0 \rightarrow V_s = V_{R1} + V_{R2} + V_{R3} + V_{R4}$$

$$\Rightarrow V_s = i_s R_1 + i_s R_2 + i_s R_3 + i_s R_4 = i_s (R_1 + R_2 + R_3 + R_4)$$

$$\Rightarrow \frac{V_s}{i_s} = R_s$$

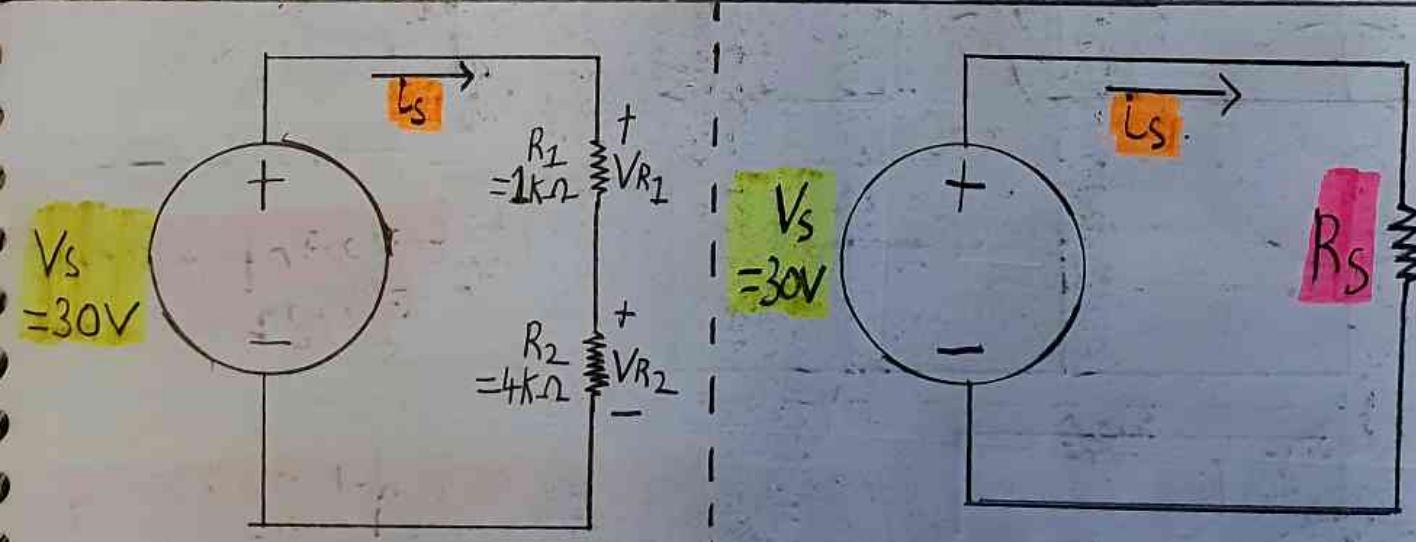

Case 1:

$$-30V + V_{R1} + V_{R2} = 0$$

$$\Rightarrow 30V = V_{R1} + V_{R2}$$

$$\Rightarrow 30V = i_s (R_1 + R_2)$$

$$i_s = \frac{30V}{R_1 + R_2}$$

$$= \frac{30V}{1\text{k}\Omega + 4\text{k}\Omega}$$


$$= 6\text{mA}$$

Case 2:

$$R_s = 1\text{k}\Omega + 4\text{k}\Omega = 5\text{k}\Omega$$

$$V = i_s R \rightarrow i_s = V/R \Rightarrow i_s = \frac{30V}{5\text{k}\Omega} = 6\text{mA}$$

Parallel Resistors

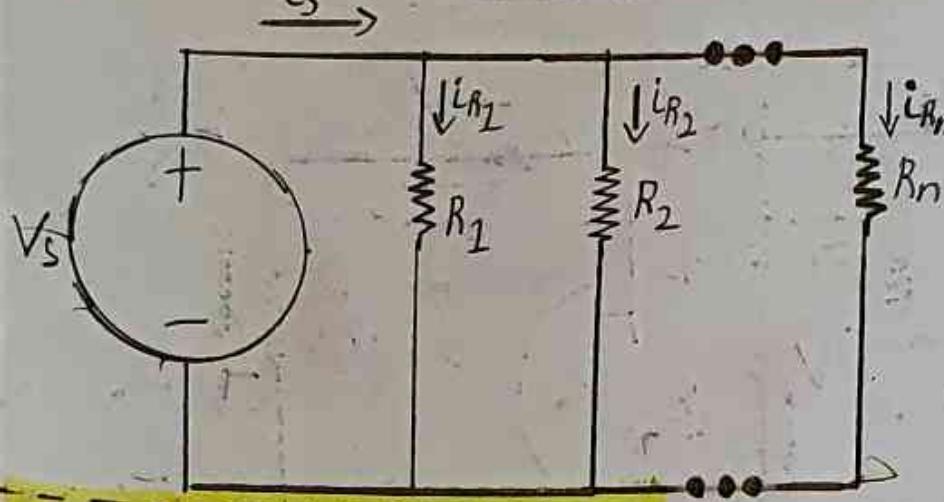


$$\text{Equation: } \frac{1}{R_p} = \sum_{j=1}^n \frac{1}{R_j}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$\Rightarrow R_p = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)^{-1}$$

means infinite

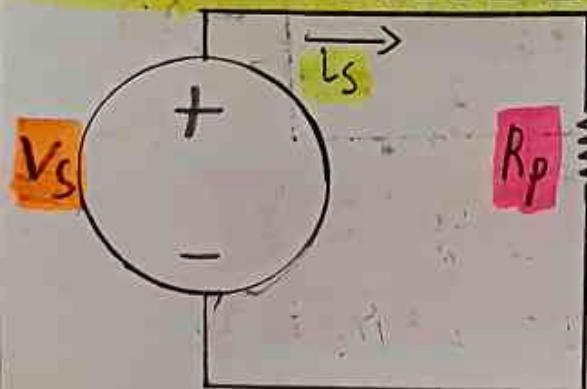


$$i_s = i_{R1} + i_{R2} + \dots + i_{Rn}, V = iR \rightarrow i = V/R$$

$$\therefore i_s = \frac{V_s}{R_1} + \frac{V_s}{R_2} + \dots + \frac{V_s}{R_n} = V_s \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right)$$

$$\therefore \frac{i_s}{V_s} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$V_s = i_s R_p \rightarrow \frac{i_s}{V_s} = \frac{1}{R_p}, R_p = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left(\frac{R_1 + R_2}{R_1 R_2} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2}$$

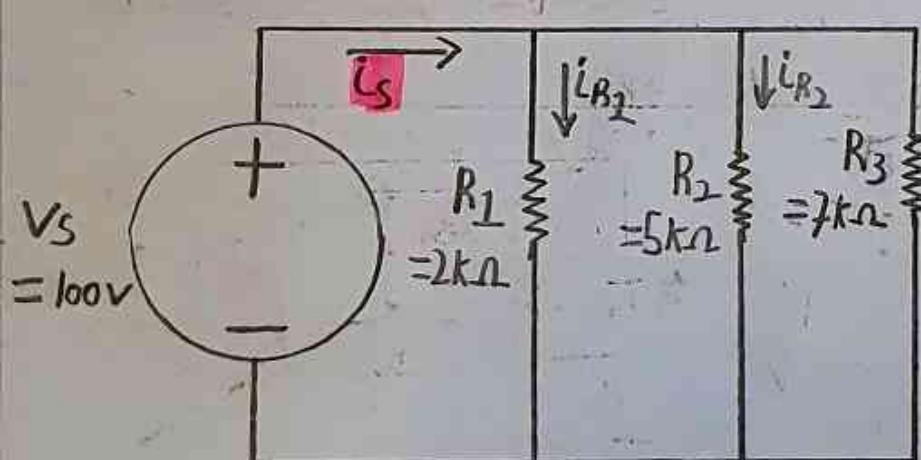

Case 1:

$$i_s - i_{R1} - i_{R2} - i_{R3} = 0$$


$$\therefore i_s = i_{R1} + i_{R2} + i_{R3}$$

$$\therefore i_s = \frac{100V}{2k\Omega} + \frac{100V}{5k\Omega} + \frac{100V}{7k\Omega}$$

$$\therefore i_s = 50mA + 20mA + 14.29mA$$

$$= 84.29mA$$

$$V = iR \rightarrow i = V/R$$


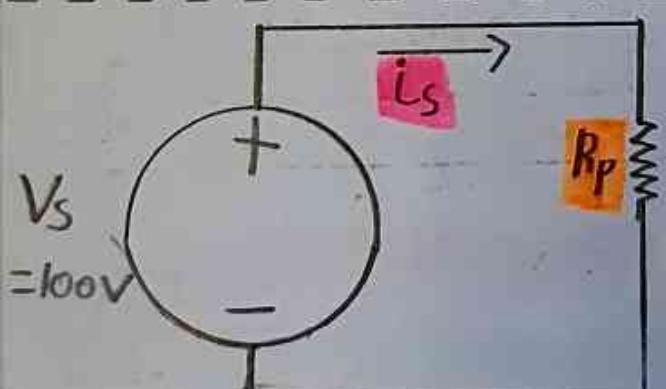


Case 2:



$$R_p = \left(\frac{1}{2k\Omega} + \frac{1}{5k\Omega} + \frac{1}{7k\Omega} \right)^{-1} = 1.186k\Omega$$

$$i_s = 100V / 1.186k\Omega = 84.32mA$$

Series/Parallel Combination of Resistors

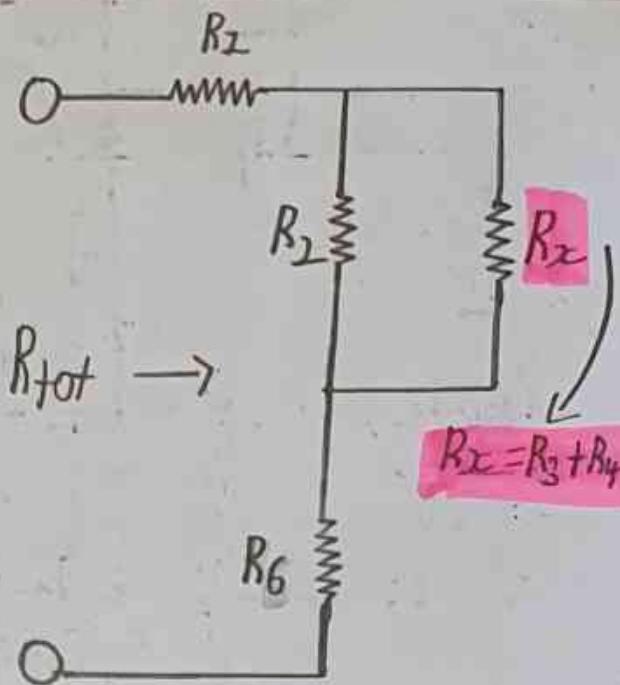
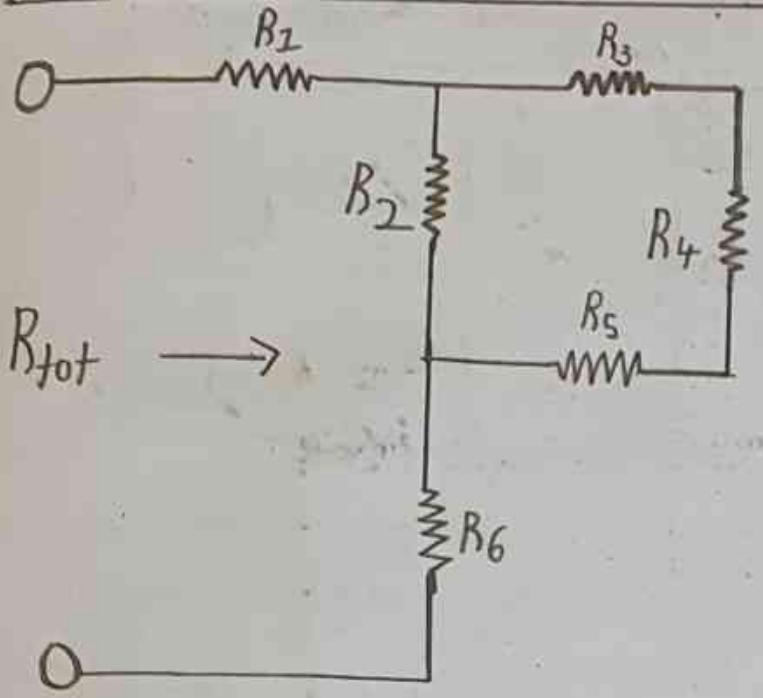


1 2

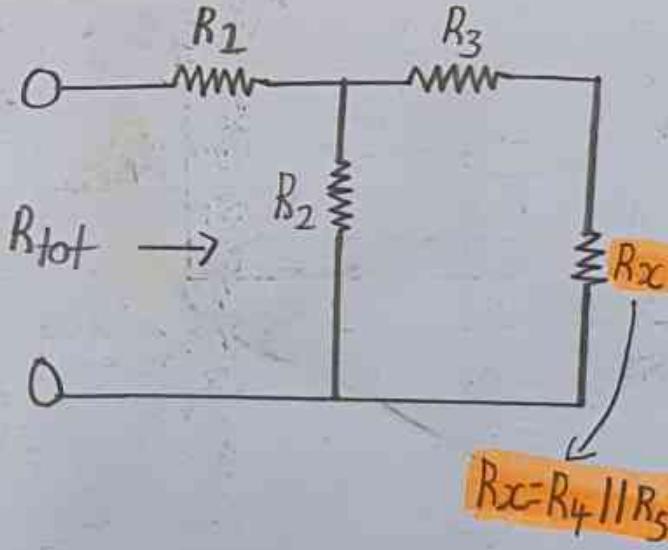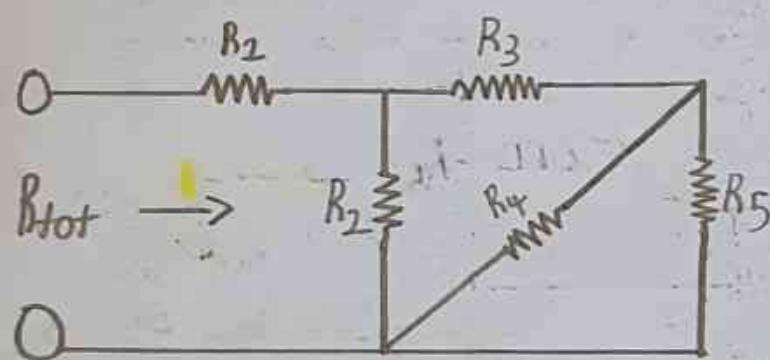

1 2

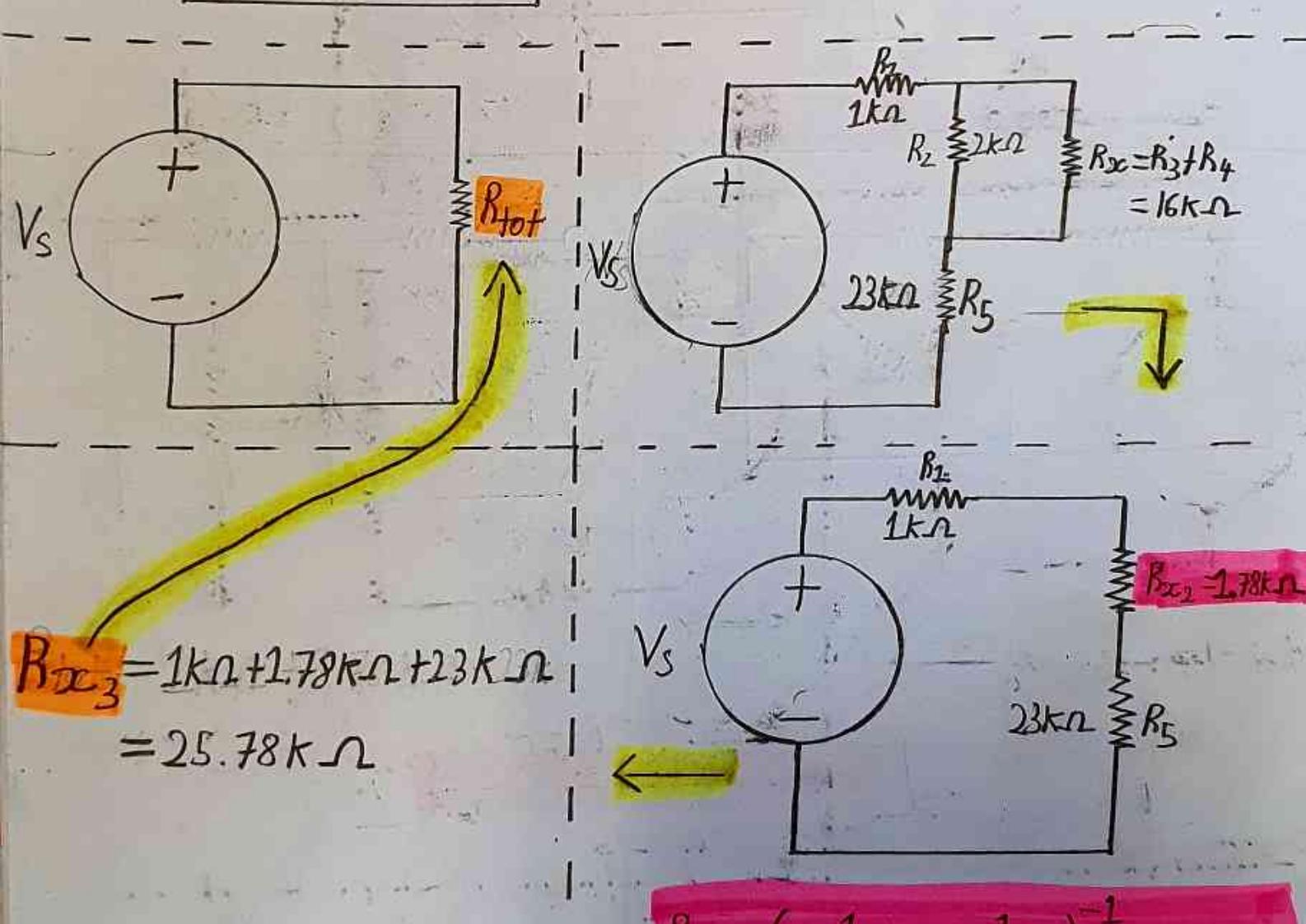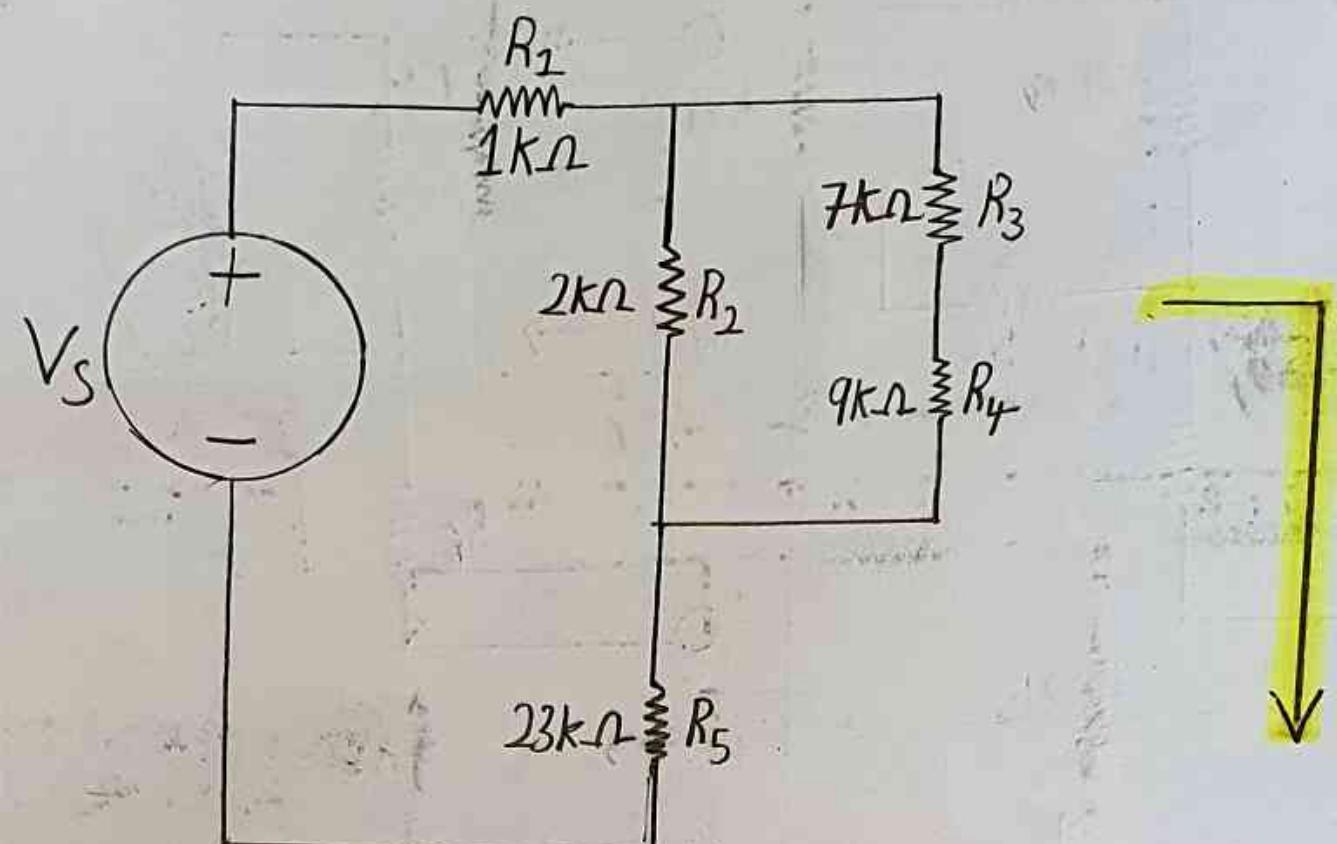Example – Series/Parallel Combinations of Resistors







$$R_{x3} = 1\text{k}\Omega + 1.78\text{k}\Omega + 23\text{k}\Omega$$

$$= 25.78\text{k}\Omega$$

$$R_P = \left(\frac{1}{2\text{k}\Omega} + \frac{1}{16\text{k}\Omega} \right)^{-1} = 1.78\text{k}\Omega$$

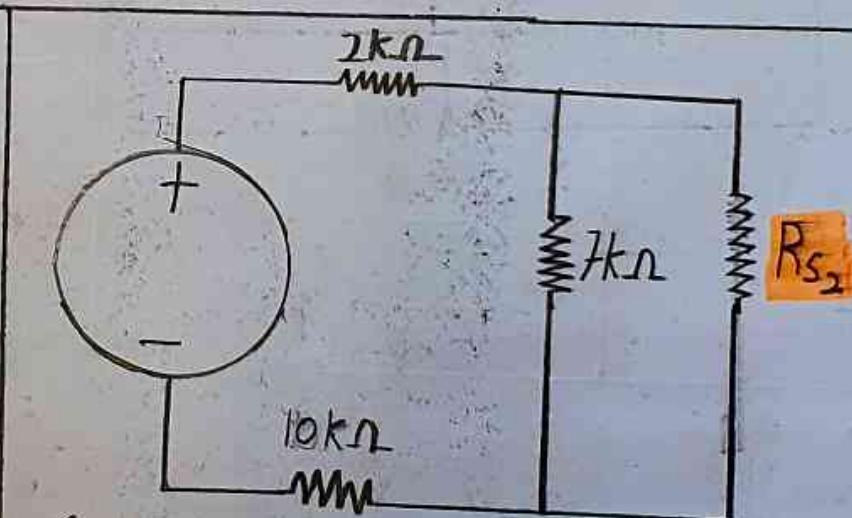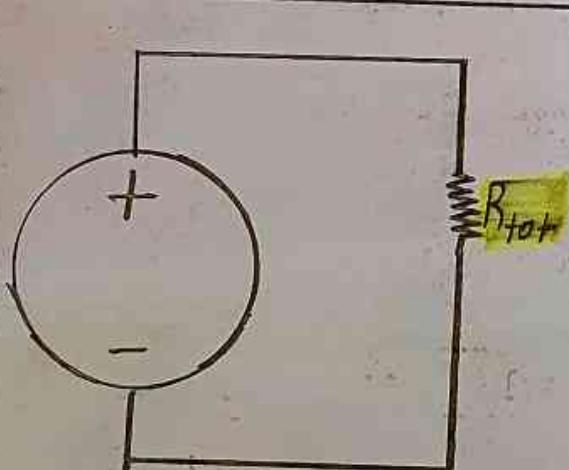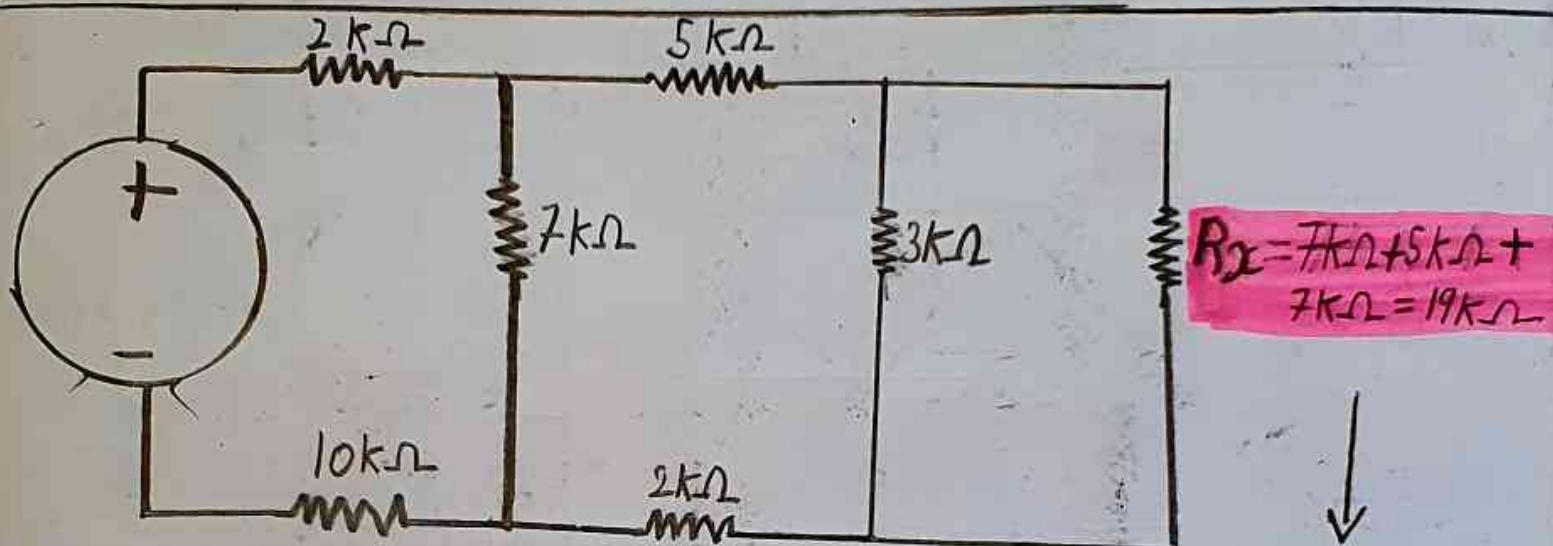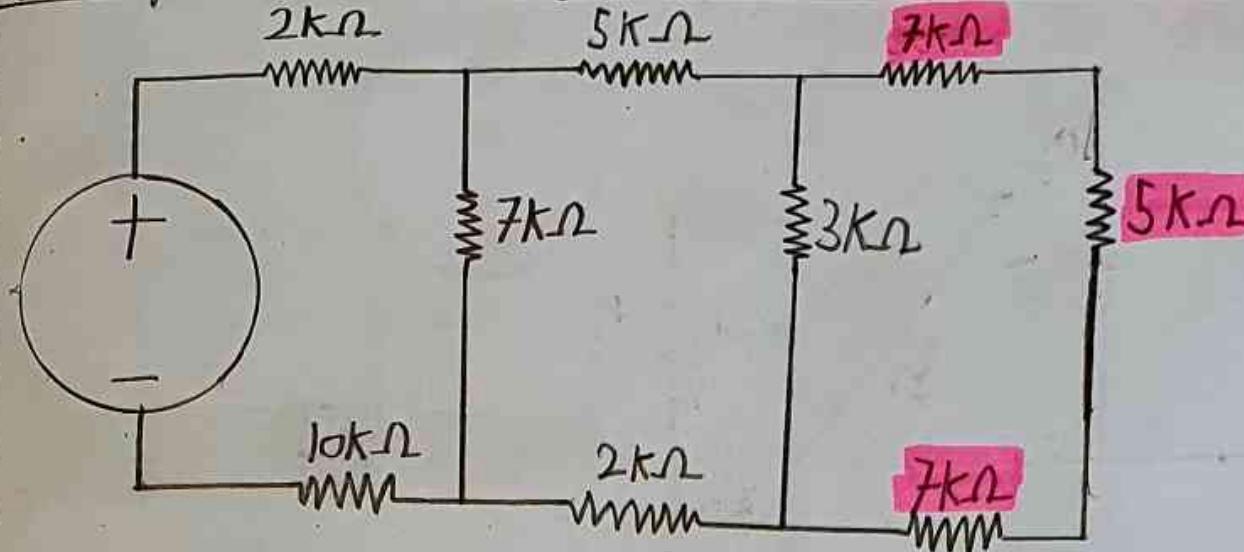Example - Series / Parallel Combinations of Resistors



$$R_{\text{parallel}} = R_p = \left(\frac{1}{7\text{k}\Omega} + \frac{1}{9.59\text{k}\Omega} \right)^{-1}$$

$$= 2\text{k}\Omega + 4.05\text{k}\Omega + 10\text{k}\Omega$$

$$= 16.05\text{k}\Omega$$


$$R_{\text{parallel}} = 16.05\text{k}\Omega$$

$$R_{\text{parallel}} = R_p = \left(\frac{1}{3\text{k}\Omega} + \frac{1}{19\text{k}\Omega} \right)^{-1} = 2.59\text{k}\Omega$$

$$R_{\text{parallel}} = 2.59\text{k}\Omega + 5\text{k}\Omega + 2\text{k}\Omega$$


$$= 9.59\text{k}\Omega$$

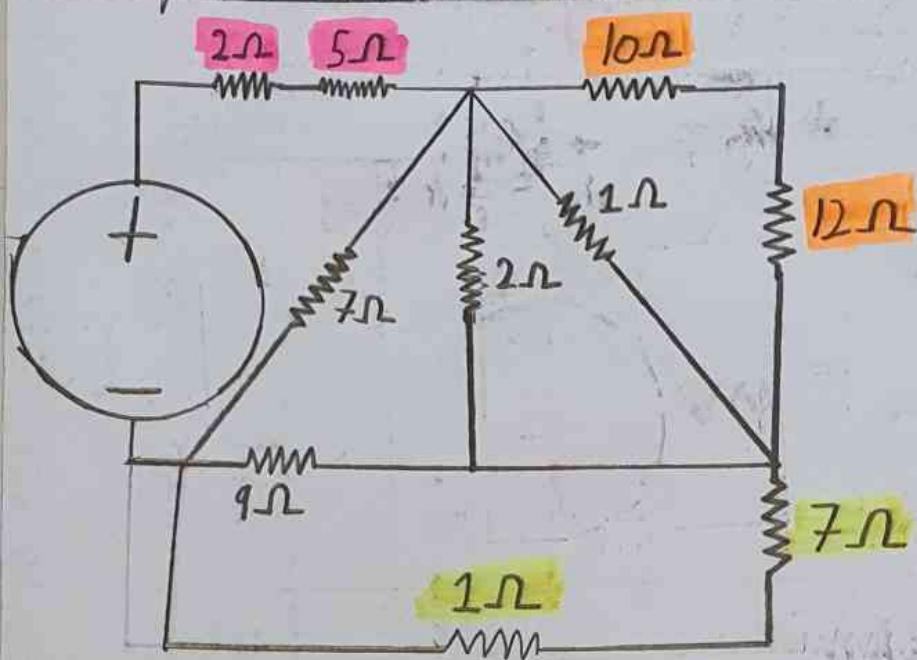Example - Series/Parallel Combinations of Resistors



$$R_{\text{tot}} = 7\Omega + \left(\frac{1}{7\Omega} + \frac{1}{4.875\Omega} \right)^{-1}$$

$$= 9.876\Omega$$

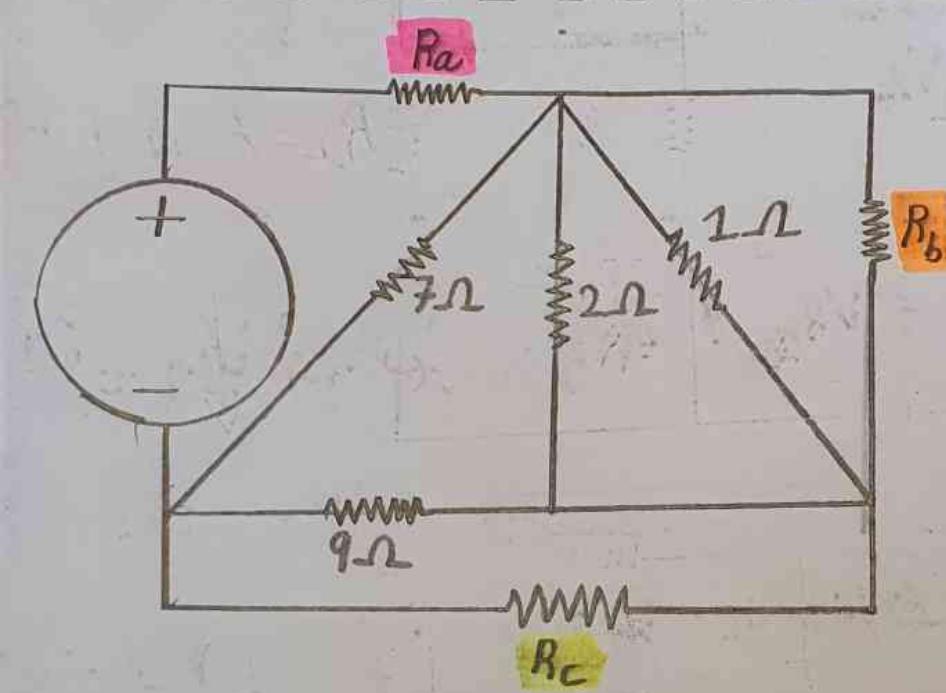

$$R_{bc} = R_{c_2} + R_{b_2}$$


$$= 0.647\Omega + 4.235\Omega$$

$$= 4.882\Omega$$

$$R_a = 5\Omega + 2\Omega = 7\Omega$$

$$R_b = 10\Omega + 12\Omega = 22\Omega$$


$$R_c = 7\Omega + 1\Omega = 8\Omega$$

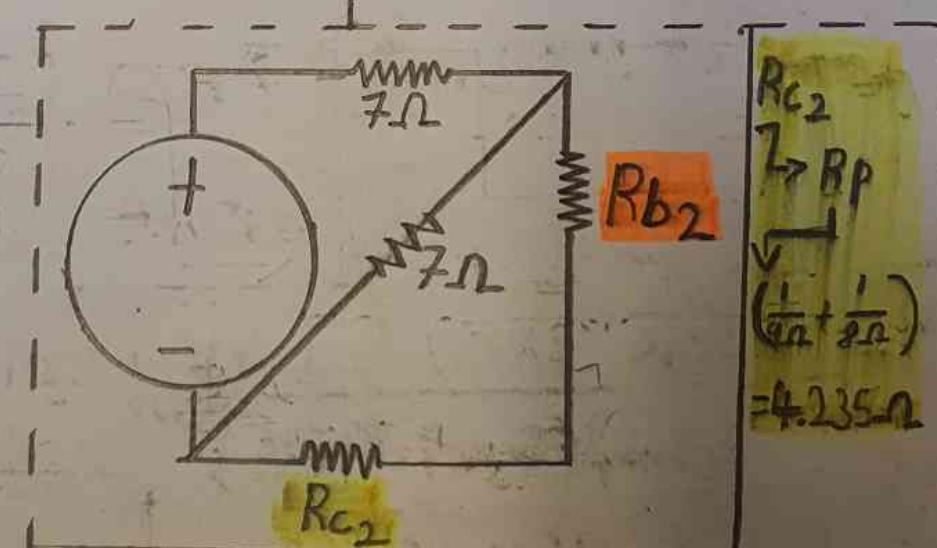

$$R_{b_2} = R_p = \left(\frac{1}{2\Omega} + \frac{1}{1\Omega} + \frac{1}{22\Omega} \right)^{-1}$$

$$= 0.647\Omega$$

Example - Resistive Circuit Analysis

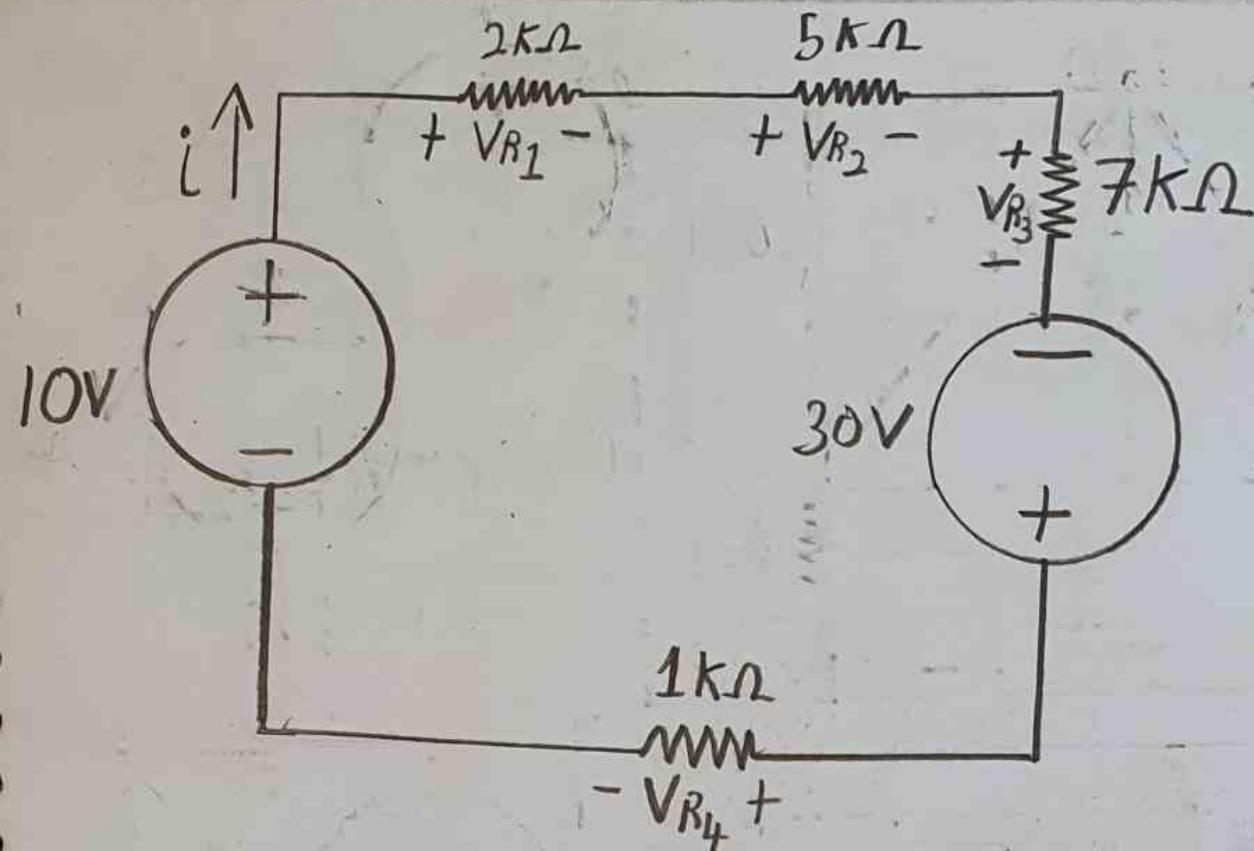

-Loop 1: $-10V + VR_1 + VR_2 + VR_3 - 30V + VR_4 = 0$

$V = LR$

$\rightarrow -10V + i(2k\Omega) + i(5k\Omega) + i(7k\Omega) - 30V + i(1k\Omega) = 0$

$\rightarrow i(2k\Omega + 5k\Omega + 7k\Omega + 1k\Omega) = 40V$

$i = \frac{40V}{15k\Omega} = 2.667mA$

$VR_1 = (2.667mA)(2k\Omega) = 5.334V$


$VR_2 = (2.667mA)(5k\Omega) = 13.335V$

$VR_3 = (2.667mA)(7k\Omega) = 18.669V$

$VR_4 = (2.667mA)(1k\Omega) = 2.667V$

$-10V + 5.334V + 13.335V + 18.669V - 30V + 2.667V = 0$

Example - Resistive Circuit Analysis

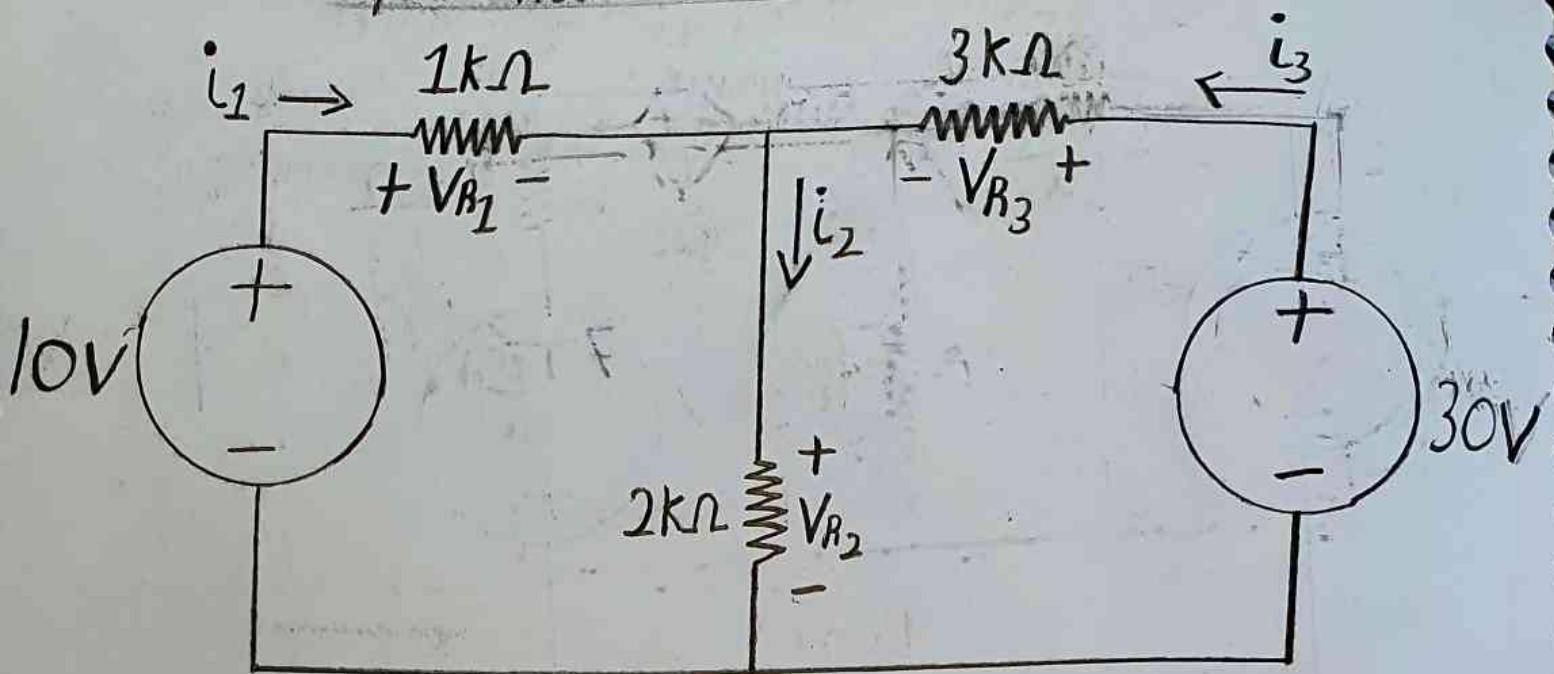

$$i_1 + i_3 - i_2 = 0$$

-Loop 1: $-10V + VR_1 + VR_2 \rightarrow -10 + 1k\Omega i_1 + 2k\Omega i_2 = 0$

-Loop 2: $-VR_2 - VR_3 + 30V \rightarrow -2k\Omega i_2 - 3k\Omega i_3 + 30V = 0$

$$V = LR$$

$$i_1 = \frac{10V - 2k\Omega i_2}{1k\Omega}, \quad i_3 = \frac{30V - 2k\Omega i_2}{3k\Omega}$$


$$\frac{10V - 2k\Omega i_2}{1k\Omega} + \frac{30V - 2k\Omega i_2}{3k\Omega} - i_2 = 0$$

$$\hookrightarrow 10mA - 2i_2 + 10mA - \frac{2}{3}i_2 - i_2 = 0$$

$$\hookrightarrow 20mA = 3.667i_2 \rightarrow i_2 = 5.454mA$$

$$i_1 = 10mA - 2(5.454mA) = -0.908mA, \quad i_3 = 10mA - \frac{2}{3}(5.454mA) = 6.364mA$$

Example - Resistive Circuit Analysis

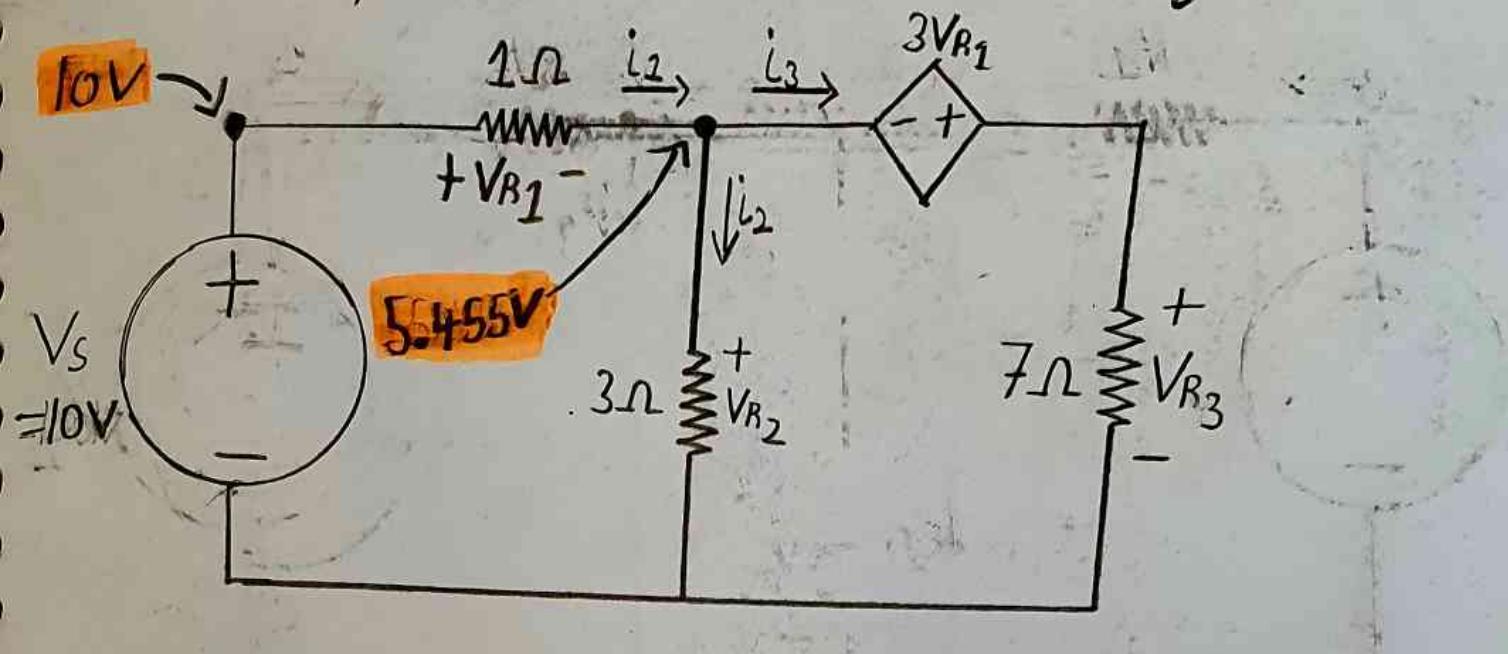

$$i_1 - i_2 - i_3 = 0$$

$$\text{Loop 1: } -10V + V_{R_1} + V_{R_2} = 0 \rightarrow V_{R_1} + V_{R_2} = 10V$$

$$\text{Loop 2: } -V_{R_2} - 3V_{R_1} + V_{R_3} = 0 \rightarrow -3V_{R_1} - V_{R_2} + V_{R_3} = 0V$$

$$V = IR \rightarrow i = V/R$$

$$\textcircled{1} \quad \frac{V_{R_1}}{1\Omega} - \frac{V_{R_2}}{3\Omega} - \frac{V_{R_3}}{7\Omega} = 0V \rightarrow V_{R_1} = 4.545V$$

$$V_{R_2} = 5.455V$$


$$V_{R_3} = 19.091V$$

$$i_1 = 4.545A$$

$$i_2 = 1.818A$$

$$i_3 = 2.727A$$

Definition of Nodal Analysis

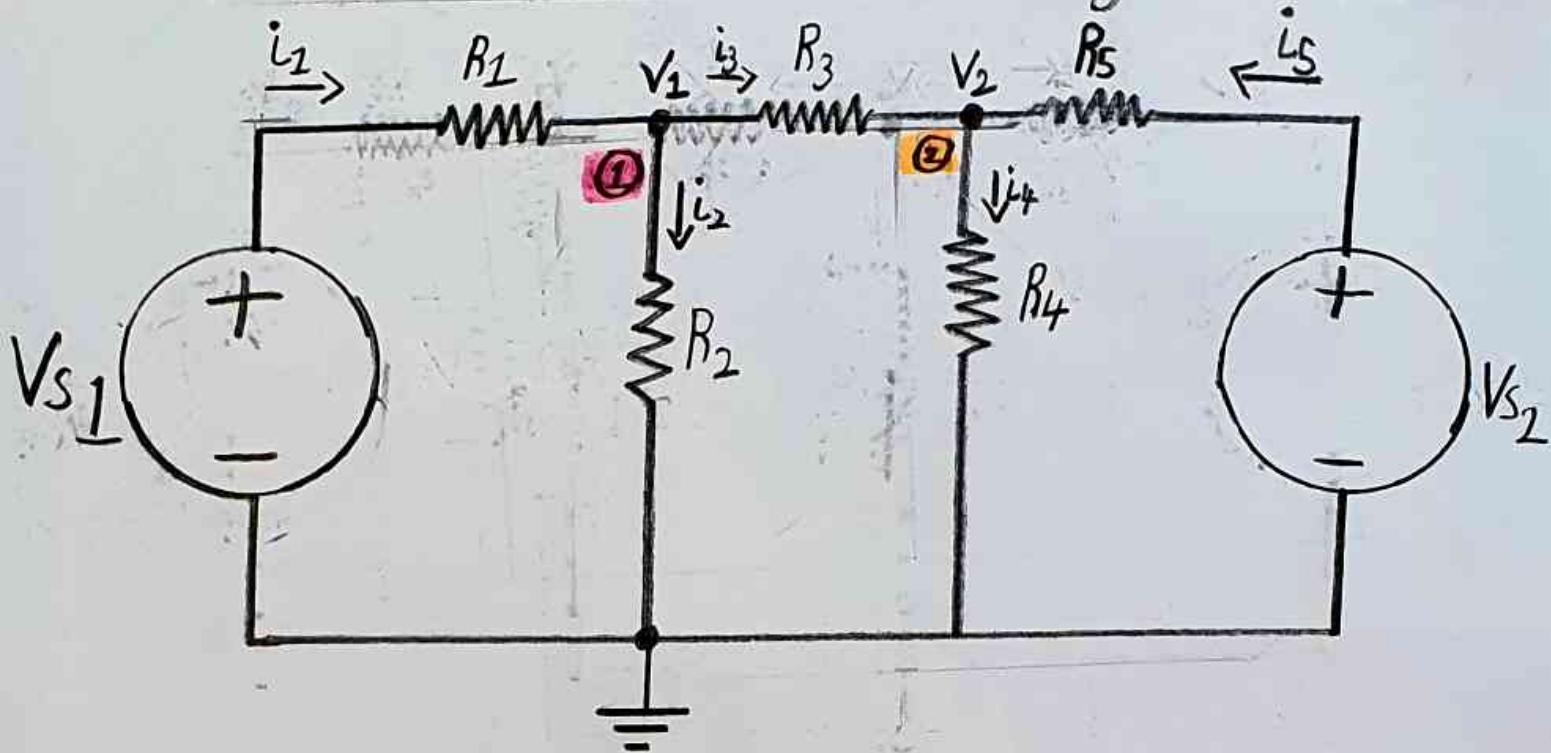

At node 1: $i_1 - i_2 - i_3 = 0$


$$i = V/R, \frac{V_{S1} - V_1}{R_1} - \frac{V_1}{R_2} - \frac{V_1 - V_2}{R_3} = 0$$

At node 2: $i_3 - i_4 + i_5 = 0$

$$i = V/R, \frac{V_1 - V_2}{R_3} - \frac{V_2}{R_4} + \frac{V_{S2} - V_2}{R_5} = 0$$

$$i_1 = \frac{V_{S1} - V_1}{R_1}, i_2 = \frac{V_1}{R_2}, i_3 = \frac{V_1 - V_2}{R_3}, i_4 = \frac{V_2}{R_4}, i_5 = \frac{V_{S2} - V_2}{R_5}$$

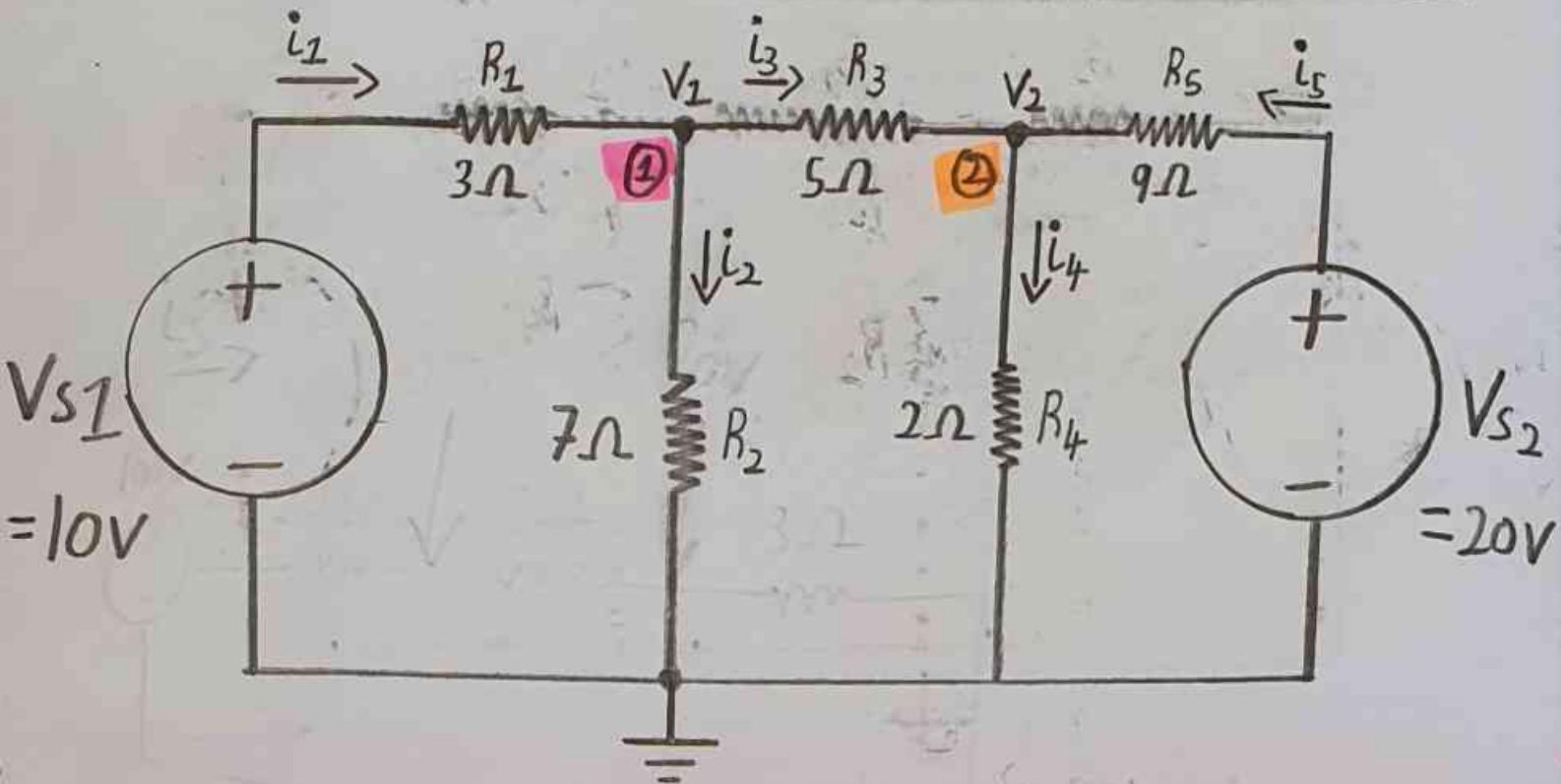Example - Nodal Analysis with Independent sources



At node 1: $i_1 - i_2 - i_3 = 0 \rightarrow \frac{VS_1 - V_1}{R_1} - \frac{V_1}{R_2} - \frac{V_1 - V_2}{R_3} = 0$

$\hookrightarrow \frac{VS_1}{R_1} - \frac{V_1}{R_1} - \frac{V_1}{R_2} - \frac{V_1}{R_3} + \frac{V_2}{R_3} = 0$

$\hookrightarrow \frac{VS_1}{R_1} + V_1 \left(-\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_3} \right) + V_2 \left(\frac{1}{R_3} \right) = 0$

$\hookrightarrow \frac{10V}{3\Omega} + V_1 \left(-\frac{1}{3\Omega} - \frac{1}{7\Omega} - \frac{1}{5\Omega} \right) + V_2 \left(\frac{1}{5\Omega} \right) = 0$

$\hookrightarrow V_1(-0.676) + V_2(0.200) = -3.333 \quad \textcircled{1}$

At node 2: $i_3 - i_4 + i_5 = 0 \rightarrow \frac{V_1 - V_2}{R_3} - \frac{V_2}{R_4} + \frac{VS_2 - V_2}{R_5} = 0$

$\hookrightarrow \frac{V_1}{R_3} - \frac{V_2}{R_3} - \frac{V_2}{R_4} + \frac{VS_2}{R_5} - \frac{V_2}{R_5} = 0$


$\hookrightarrow V_1 \left(\frac{1}{R_3} \right) + V_2 \left(-\frac{1}{R_3} - \frac{1}{R_4} - \frac{1}{R_5} \right) + \frac{VS_2}{R_5} = 0 \quad | V_1 = 6.193V$

$\hookrightarrow V_1 \left(\frac{1}{5\Omega} \right) + V_2 \left(-\frac{1}{5\Omega} - \frac{1}{2\Omega} - \frac{1}{9\Omega} \right) + \frac{20V}{9\Omega} = 0 \quad | V_2 = 4.267V$

$\hookrightarrow V_1(0.200) + V_2(-0.811) = -2.222 \quad \textcircled{2}$

Full Breakdown
Node Voltage Method Circuit analysis with Current Sources
Youtube

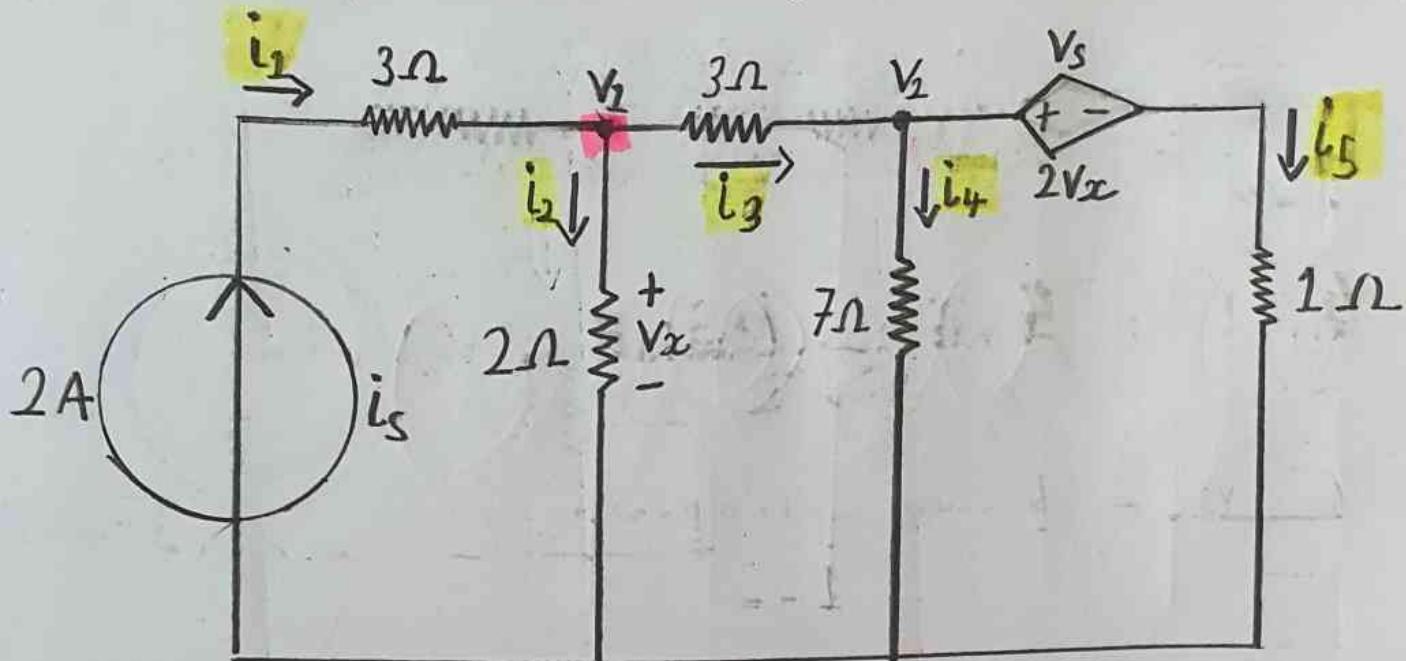Example - Nodal Analysis with Dependant sources



$$\text{At node 1: } i_1 - i_2 - i_3 = 0 \rightarrow 2A - \frac{V_1}{2\Omega} - \frac{V_1 - V_2}{3\Omega} = 0$$

$$\hookrightarrow 2A - \frac{V_1}{2\Omega} - \frac{V_1}{3\Omega} + \frac{V_2}{3\Omega} = 0$$

$$\hookrightarrow V_1 \left(-\frac{1}{2\Omega} - \frac{1}{3\Omega} \right) + V_2 \left(\frac{1}{3} \right) = -2A$$

$$\hookrightarrow V_1 (-0.833) + V_2 (0.333) = -2A \quad ①$$

$$\text{At node 2: } i_3 - i_4 - i_5 = 0 \rightarrow \frac{V_1 - V_2}{3\Omega} - \frac{V_2}{7\Omega} - \frac{V_2 - V_s}{1\Omega} = 0$$

$$\text{but } V_s = 2V_x = 2V_1$$

$$\hookrightarrow \frac{V_1 - V_2}{3\Omega} - \frac{V_2}{7\Omega} - \frac{V_2 - (2V_1)}{1\Omega} = 0 \quad \rightarrow$$

$$\hookrightarrow \frac{V_1}{3\Omega} - \frac{V_2}{3\Omega} - \frac{V_2}{7\Omega} - \frac{V_2}{1\Omega} + \frac{2V_1}{1\Omega} = 0$$

$$\hookrightarrow V_1 \left(\frac{1}{3\Omega} - \frac{2}{1\Omega} \right) + V_2 \left(-\frac{1}{3\Omega} - \frac{1}{7\Omega} - 1 \right) = 0 \quad | V_1 = 6.522V$$

$$\hookrightarrow V_1 (2.333) + V_2 (-1.476) = 0 \quad ② \quad | V_2 = 10.309V$$

$$i_1 = 2A$$


$$i_2 = \frac{V_1}{2\Omega} = \frac{6.522V}{2\Omega} = 3.261A$$

$$i_3 = \frac{V_1 - V_2}{3\Omega} = \frac{6.522V - 10.309V}{3\Omega} = -1.262A$$

$$i_5 = \frac{V_2 - V_s}{1\Omega} = \frac{10.309V - 2(6.522V)}{1\Omega} = -2.735A$$

$$i_4 = \frac{V_2}{7\Omega} = \frac{10.309V}{7\Omega} = 1.473A$$

Definition of Loop Analysis

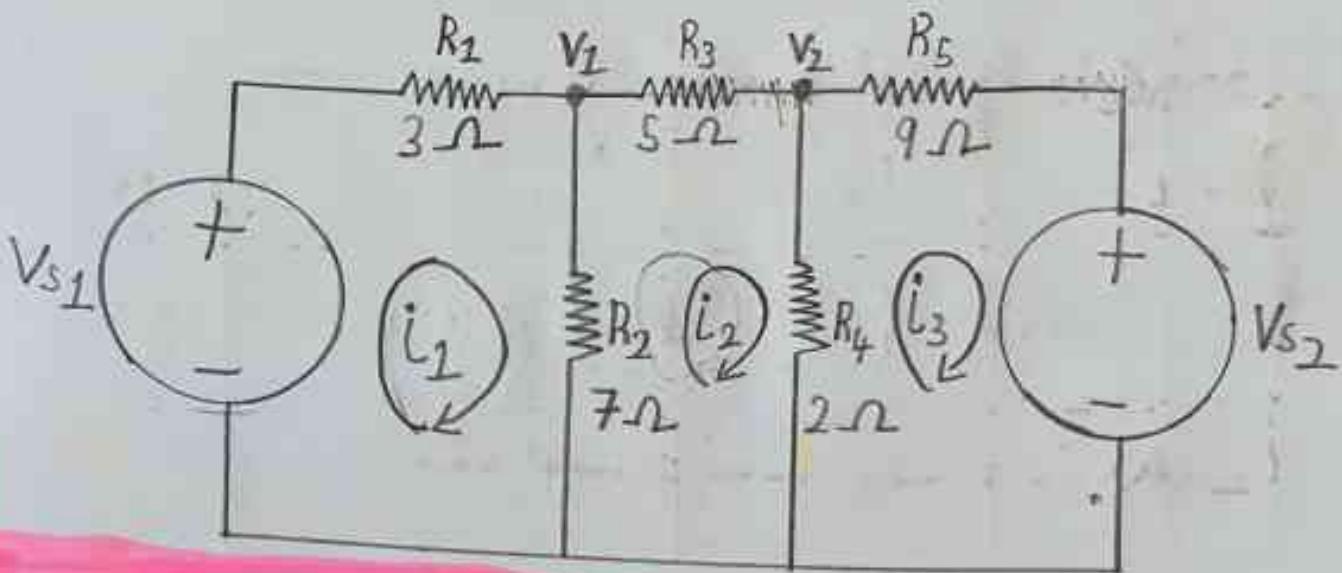

Loop 1: $-Vs_1 + i_1 R_1 + (i_1 - i_2) R_2 = 0$

$\hookrightarrow -Vs_1 + i_1 R_1 + i_1 R_2 - i_2 R_2 = 0$

$\hookrightarrow i_1(R_1 + R_2) + i_2(-R_2) = Vs_1 \quad \textcircled{1}$

Loop 2: $(i_2 - i_1) R_2 + i_2 R_3 + (i_2 - i_3) R_4 = 0$

$\hookrightarrow i_2 R_2 - i_1 R_2 + i_2 R_3 + i_2 R_4 - i_3 R_4 = 0$

$\hookrightarrow i_1(-R_2) + i_2(R_2 + R_3 + R_4) + i_3(-R_4) = 0 \quad \textcircled{2}$

Loop 3: $(i_3 - i_2) R_4 + i_3 R_5 + Vs_2 = 0$

$\hookrightarrow i_3 R_4 - i_2 R_4 + i_3 R_5 + Vs_2 = 0$

$\hookrightarrow i_2(-R_4) + i_3(R_4 + R_5) = -Vs_2 \quad \textcircled{3}$

→
Next Page

Example - Loop Analysis with Independent Sources

$$i_1(R_1 + R_2) + i_2(-R_2) = V_{S1} \quad ①$$

$$i_1(-R_2) + i_2(R_2 + R_3 + R_4) + i_3(-R_4) = 0 \quad ②$$

$$i_2(-R_4) + i_3(R_4 + R_5) = -V_{S2} \quad ③$$

$$\text{Loop 1: } i_1(10\Omega) + i_2(-7\Omega) = 10V \quad ①$$

$$\text{Loop 2: } i_1(-7\Omega) + i_2(14\Omega) + i_3(-2\Omega) = 0 \quad ②$$

$$\text{Loop 3: } i_2(-2\Omega) + i_3(11\Omega) = -20V \quad ③$$

$$① i_1 = \frac{10V + 7i_2}{10\Omega}, \quad ③ i_3 = \frac{-20V + 2i_2}{11\Omega}$$

↪ Plug in equation ②:

$$-7\Omega \left(\frac{10V + 7i_2}{10\Omega} \right) + 14i_2 + -2 \left(\frac{-20V + 2i_2}{11\Omega} \right) = 0$$

$$\hookrightarrow -7A - \frac{49}{10}i_2 + 14i_2 + \frac{40}{11}A - \frac{4}{11}i_2 = 0$$

$$\hookrightarrow -3.364A = -8.736i_2 \rightarrow i_2 = 0.385A$$

$$(i_1 - i_2)R_2 \rightarrow (1.269 - 0.385)7\Omega$$

$$\hookrightarrow V_1 = 6.188V$$

$$(i_2 - i_3)R_4 \rightarrow (0.385 + 1.748)2\Omega$$

$$\hookrightarrow V_2 = 4.266V$$

$$i_1 = 1.269A$$


$$i_3 = -1.748A$$

From Nodal Analysis:

$$V_1 = 6.193V$$

$$V_2 = 4.267V$$

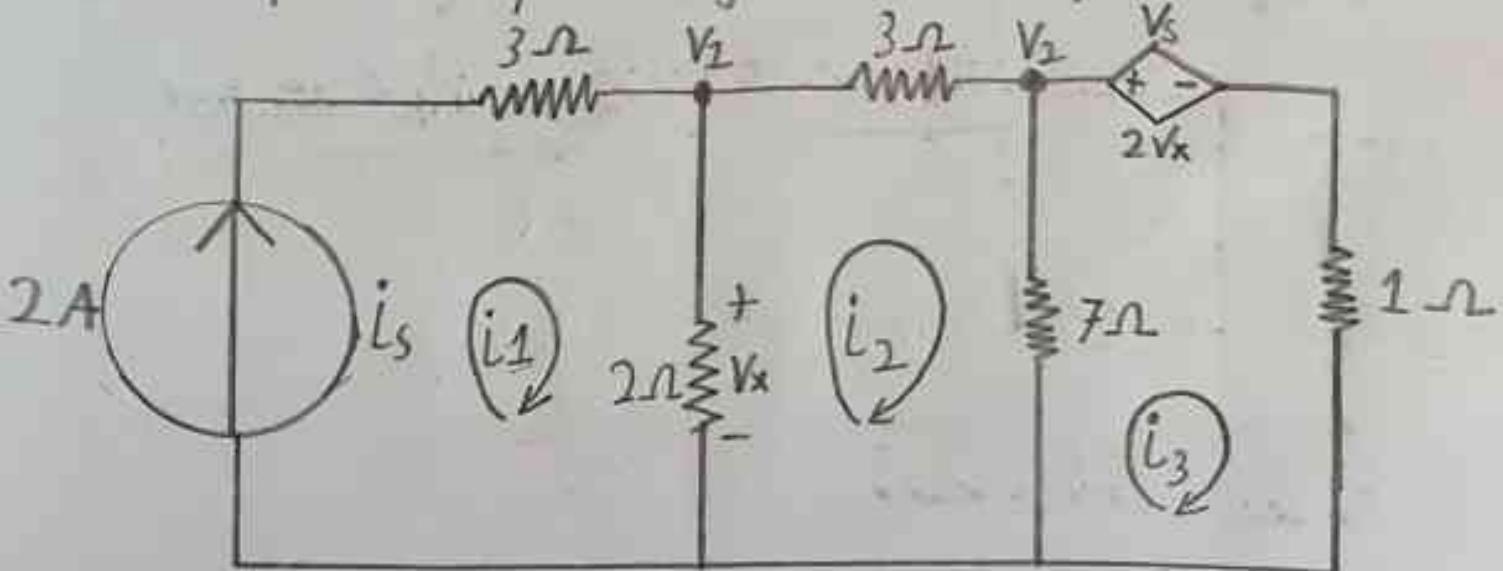Example - Loop Analysis With Dependant Sources



$$\text{Loop 1: } i_1 = 2 \text{ A} \quad ①$$

$$\text{Loop 2: } (i_2 - i_1)2\Omega + i_2(3\Omega) + (i_2 - i_3)7\Omega = 0$$

$$\Rightarrow 2i_2 - 2i_1 + 3i_2 + 7i_2 - 7i_3 = 0$$

$$\Rightarrow i_1(-2\Omega) + i_2(2\Omega + 3\Omega + 7\Omega) + i_3(-7\Omega) = 0$$

$$\Rightarrow i_1(-2\Omega) + i_2(12\Omega) + i_3(-7\Omega) = 0 \quad ②$$

$$\text{Loop 3: } (i_3 - i_2)7\Omega + 2V_x + i_3(1\Omega) = 0$$

$$\text{but } V_x = (i_2 - i_1)2\Omega$$

$$\Rightarrow (i_3 - i_2)7\Omega + 2(i_2 - i_1)2\Omega + i_3(1\Omega) = 0$$

$$\Rightarrow 7i_3 - 7i_2 + 4i_1 - 4i_2 + i_3 = 0$$

$$\Rightarrow i_1(4\Omega) + i_2(-7\Omega - 4\Omega) + i_3(7\Omega + 1\Omega) = 0$$

$$\Rightarrow i_1(4\Omega) + i_2(-11\Omega) + i_3(8\Omega) = 0 \quad ③$$

$$i_1 = 2A$$

$$i_2 = -1.263A$$

$$i_3 = -2.737A$$

from Nodal Analysis :

$$V_1 = 6.522V, V_2 = 10.309V$$

$$V_1 = (i_1 - i_2) 2\Omega$$

$$\Rightarrow (2A + 1.263A) 2\Omega$$




$$\Rightarrow V_1 = 6.526V$$

$$V_2 = (i_2 - i_3) 7\Omega$$

$$\Rightarrow (-1.263A + 2.737A) 7\Omega$$

$$\Rightarrow V_2 = 10.318V$$

Superposition Theorem

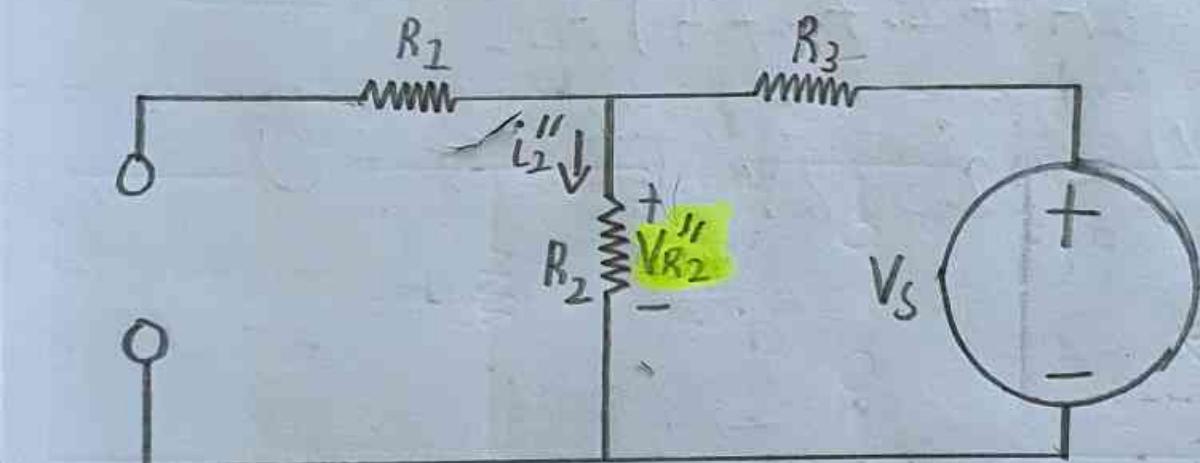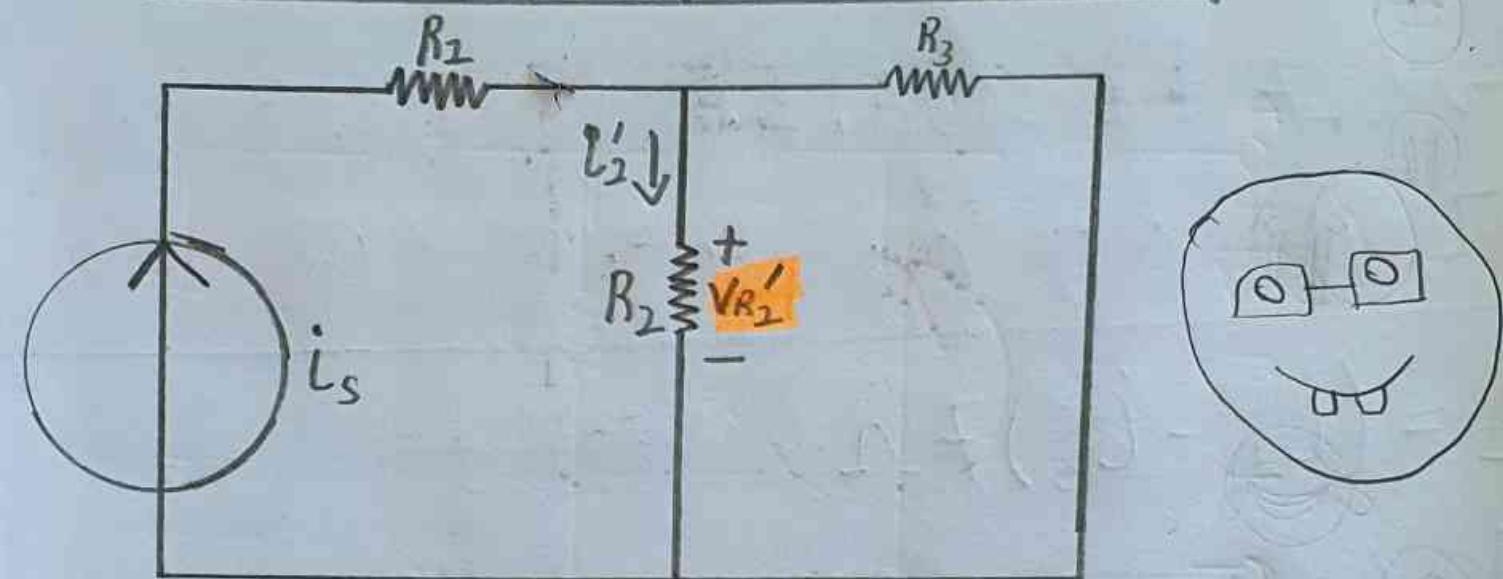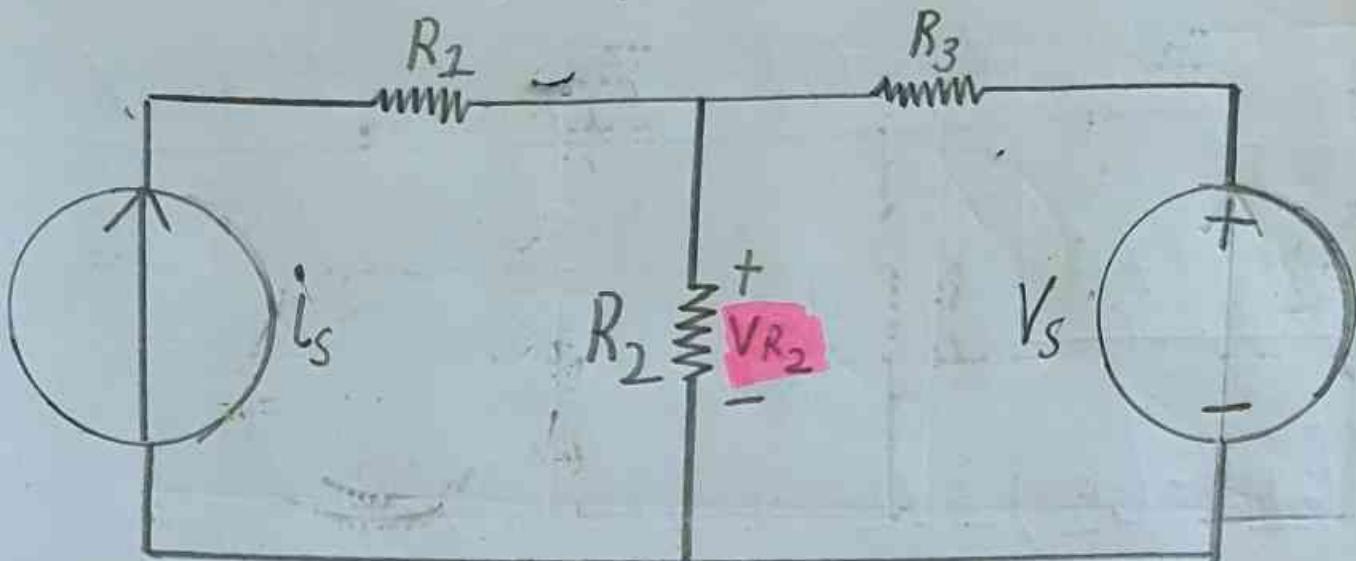

$$V_{R_2} = V_{R_2}' + V_{R_2}''$$

Solving for V_{R_2}' :

$$i_2' = \frac{i_s(R_3)}{R_2 + R_3} \rightarrow V_{R_2}' = i_2'(R_2)$$




Current Division

Solving for V_{R_2}'' :

$$V_{R_2}'' = \frac{V_s(R_2)}{R_2 + R_3}$$

Voltage Division

Example - Superposition Theorem

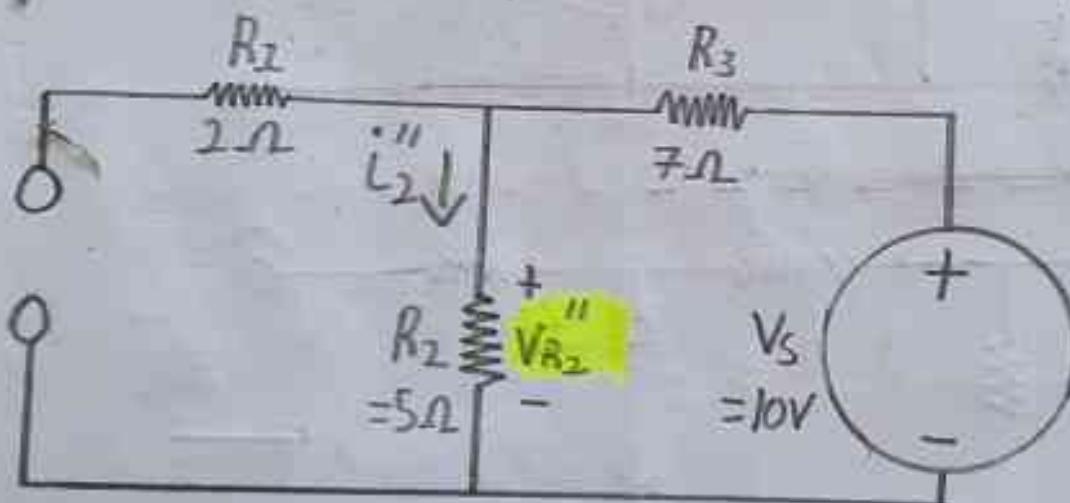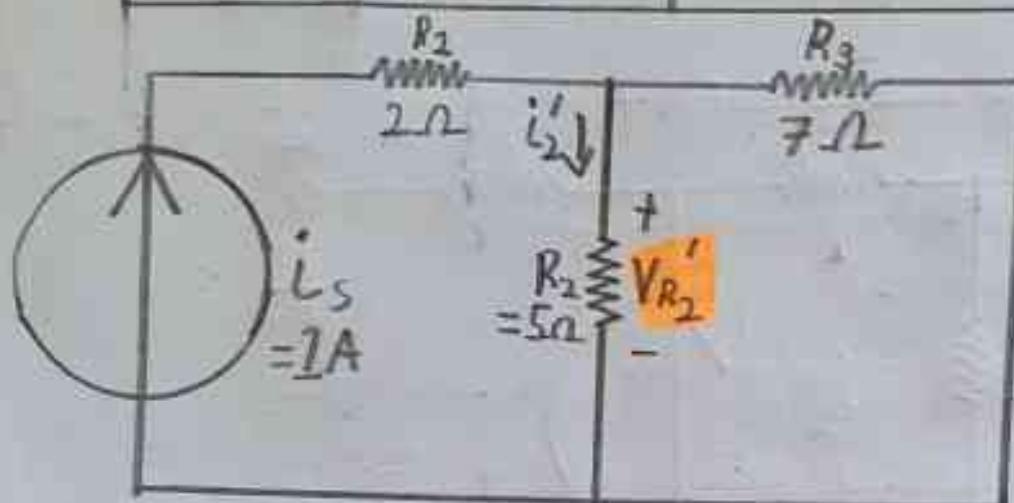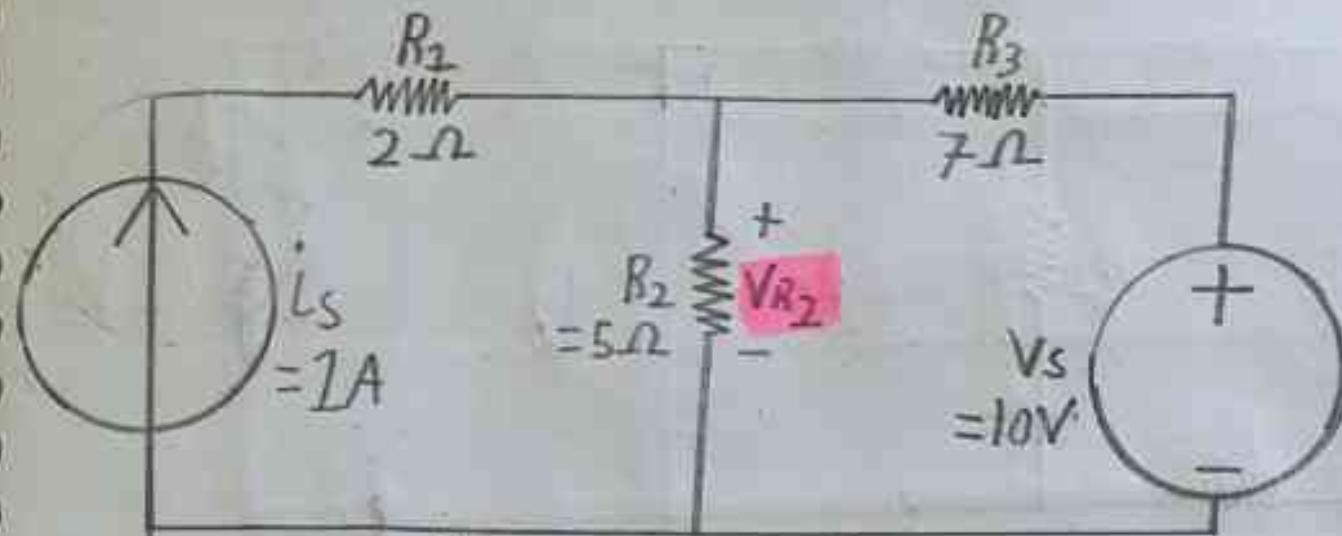

$$V_{R_2} = V'_{R_2} + V''_{R_2}$$

Solving for V'_{R_2} :

$$i'_2 = \frac{1A(7\Omega)}{5\Omega + 7\Omega} = 0.583 A$$

$$V'_{R_2} = 0.583 A \times 5 \Omega$$

$$V'_{R_2} = 2.915 V$$





Solving for V''_{R_2} :

$$V''_{R_2} = \frac{10V(5\Omega)}{5\Omega + 7\Omega}$$



$$V''_{R_2} = 4.167 V$$

$$V_{R_2} = 2.915 V + 4.167 V \rightarrow V_{R_2} = 7.082 V$$

Thevenin's Theorem

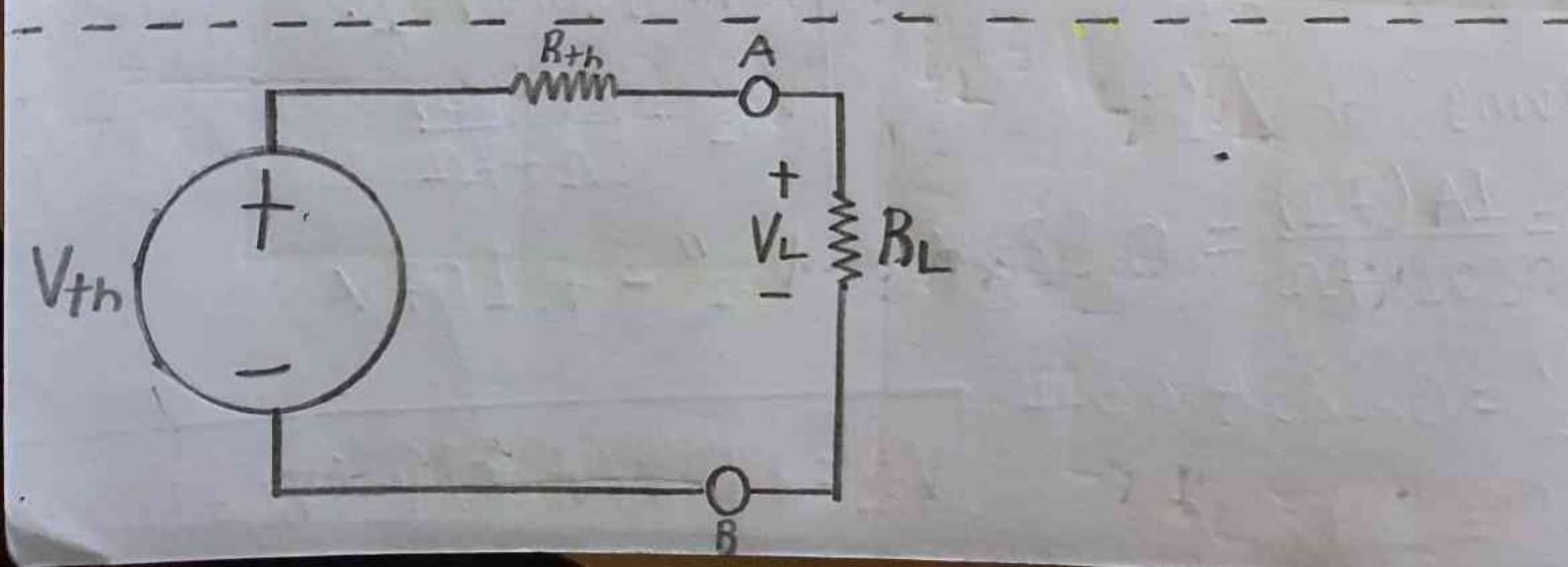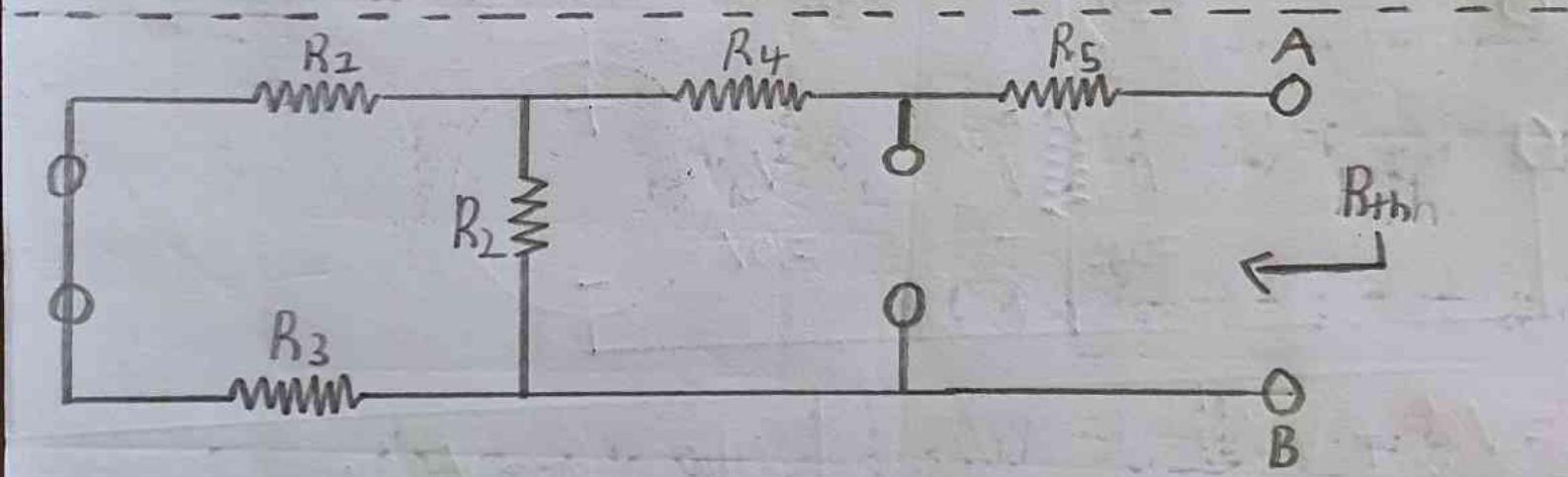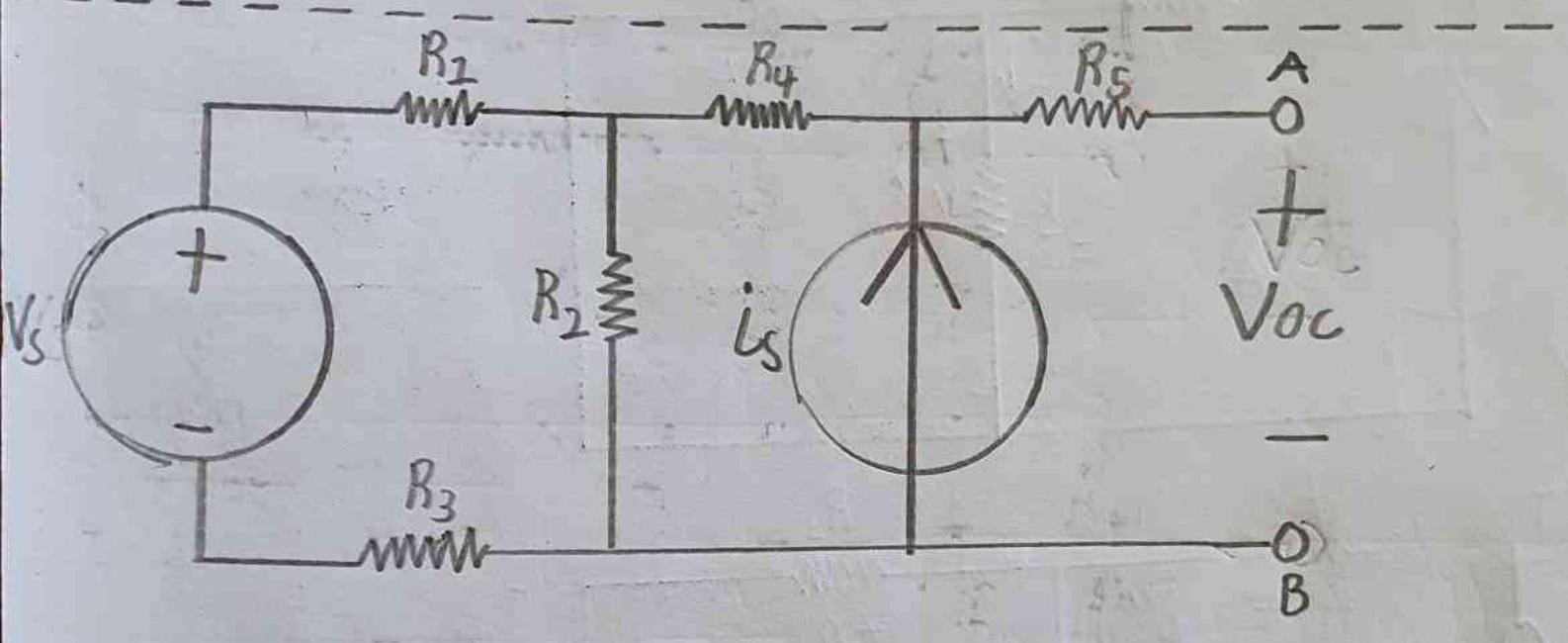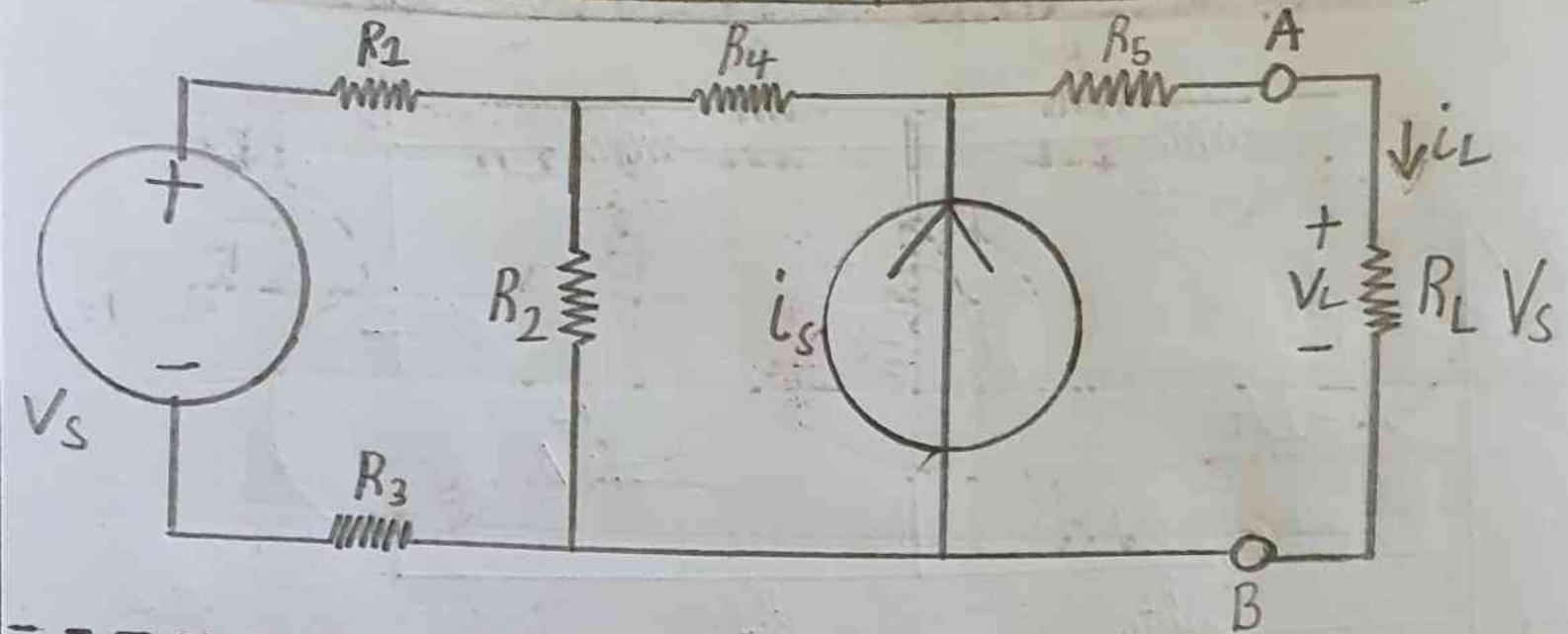

Example - Thevenin's Theorem Part 1

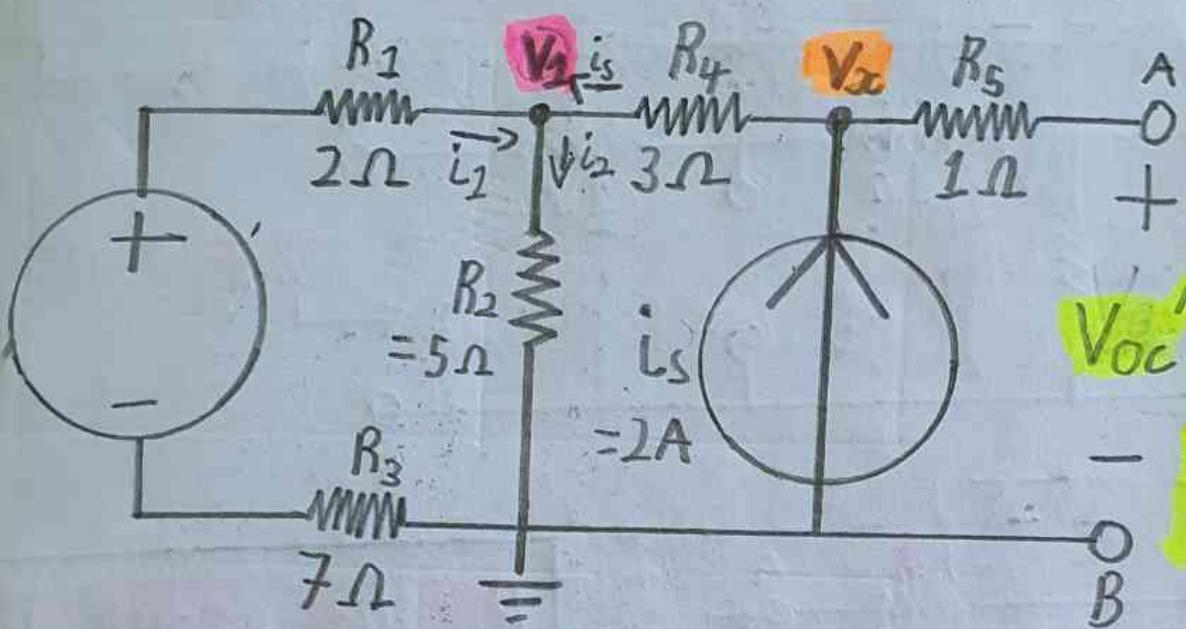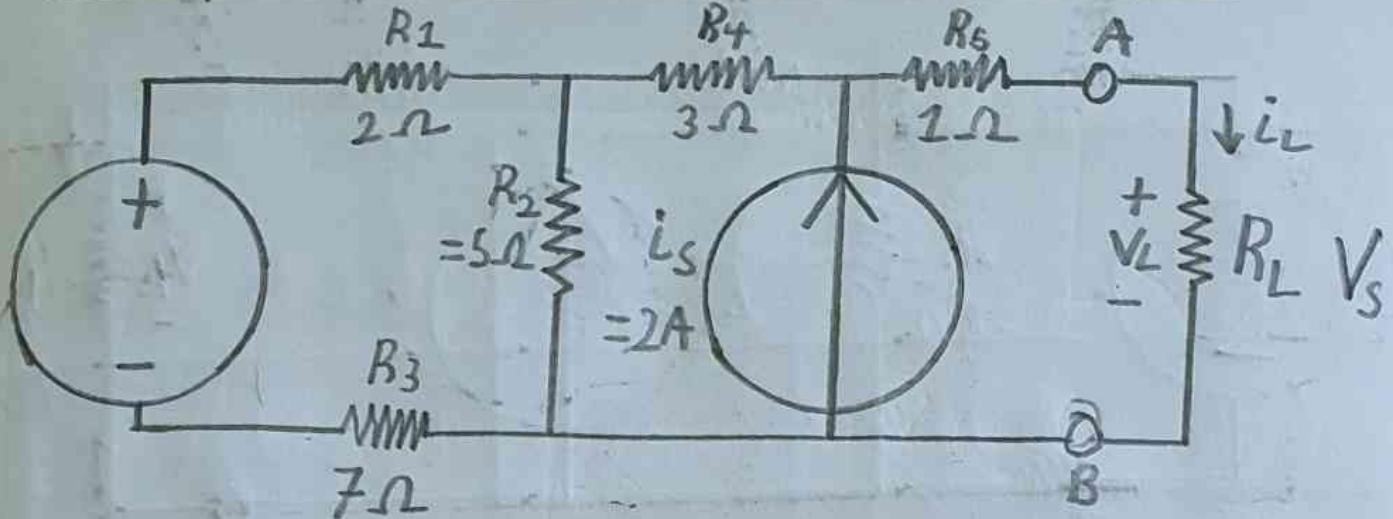

$$i_1 - i_2 + i_s = 0 \rightarrow \frac{V_s - V_1}{2\Omega} - \frac{V_1}{5\Omega} + 2A = 0$$

$$\rightarrow \frac{V_s}{2\Omega} - \frac{V_1}{2\Omega} - \frac{V_1}{5\Omega} + 2A = 0$$




$$\rightarrow V_1 \left(-\frac{1}{2\Omega} - \frac{1}{5\Omega} \right) = -2A - \frac{10V}{2\Omega} \rightarrow V_1 (-0.7) = -7A$$

$$\rightarrow V_1 = \frac{-7}{-0.7}, \quad V_1 = 10V$$

$$V_x = 10V + 2A(3\Omega) = 16V$$

$$V_x = V_{oc} = 16V = V_{th}$$

Example - Thevenin's Theorem Part 2

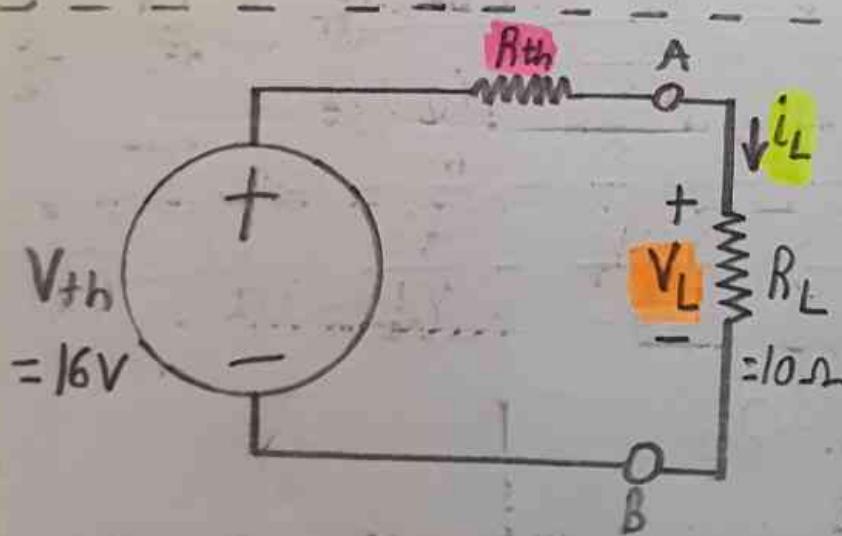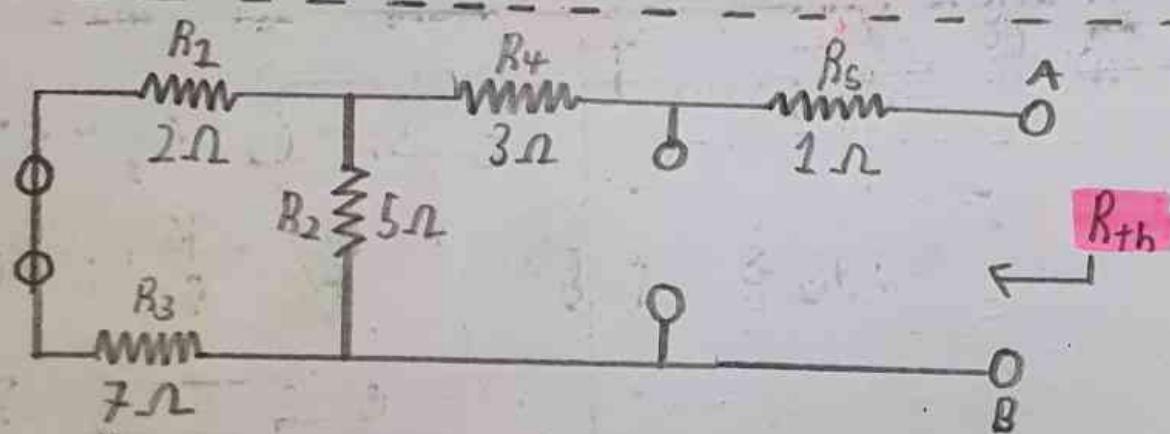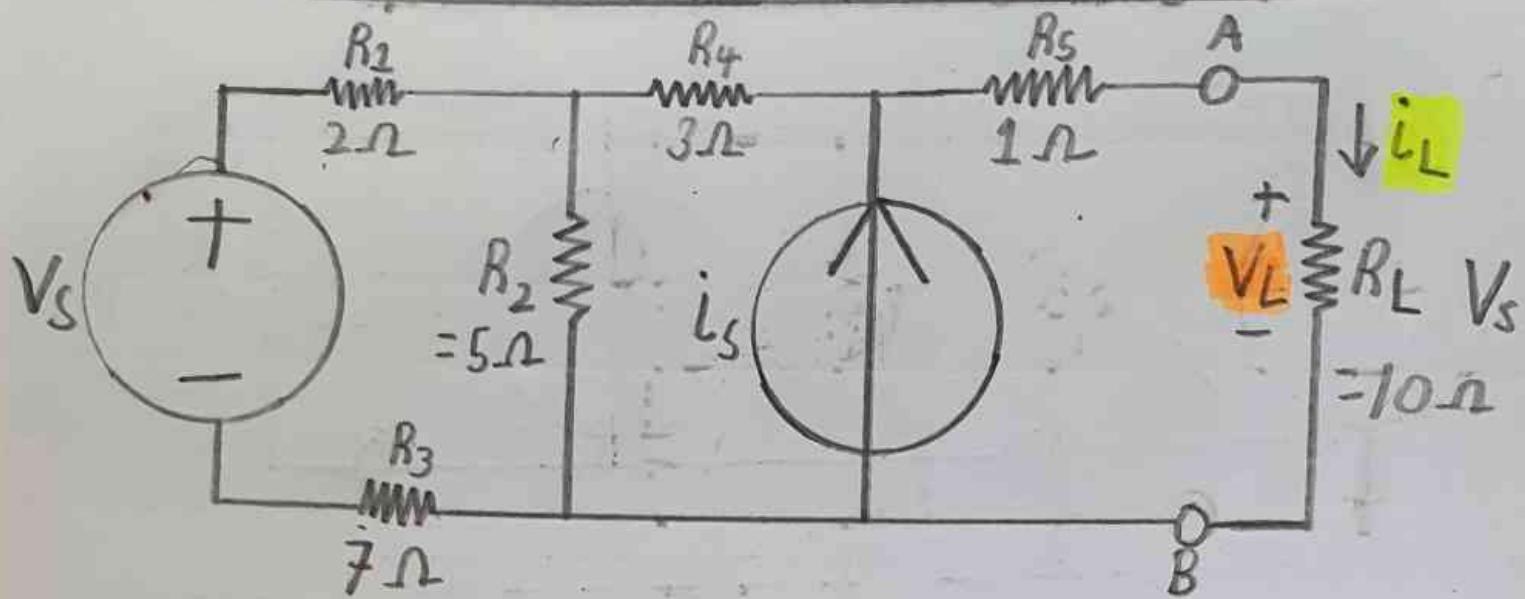

$$R_{th} = \left((2\Omega + 7\Omega) || 5\Omega \right) / 3\Omega + 1\Omega$$

$$\Rightarrow 9\Omega || 5\Omega = \left(\frac{1}{9\Omega} + \frac{1}{5\Omega} \right)^{-1}$$

$$R_{th} = 3.214\Omega + 3\Omega + 1\Omega$$

$$R_{th} = 7.214\Omega$$





$$i_L = V_L / R_L$$

$$\Rightarrow i_L = 9.295V / 10\Omega$$

$$\Rightarrow i_L = 0.9295A$$

$$V_L = \frac{16V(10\Omega)}{R_{th} + 10\Omega} = 9.295V$$

Norton's Theorem

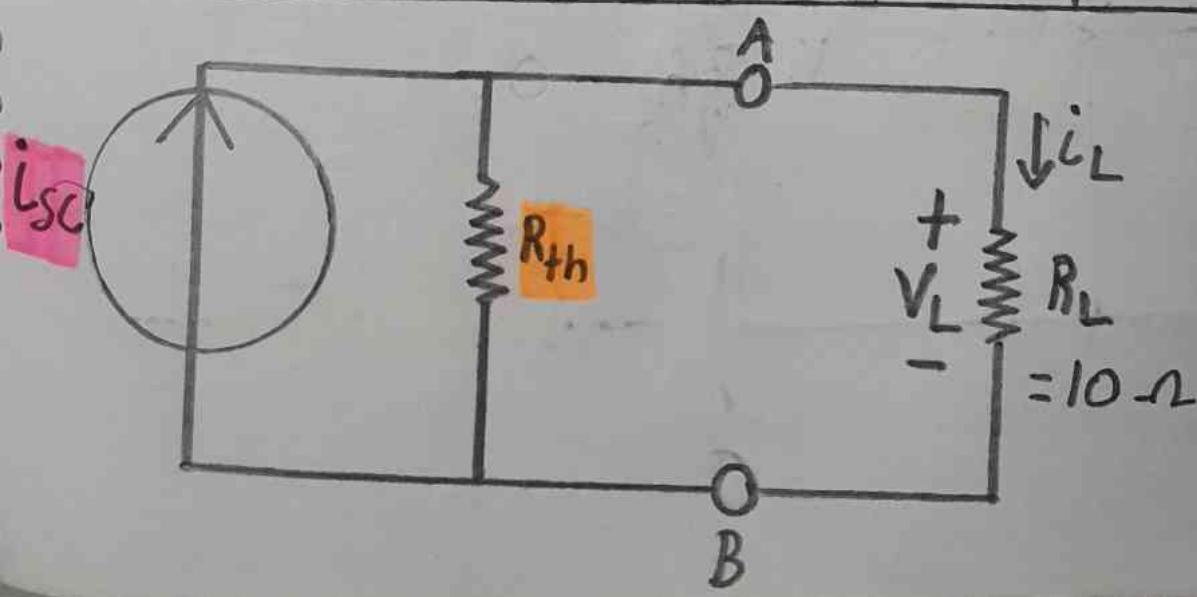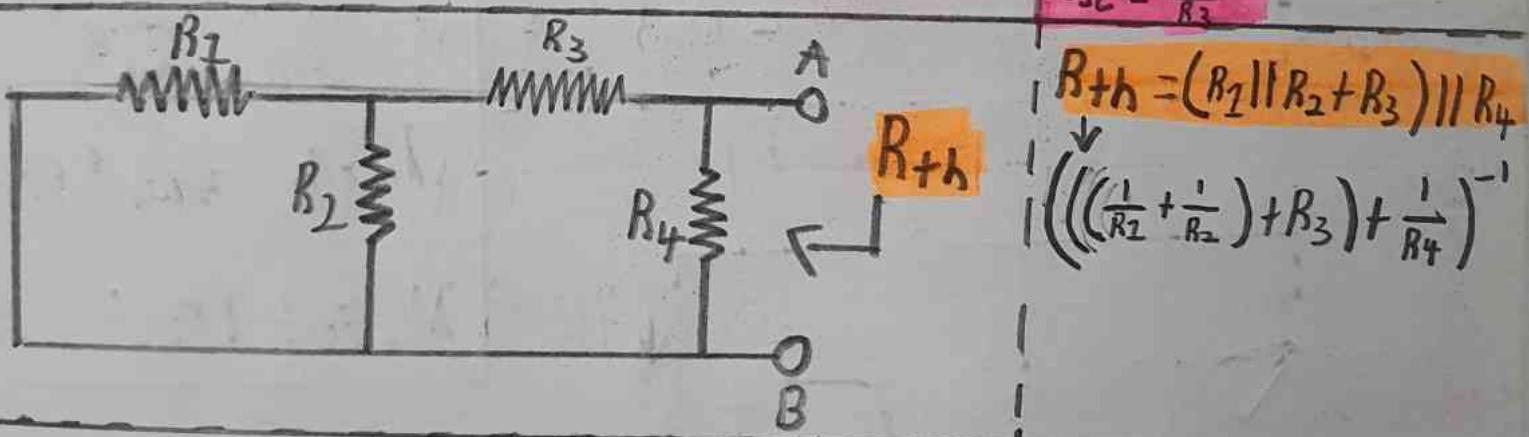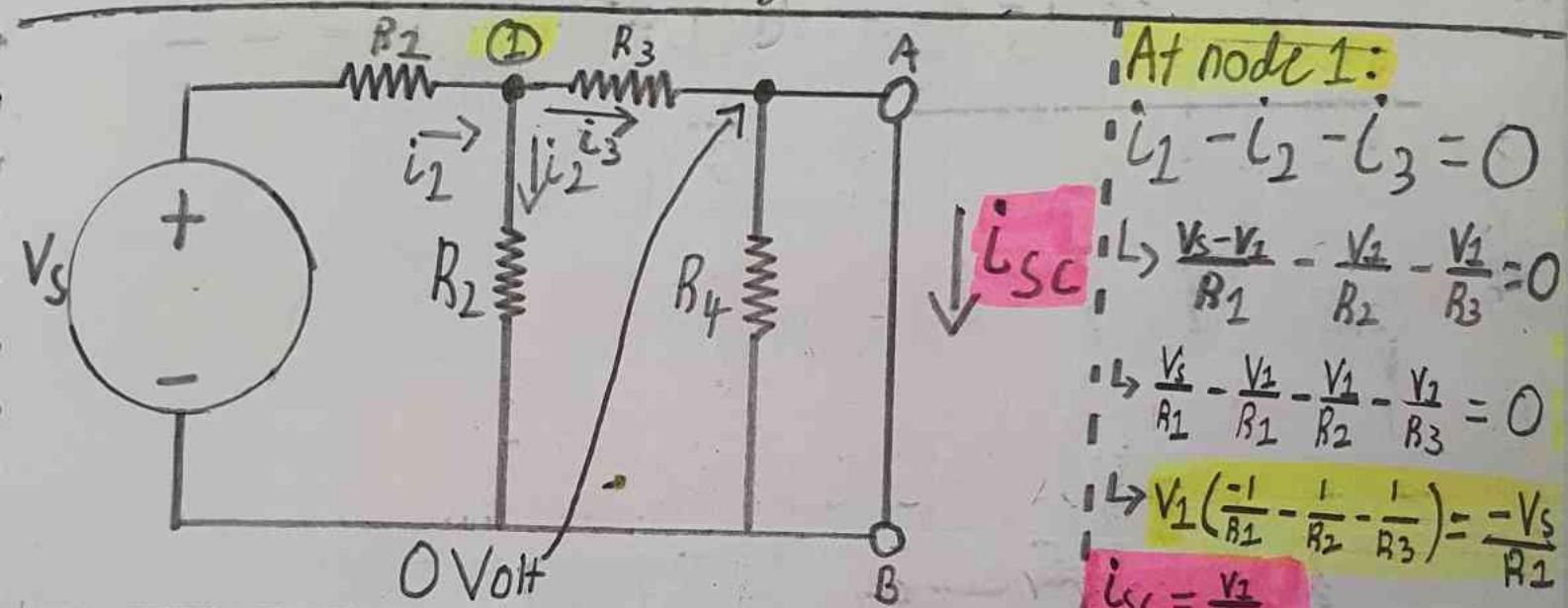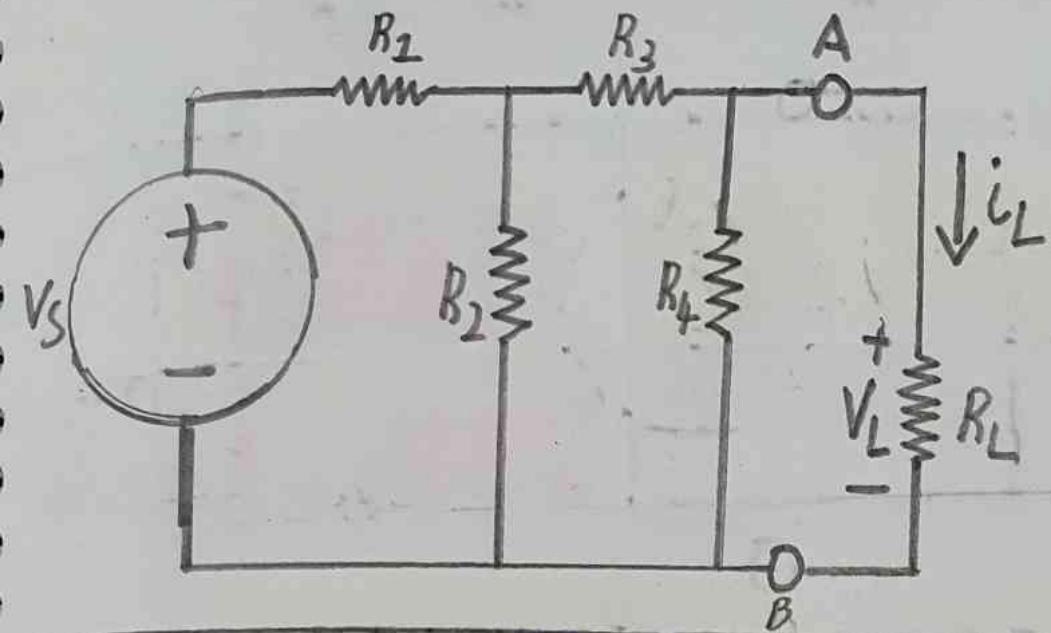

Example - Norton's Theorem

Refer to last Page:

$$V_1 \left(-\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_3} \right) = \frac{-V_s}{R_1}$$

$$i_{SC} = \frac{V_2}{R_3}$$

$$R_{Th} = (R_1 || R_2 + R_3) || R_4$$

$$i_{SC} = \frac{5.931V}{5\Omega} = 1.186A$$

$$V_1 \left(\frac{1}{2\Omega} - \frac{1}{7\Omega} - \frac{1}{5\Omega} \right) = \frac{-10V}{2\Omega} \rightarrow V_1 (-0.843) = -5$$

$$\therefore V_1 = 5.931V$$

$$R_{Th} = \left(\frac{1}{2\Omega} + \frac{1}{7\Omega} \right)^{-1} + 5\Omega = 6.556\Omega$$


$$\therefore \left(\frac{1}{6.556\Omega} + \frac{1}{8\Omega} \right)^{-1} = 3.603\Omega = R_{Th}$$

$$i_L = \frac{R_{Th} i_{SC}}{R_{Th} + R_L} = \frac{3.603\Omega (1.186A)}{3.603\Omega + 10\Omega} = 0.314A$$


$$V_L = (i_L)(R_L)$$

$$V_L = (0.314A)(10\Omega)$$

$$V_L = 3.14V$$

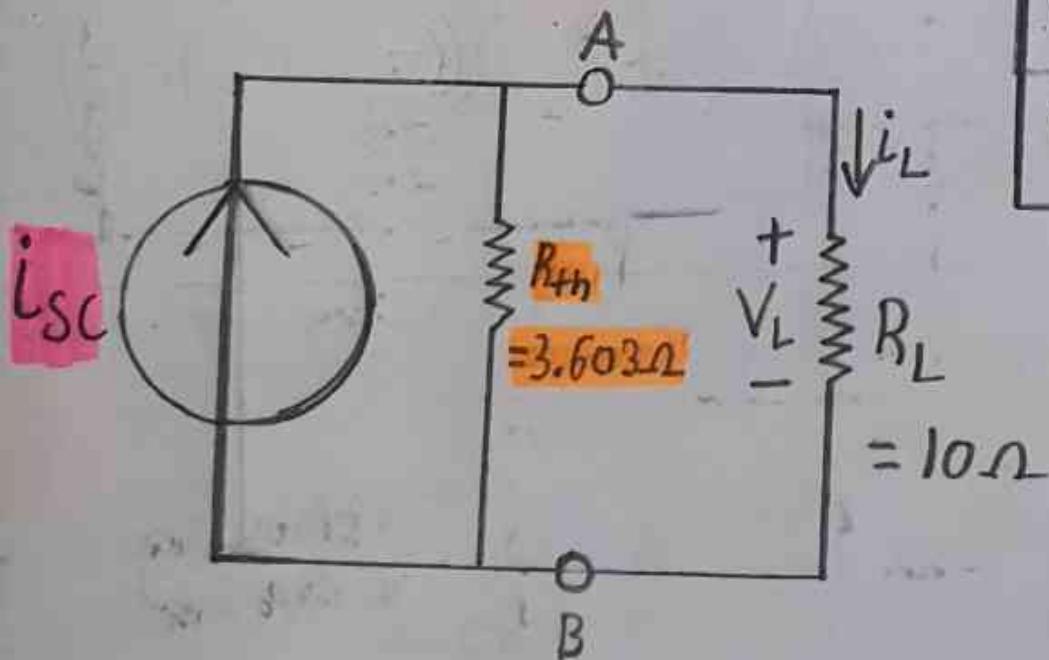

Definition of capacitor

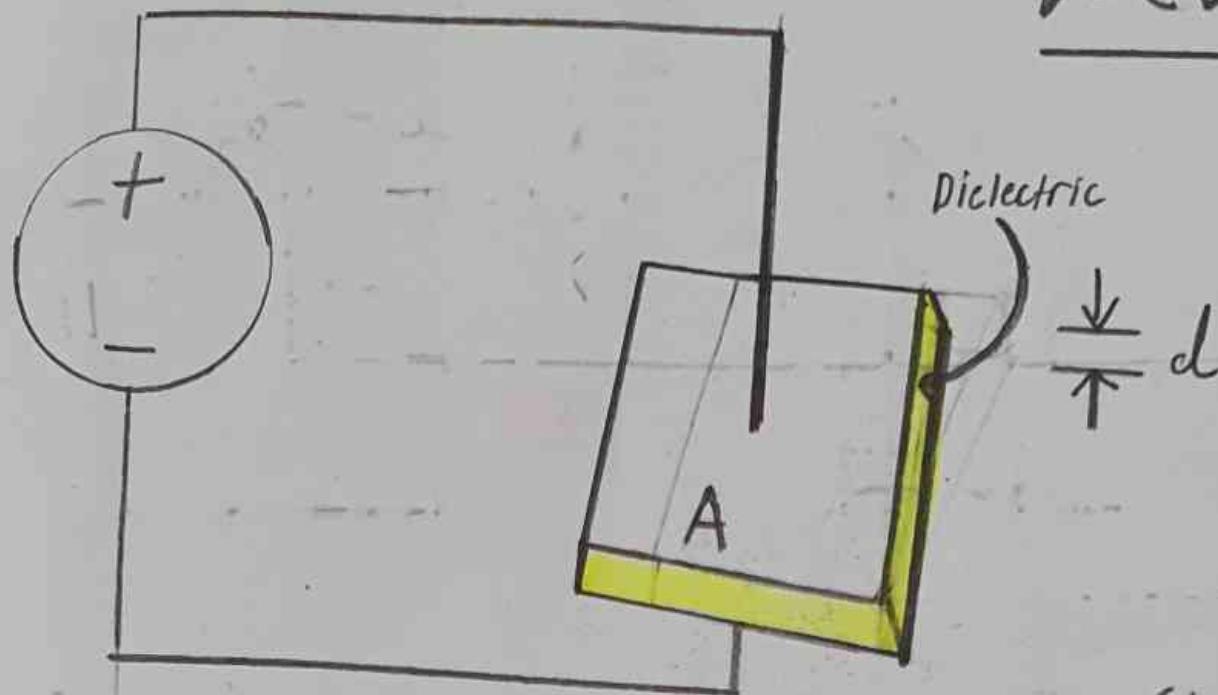

$$q = CV$$

$W_C(t) = \frac{1}{2} C V^2(t) J$

Energy stored
in a capacitor

Charge in a
capacitor

$$C = \frac{\epsilon A}{d}$$

$$i = \frac{dq}{dt} = \frac{d(CV)}{dt}$$


$$i_C = C \frac{dv}{dt}$$

Current through a capacitor

$$V_C(t) = V_C(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

Voltage Across
a capacitor

Series Capacitors

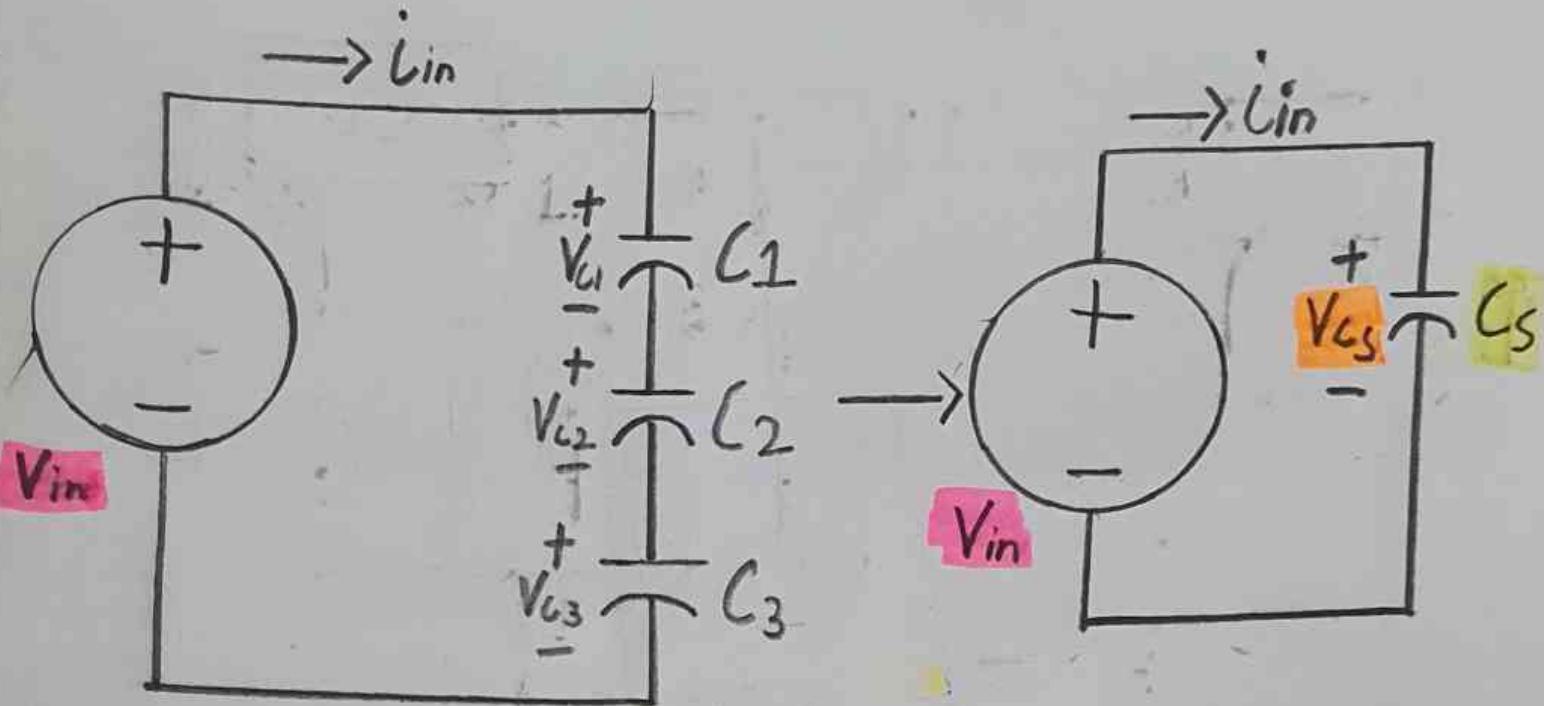

$$V_C = \frac{1}{C} \int_{t_0}^t i_C(t) dt + V_C(t_0)$$

$$V_{in} = V_{c1} + V_{c2} + V_{c3}$$


$$V_{in} = \left[\frac{1}{C_1} \int_{t_0}^t i_{in} dt + V_{c1}(t_0) \right] + \left[\frac{1}{C_2} \int_{t_0}^t i_{in} dt + V_{c2}(t_0) \right] \\ + \left[\frac{1}{C_3} \int_{t_0}^t i_{in} dt + V_{c3}(t_0) \right]$$

$$= \left[\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right] \int_{t_0}^t i_{in} dt + V_{c1}(t_0) + V_{c2}(t_0) + V_{c3}(t_0)$$

$$V_{cs} = \frac{1}{C_s} \int_{t_0}^t i_{in} dt + V_{cs}(t_0)$$

$$\hookrightarrow C_s = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1} \rightarrow \frac{1}{C_s} = \sum_{i=1}^3 \frac{1}{C_i}$$

Parallel Capacitors

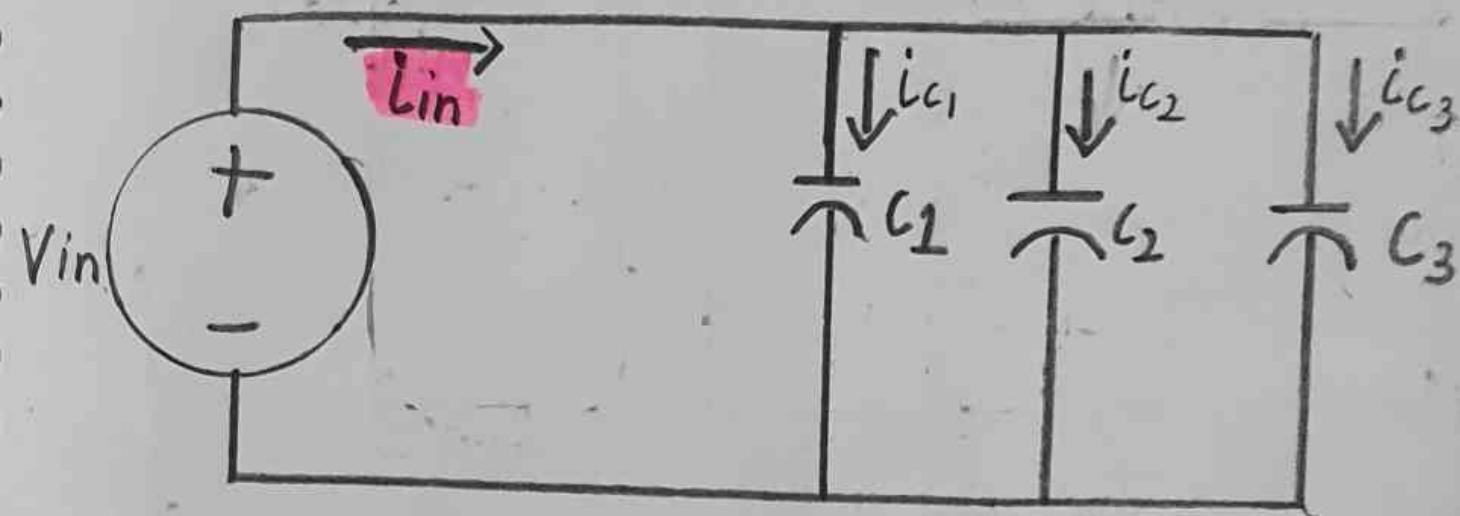

$$i_{in} = C_p \frac{dV_{in}}{dt}$$

For parallel capacitors:


$$i_{in} = i_{c1} + i_{c2} + i_{c3}$$

$$\Rightarrow C_1 \frac{dV_{in}}{dt} + C_2 \frac{dV_{in}}{dt} + C_3 \frac{dV_{in}}{dt}$$

$$i_{in} = (C_1 + C_2 + C_3) \frac{dV_{in}}{dt}$$

$$C_p = C_1 + C_2 + C_3 \rightarrow C_p = \sum_{n=1}^N C_n$$

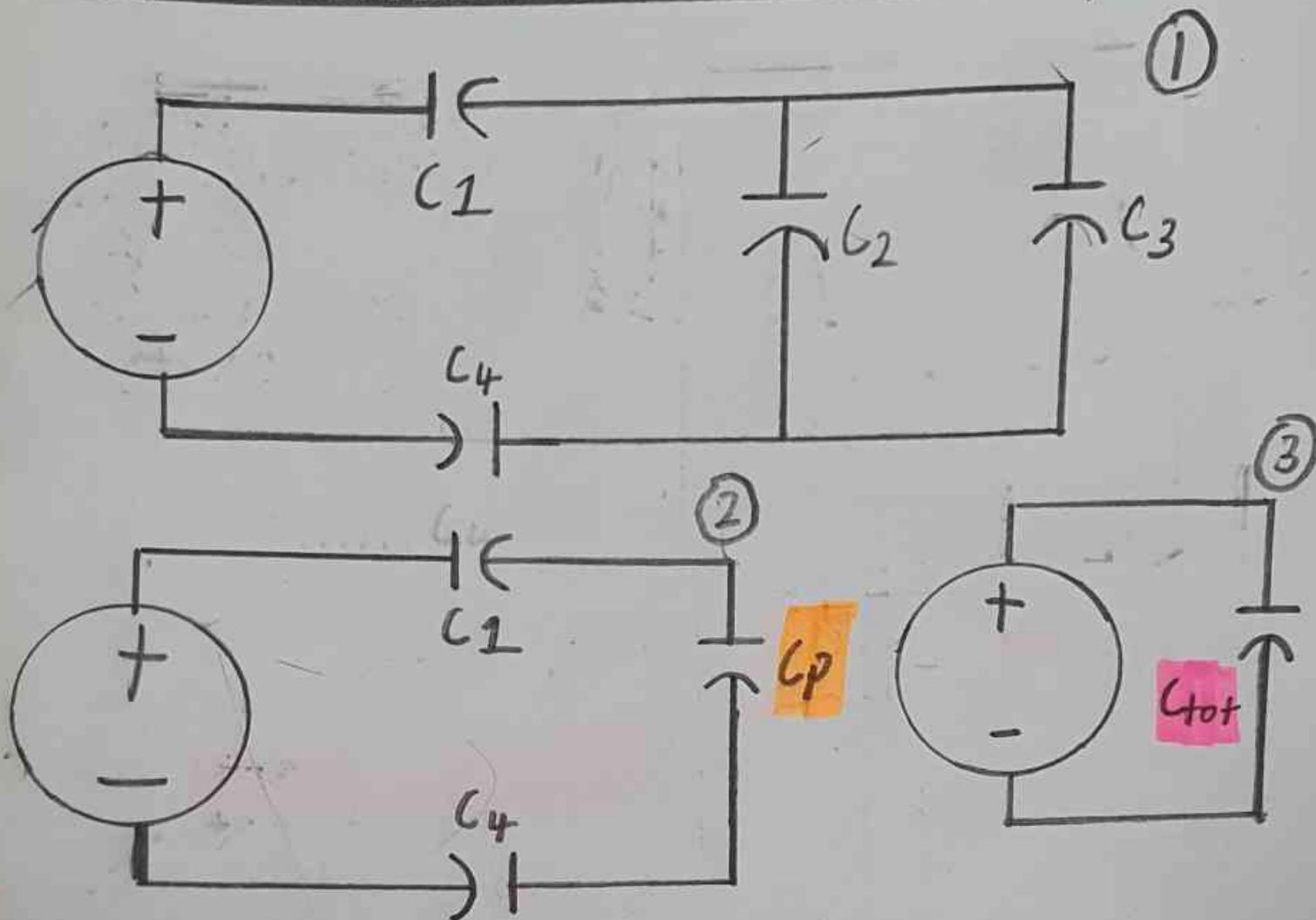Series/Parallel combination of capacitors




$$C_P = \sum_{i=1}^n C_i, \frac{1}{C_S} = \sum_{i=1}^n \frac{1}{C_i}$$

$$C_P = C_2 + C_3$$


$$\Rightarrow C_{tot} = \left[\frac{1}{C_1} + \frac{1}{(C_2+C_3)} + \frac{1}{C_4} \right]^{-1}$$

Definition of Inductors

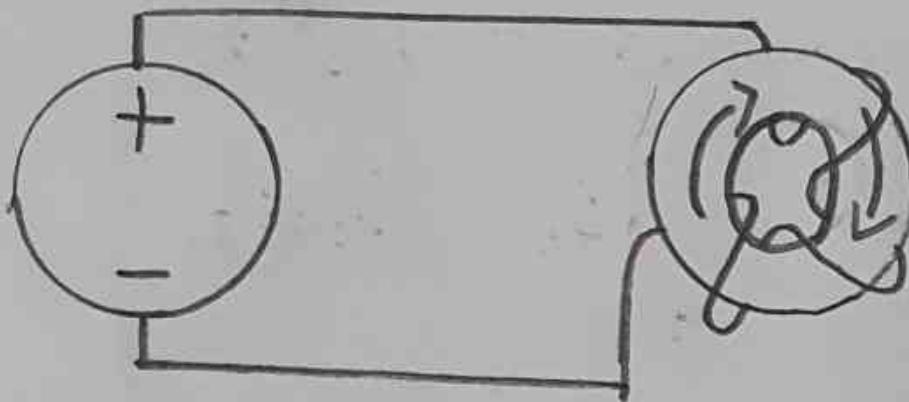

$$V_L = L \frac{di}{dt}$$

Voltage across an Inductor

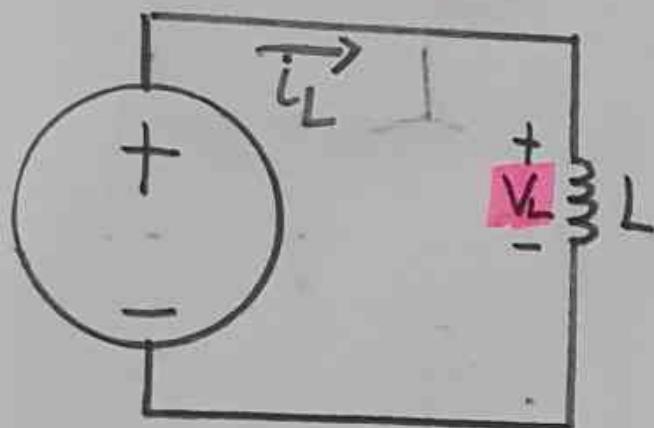

Current through an Inductor

$$V_L = L \frac{di}{dt} \rightarrow di = \frac{V_L}{L} dt \rightarrow i(t) = \int_{-\infty}^t \frac{V_L}{L} dt$$

$$\hookrightarrow i(t) = \frac{1}{L} \int_{-\infty}^t V_L dt \rightarrow i(t) = i(t_0) + \int_{t_0}^t V_L(x) dx$$


$$V_L = L \frac{di}{dt}, P(t) = V(t) i(t)$$

$$P_L(t) = L \frac{d}{dt} i, W_L(t) = \int_{-\infty}^t L \frac{d}{dx} i(x) i(x) dx$$

$$\hookrightarrow W_L(t) = L \int_{-\infty}^t i(x) di(x)$$

$$= \frac{1}{2} L i^2(t) \quad \rightarrow \text{Energy stored in a Inductor}$$

Series Inductors

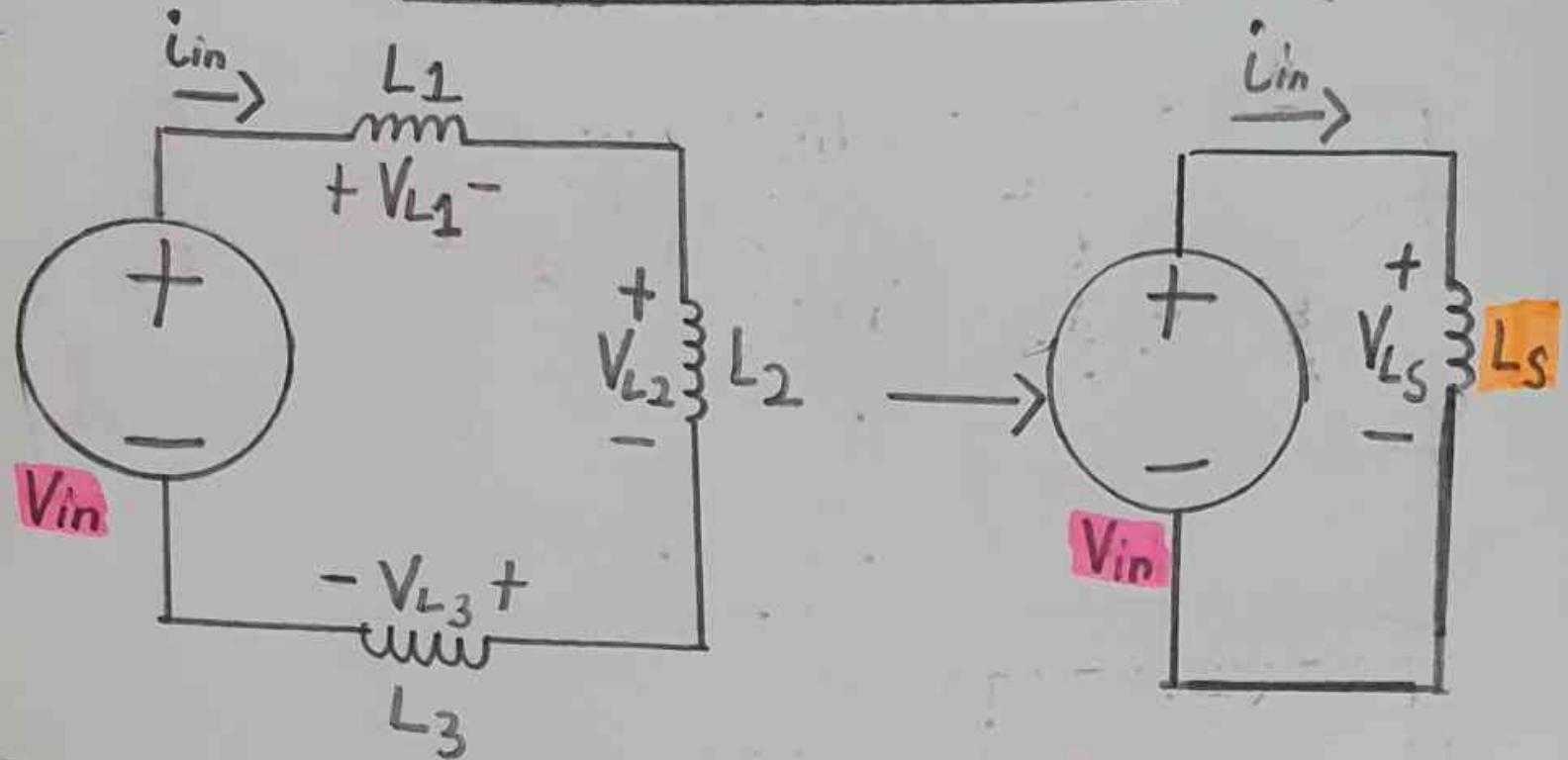

$$V_L = L \frac{di}{dt}$$

$$V_{in} = V_{L_1} + V_{L_2} + V_{L_3}$$



$$= L_1 \frac{di_{in}}{dt} + L_2 \frac{di_{in}}{dt} + L_3 \frac{di_{in}}{dt}$$

$$= (L_1 + L_2 + L_3) \frac{di_{in}}{dt}$$

$$V_{in} = L_s \frac{di_{in}}{dt}$$

$$L_s = L_1 + L_2 + L_3 \rightarrow L_s = \sum_{i=1}^n L_i$$

Parallel Inductors

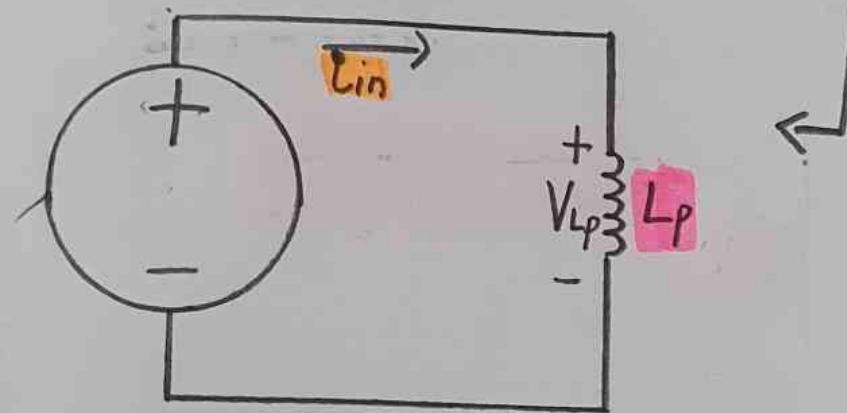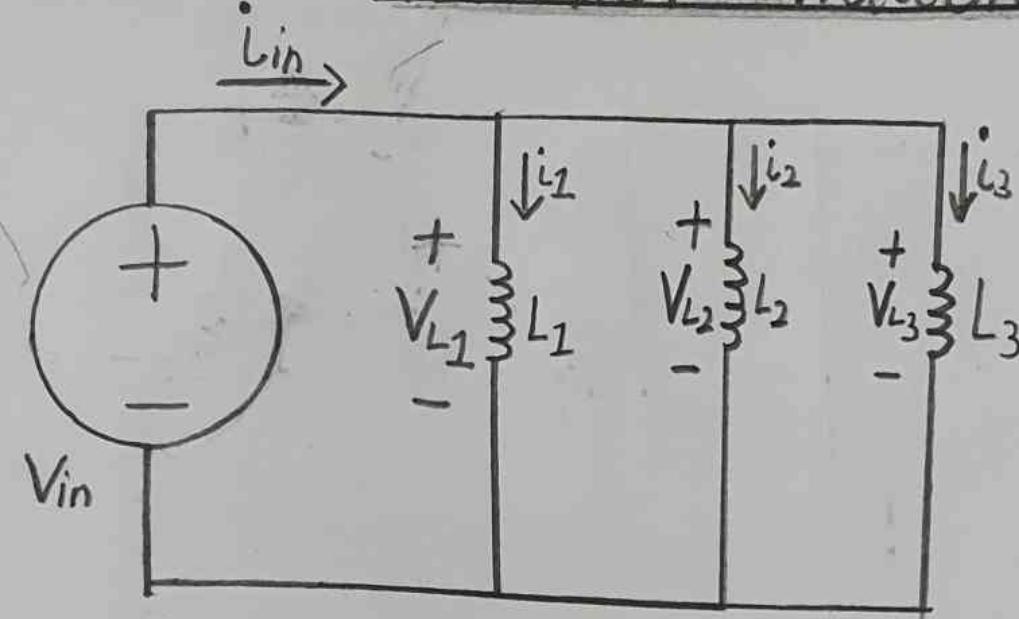

$$\dot{i}_L = \dot{i}_L(t_0) + \frac{1}{L} \int_{t_0}^t V_L(x) dx$$

$$i_{in} = i_1 + i_2 + i_3$$


$$\hookrightarrow \left[i_1(t_0) + \frac{1}{L_1} \int_{t_0}^t V_{L1}(x) dx \right] + \left[i_2(t_0) + \frac{1}{L_2} \int_{t_0}^t V_{L2}(x) dx \right] + \left[i_3(t_0) + \frac{1}{L_3} \int_{t_0}^t V_{L3}(x) dx \right], i_{in}(t_0) = i_1(t_0) + i_2(t_0) + i_3(t_0)$$

$$= i_{in}(t_0) + \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right) \int_{t_0}^t V_{in}(x) dx \quad \left. \right\} L_p = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right)^{-1}$$



$$\dot{i}_{in}(t) = i_{in}(t_0) + \frac{1}{L_p} \int_{t_0}^t V_{in}(x) dx$$

$$\frac{1}{L_p} = \sum_{i=1}^n \frac{1}{L_i}$$

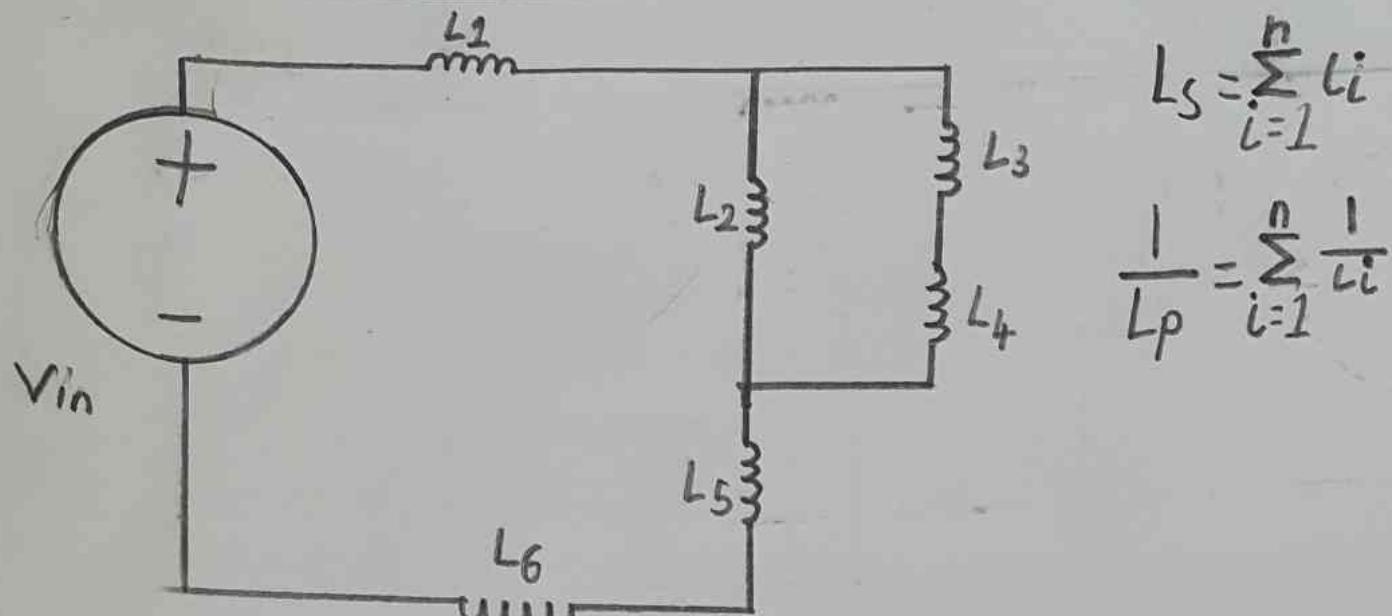Series / Parallel combination of Inductors



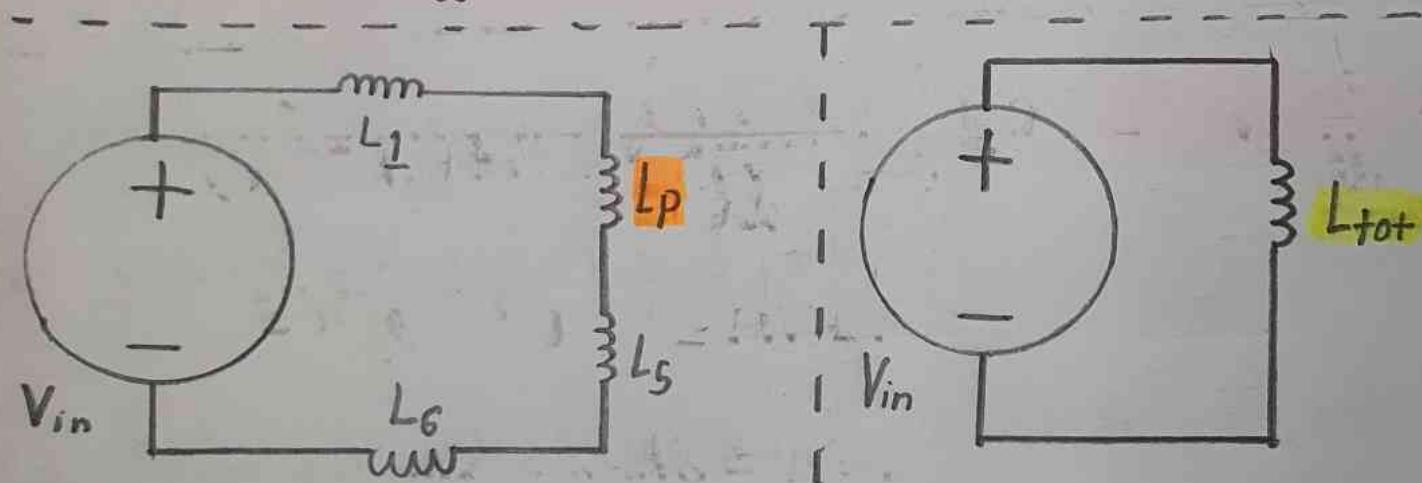
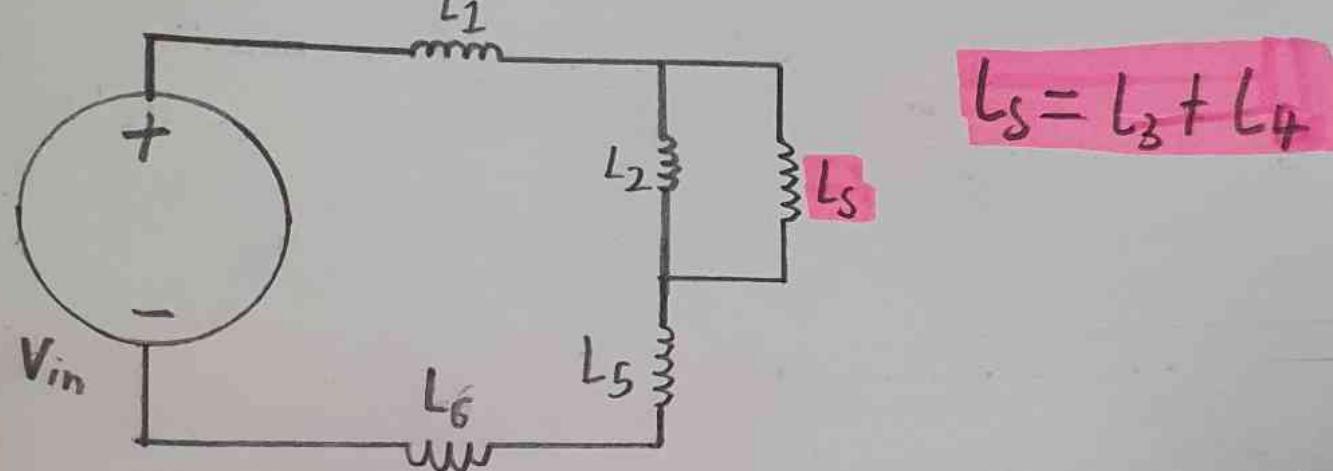
$$\frac{1}{L_p} = \sum_{i=1}^n \frac{1}{L_i}$$



$$L_p = \left(\frac{1}{L_2} + \frac{1}{L_3} \right)^{-1}$$

$$L_{tot} = L_1 + L_p + L_5 + L_6$$

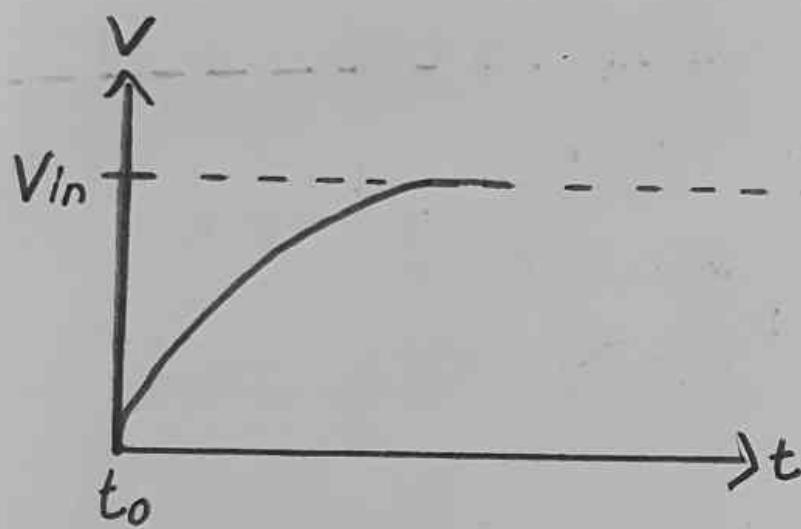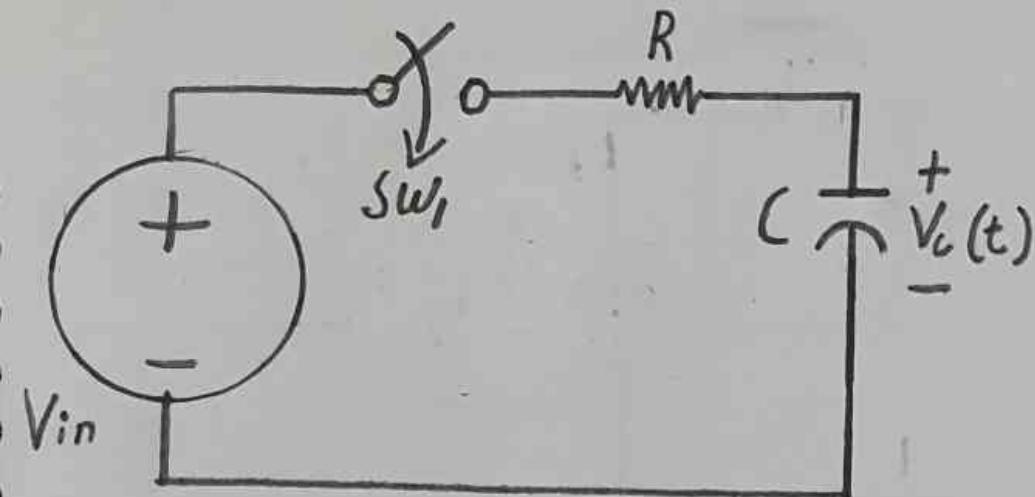First-Order Transient Circuits - Introduction





$$i_C = C \frac{dV}{dt}, \quad V_L = L \frac{di}{dt} \quad | \quad \frac{dx(t)}{dt} + \alpha x(t) = f(t)$$

$$| \quad x(t) = k_1 + k_2 e^{-t/\tau}$$

| k_1 = Steady state

| τ = time constant

Series RC Circuits

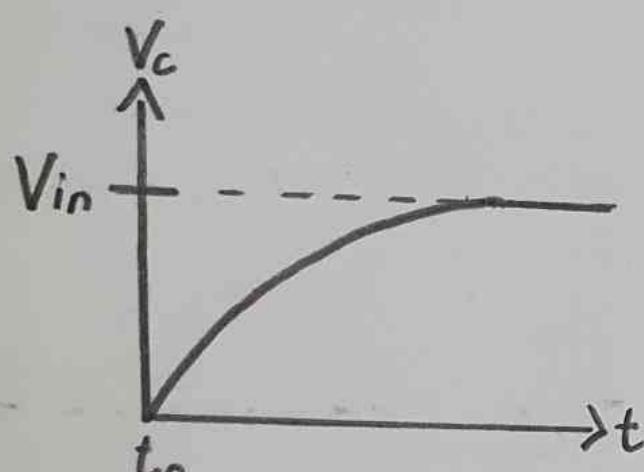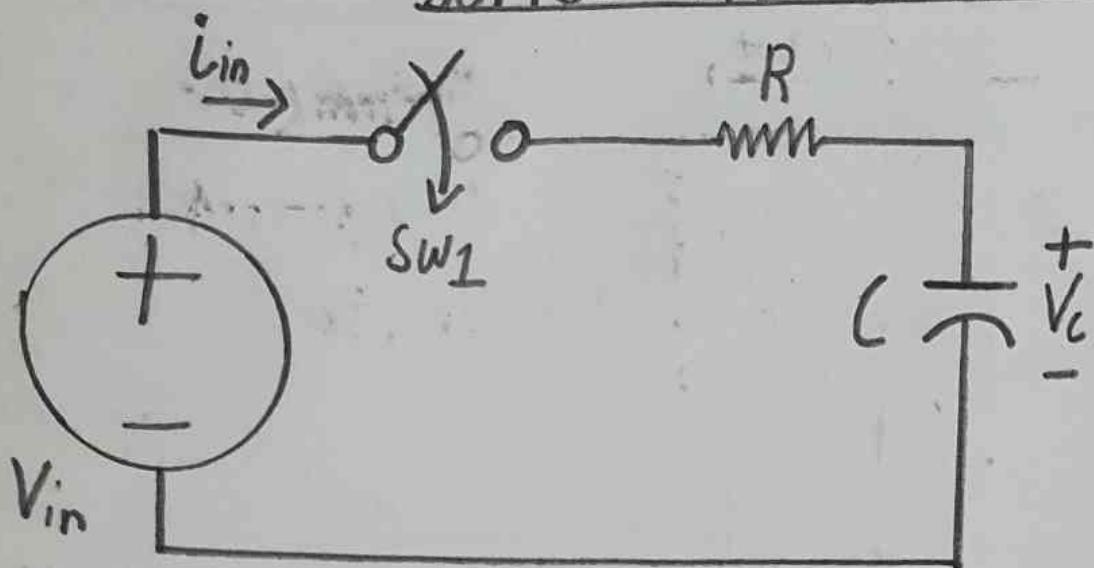

$$\frac{dx(t)}{dt} + ax(t) = f(t)$$

$$x(t) = k_1 + k_2 e^{-t/\tau}$$

$$V_c = k_1 + k_2 e^{-t/\tau}$$

$$i_c = C \frac{dV}{dt}$$

$$\hookrightarrow \frac{V_{in}(t) - V_c(t)}{R} = C \frac{dV_c(t)}{dt} \rightarrow \frac{dV_c(t)}{dt} + \frac{V_c(t)}{RC} = \frac{V_{in}(t)}{RC}$$

$$\hookrightarrow \frac{d}{dt} (k_1 + k_2 e^{-t/\tau}) + \frac{k_1 + k_2 e^{-t/\tau}}{RC} = \frac{V_{in}(t)}{RC}$$




$$\hookrightarrow -\frac{k_2 e^{-t/\tau}}{\tau} + \frac{k_1}{RC} = \frac{V_{in}(t)}{RC} \rightarrow \frac{k_1}{RC} = \frac{V_{in}}{RC} \rightarrow \boxed{k_1 = V_{in}}$$

$$\frac{k_2 e^{-t/\tau}}{\tau} = \frac{k_2 e^{-t/\tau}}{RC} \rightarrow \boxed{\tau = RC}$$

$$V_c(t_0) = 0 = k_1 + k_2 e^{-t_0/\tau} = 1 \rightarrow 0 = V_{in} + k_2 \rightarrow \boxed{k_2 = -V_{in}}$$

$$\hookrightarrow V_c(t) = V_{in} - V_{in} e^{-t/RC}$$

Ideal Rectifiers

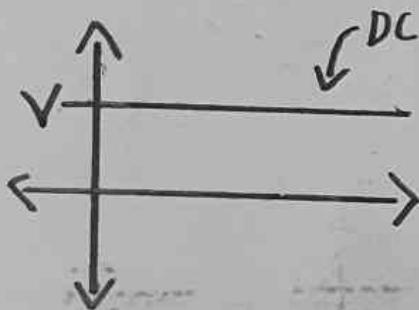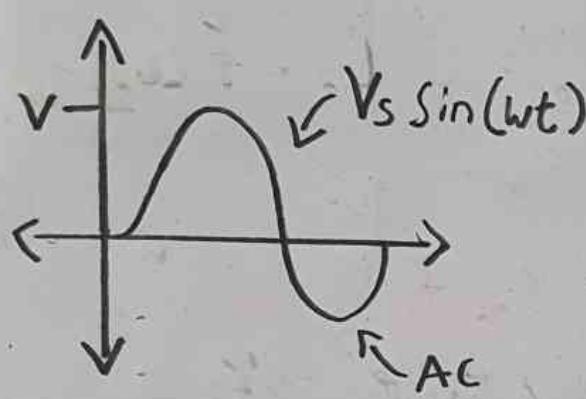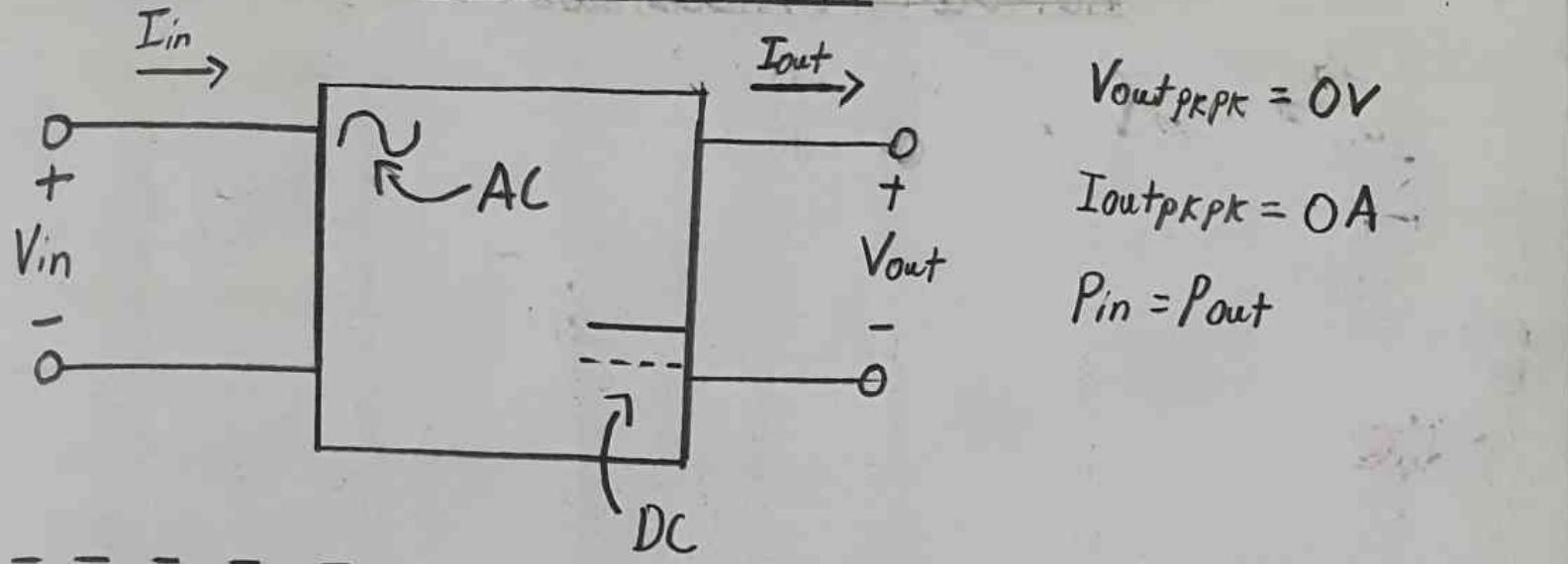

Q1. What is the Voltage Ripple at the Output of an Ideal Rectifier?



Answer = Zero because the output voltage of an ideal rectifier is a perfect DC voltage. In technical terms, the voltage only has a 0Hz component.

Q2. What is the efficiency of an ideal rectifier?


Answer = 100% because ideally, there are no losses in an ideal rectifier, which means that the input power and output power are equal, hence the 100% efficiency.

Review of the Diode

Circuit Symbol:

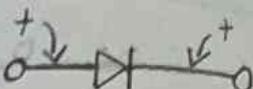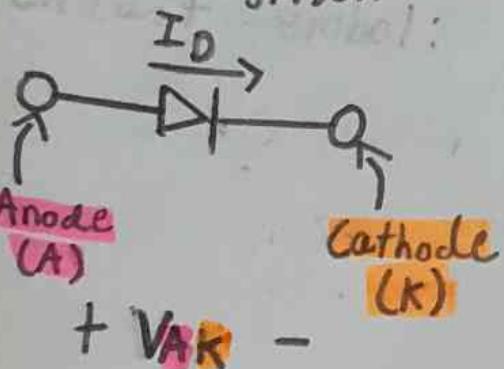


Reverse Bias

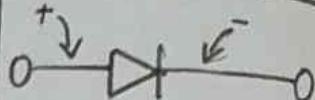

Forward Bias



Reverse Bias

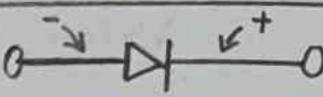

Reverse Bias

If Voltage from A to K is positive:


Short circuit



Forward Bias

If voltage from A to K is negative:

Open circuit

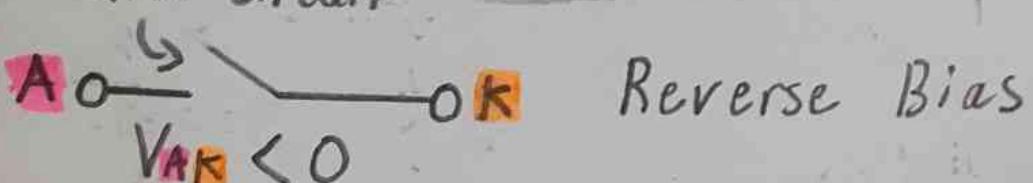


Reverse Bias

Q1. When a Diode is OFF, the anode - cathode voltage (V_{AK}) is:

Answer: Either zero or negative because for a diode to be ON, it needs to be forward biased, (V_{AK} needs to be positive)

Half-Wave Rectifiers with Resistive Load

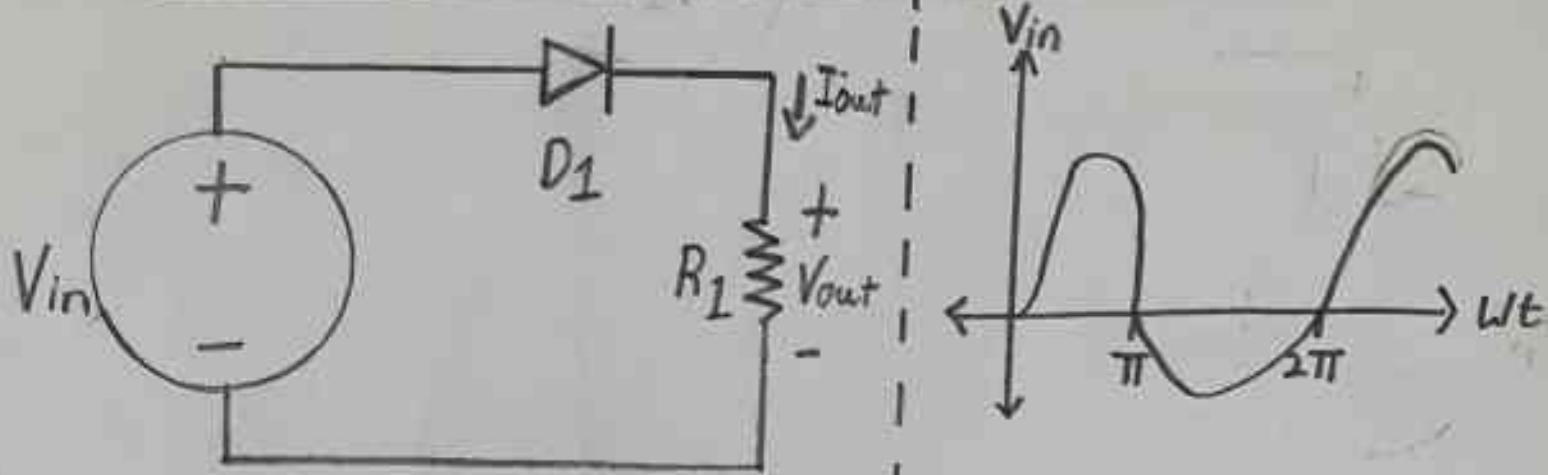

$$V = IR$$

$$\therefore I = V/R$$



$$V_{in} = 120V_{rms} \text{ at } 60 \text{ Hz}$$

$$V_{in} = 170 \sin(377t) \text{ V}$$

$$120V_{rms}\sqrt{2} = 170V, 2\pi f = 2\pi(60) = 377$$

π = Half cycle

2π = Full cycle

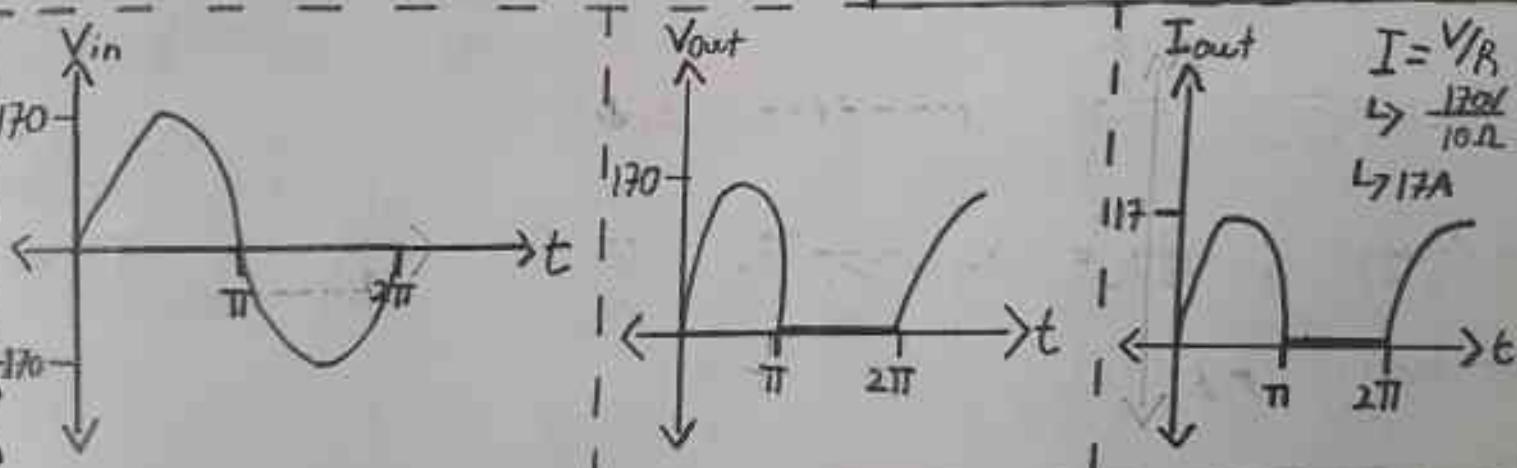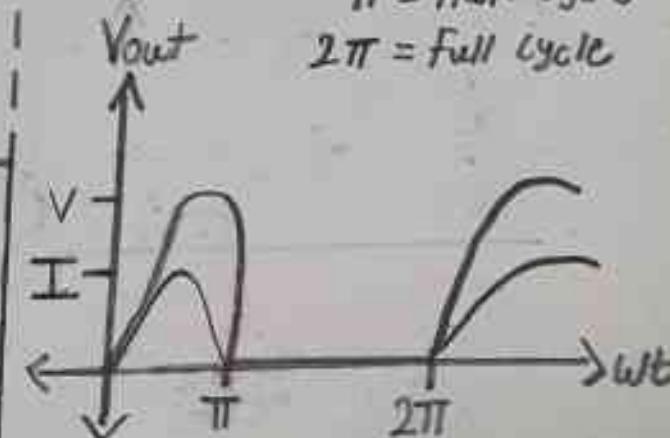

Average of output voltage

$$\langle V_{out} \rangle = \frac{1}{T} \int_0^T V_{in} dt \rightarrow \frac{1}{16.6} \int_0^{8.3} 170 \sin(377t) dt$$


$$T = \frac{1}{60} = 16.6 \text{ ms}$$

$$\langle V_{out} \rangle = \frac{\text{Voltage Peak}}{\pi}$$

$$= 0.319(170) = 54.23 \text{ V}$$

$$\therefore \frac{170V}{\pi} = 54.23V$$

Half-Wave Rectifiers With Inductive Load

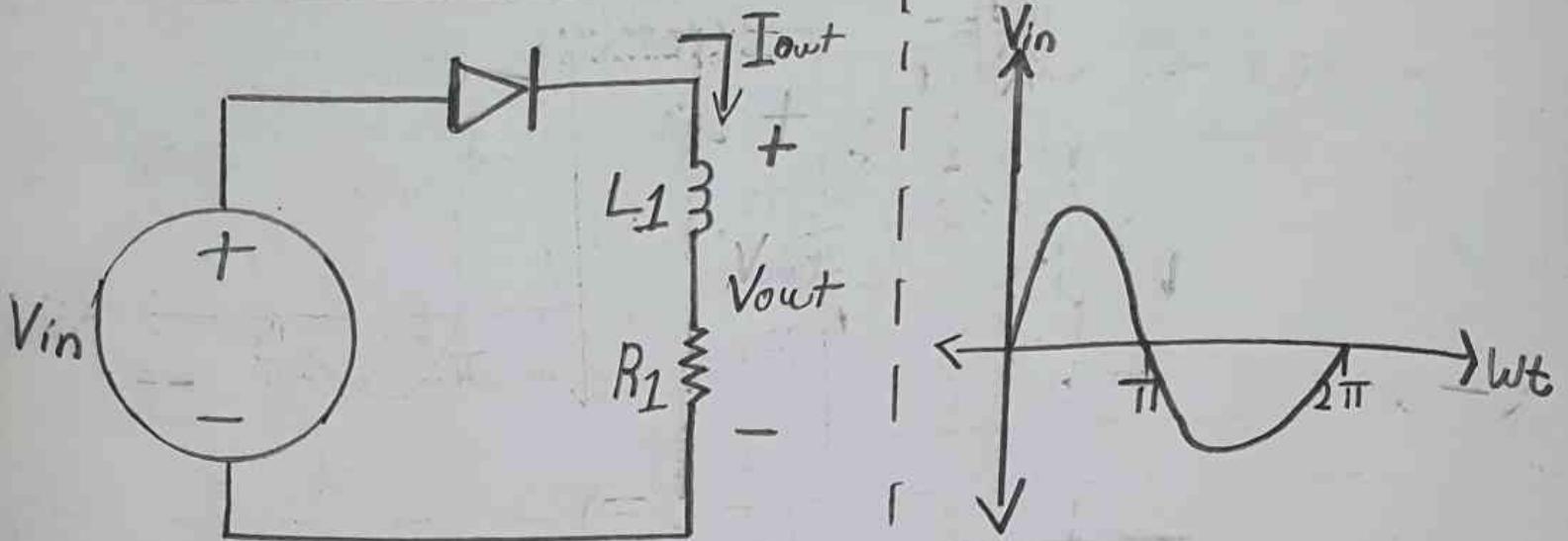

$$V_L = L \frac{di}{dt} \rightarrow \frac{di}{dt} = \frac{V_L}{L}$$

$$Z = \sqrt{R^2 + (wt)^2}$$

$$\phi = \tan^{-1}\left(\frac{wt}{R}\right)$$

$$V_{in} = 170 \sin(377t) V, 60 \text{ Hz}$$

$$L_1 = 20 \text{ mH}, R_1 = 10 \Omega$$

Millaheneries

$$X = \omega L = 377 (20 \text{ mH} \times 10^{-3} \Omega) = 7.54 \Omega$$


$$Z = \sqrt{10^2 + 7.54^2} = 12.52 \Omega$$

$$I_{out,PK} = \frac{170}{12.52} = 13.58 \text{ A}$$

$$\phi = \tan^{-1}\left(\frac{X}{10 \Omega}\right) = 37.02^\circ$$


$$L > 16.6 \text{ ms} \left(\frac{37.02^\circ}{360^\circ}\right) = 1.7 \text{ ms}$$

Note: V and I have same peak.

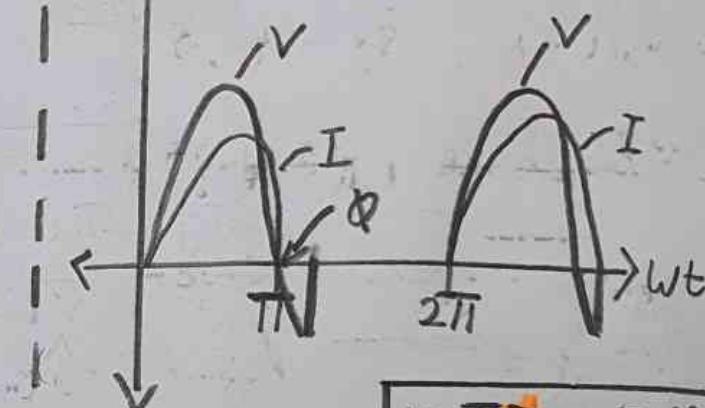

$$V = IZ \rightarrow I = \frac{V}{Z}$$

$$V = IR \rightarrow I = \frac{V}{R}$$

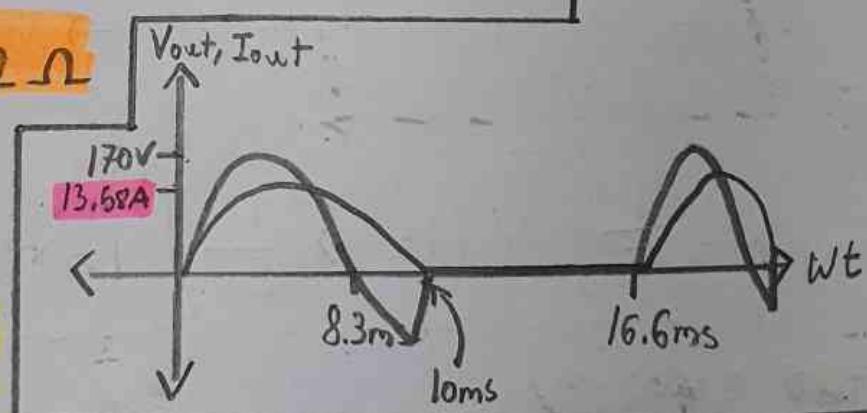


$$\langle V_{out} \rangle = \frac{1}{16.6 \times 10^{-3}} \int_0^{10 \times 10^{-3}} 170 \sin(377t) dt = 0.289 (170)$$

$$= 49.13 \text{ V}$$

$$L > 54.23 \text{ V}$$

The freewheeling Diode

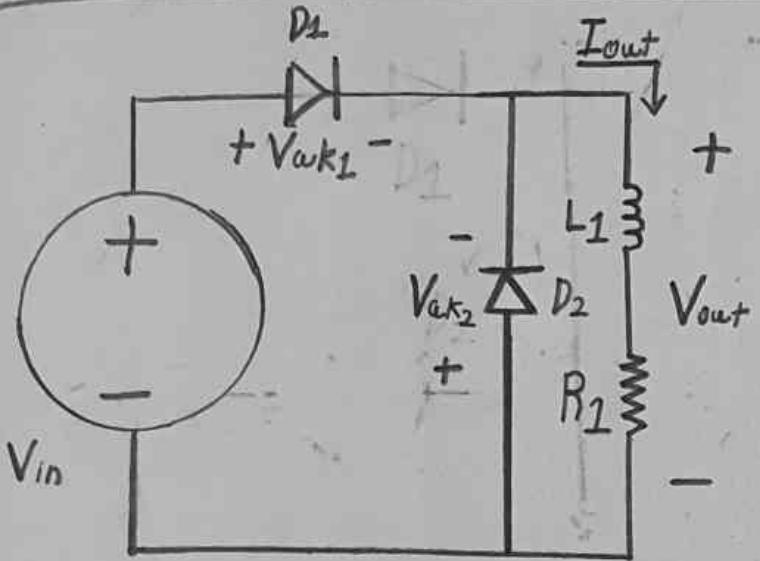

State 1:

D_1 is ON, D_2 is OFF

State 2:

D_1 is OFF, D_2 is ON

$$V_{in} = 170 \sin(377t) \text{ V}, 60 \text{ Hz}$$



$$L_1 = 20 \text{ mH}, R_1 = 10 \Omega$$

$$Z = 12.52 \Omega, Z = \sqrt{R^2 + (wt)^2}$$

$$I_{out,PK} = \frac{170}{12.52} = 13.58 \text{ A}$$


$$\tau = L/R = \frac{20 \times 10^{-3}}{10} = 0.002$$
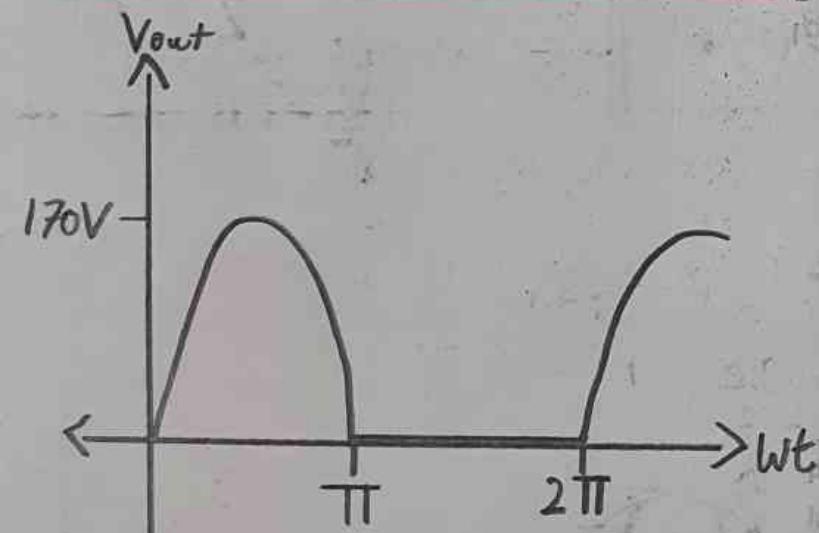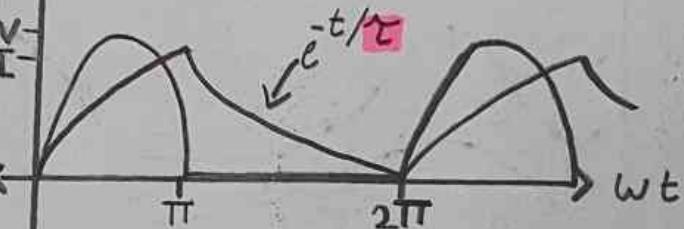
$$V_{out}, I_{out} \quad I = \frac{V}{Z} \quad \tau = \frac{L}{R}$$




$$\langle V_{out} \rangle = 49.13 \text{ V}$$

$$\hookrightarrow 54.23 \text{ V}$$

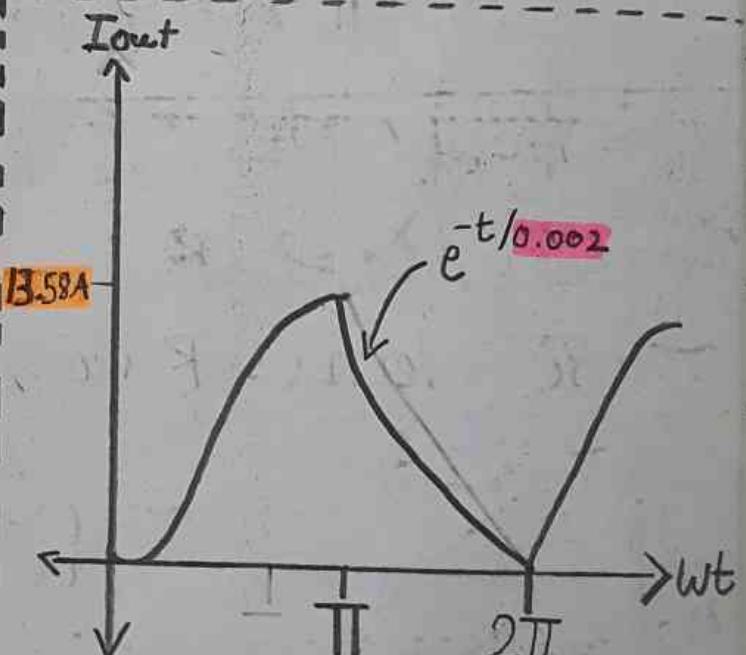


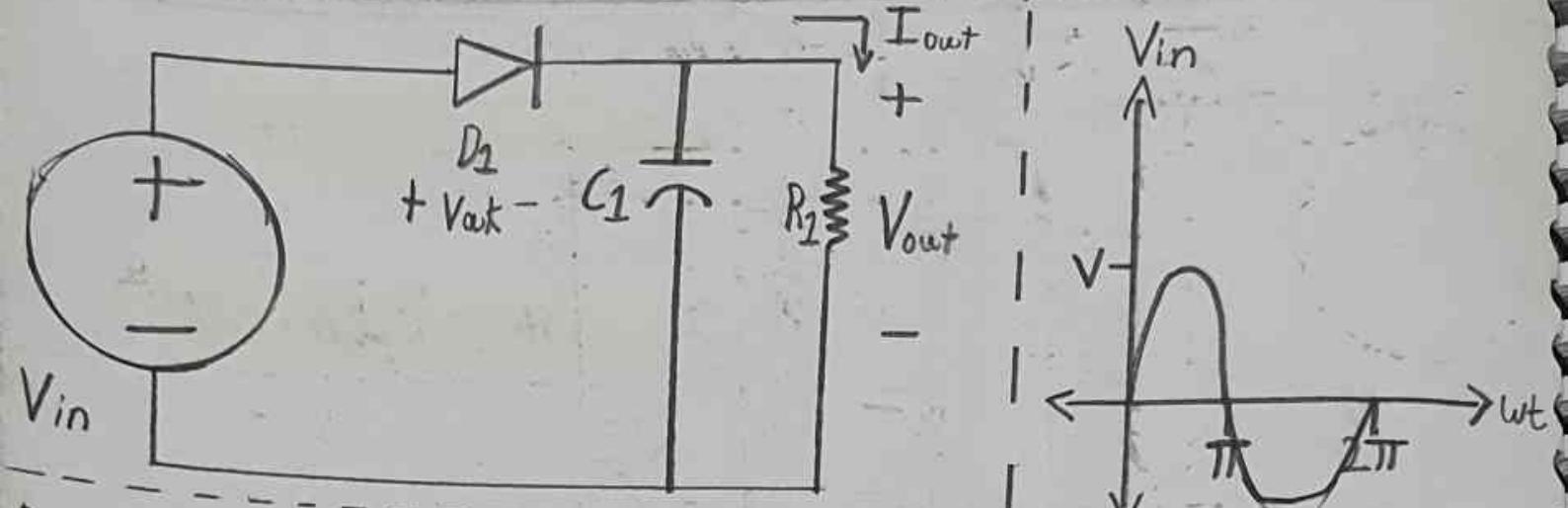Half-Wave Rectifiers with Capacitive filters



$i_C = C \frac{dV}{dt} \rightarrow \frac{dV}{dt} = \frac{i_C}{C}$

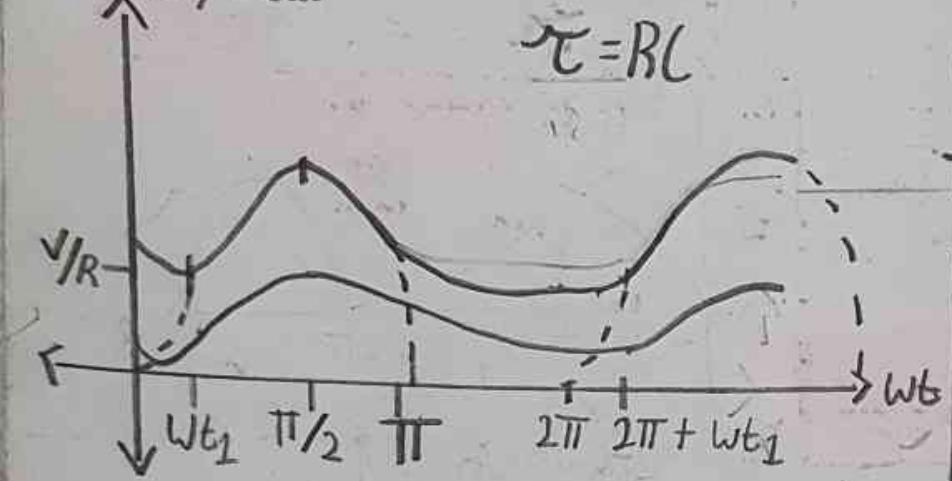From $\pi/2$ to $\pi/2 + wt_1$, D_1 is ON
 From $\pi/2 + wt_1$ to $2\pi + wt_1$, D_1 is OFF



$$\tau = RC$$

$$wt_1 \text{ to } \pi/2 = V_s \sin(wt)$$


$$\pi/2 \text{ to } 2\pi + wt_1 = e^{-t/\tau}$$

$$\begin{aligned} t &= 16.6 \text{ ms} \times 10^{-3} + t_1 \\ 170 \sin(377(16.6 \times 10^{-3} + t_1)) & \\ \Rightarrow 170e^{-(t - 4.15 \text{ ms})/0.02} & \end{aligned}$$

$$V_{in} = 170 \sin(377t) \text{ V, } 60 \text{ Hz}$$

$$R_1 = 10 \Omega, C_1 = 2 \text{ mF}$$
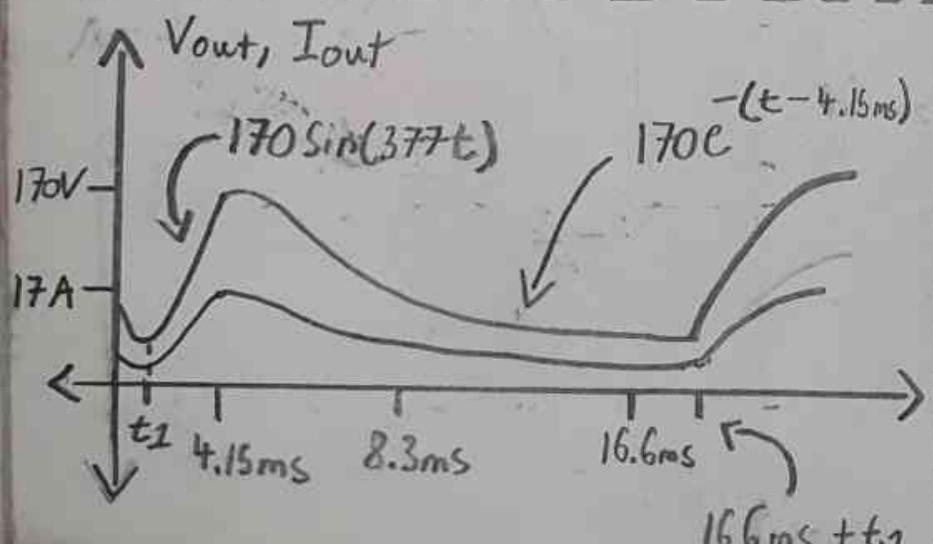
$$\tau = RC = 10 \Omega (2 \text{ mF} \times 10^{-3}) = 0.02$$



$$\Rightarrow t_1 = 1.45 \text{ ms}$$

$$= 0.74 \text{ V/h}$$

$$= 0.74 (170)$$

$$= 125.8 \text{ V}$$

Integral


Decaying exponential function

Sin Wave Integral

$$\int_{4.15 \times 10^{-3}}^{16.6 \times 10^{-3}} 170 \sin(377t) dt + 125.8$$

$$\int_{4.15 \times 10^{-3}}^{16.6 \times 10^{-3}} 170 e^{-(t - 4.15 \times 10^{-3})/0.02} dt$$

Full-Wave Rectifiers with Inductive Load

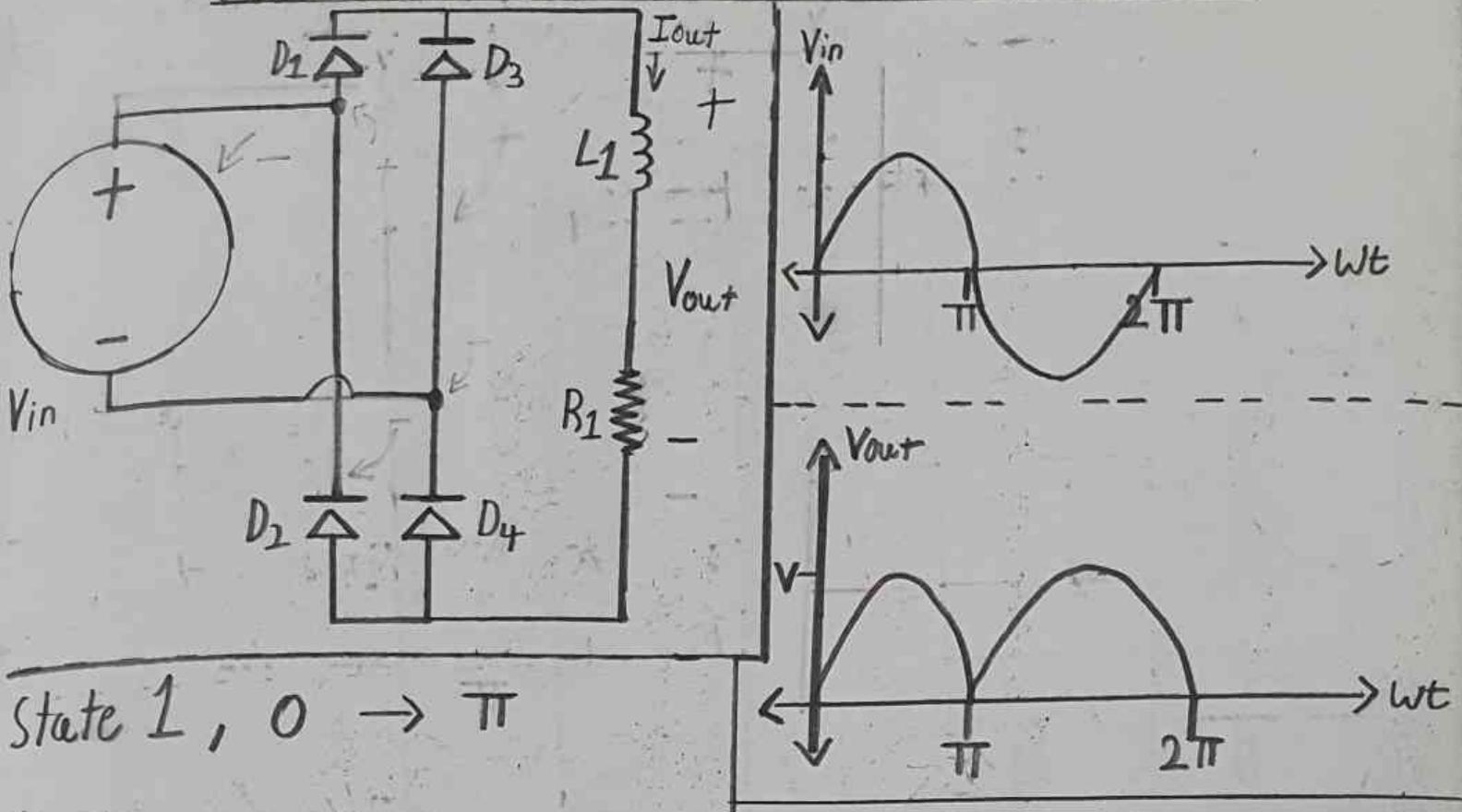

State 1, $0 \rightarrow \pi$

D_1/D_4 ON, D_2/D_3 OFF

State 2, $\pi \rightarrow 2\pi$

D_1/D_4 OFF, D_2/D_3 ON

$$V_{in} = 170 \sin(377t) \text{ V}$$

$$L_1 = 20 \text{ mH}, R_1 = 10 \Omega$$

$$V_L = L \frac{di}{dt}, V_{out} = V_L + I_{out} \times R$$

$$V_{out} = |170 \sin(377t)|$$


$$|170 \sin(377t)| = 0.02 \frac{di}{dt} + C(10)$$



$$\langle V_{out} \rangle = \frac{1}{16.6 \times 10^{-3}} \left[\int_{8.3 \times 10^{-3}}^{8.3 \times 10^{-3}} 170 \sin(377t) dt \right]$$

$$+ \int_{8.3 \times 10^{-3}}^{16.6 \times 10^{-3}} -170 \sin(377t) dt \Big] = 0.639 (170 \text{ V}) = 108.64 \text{ V}$$

$$\langle I_{out} \rangle = V_{out}/R = \frac{108.64 \text{ V}}{10 \Omega}$$

$$\therefore I_{out} = 10.86 \text{ A}$$

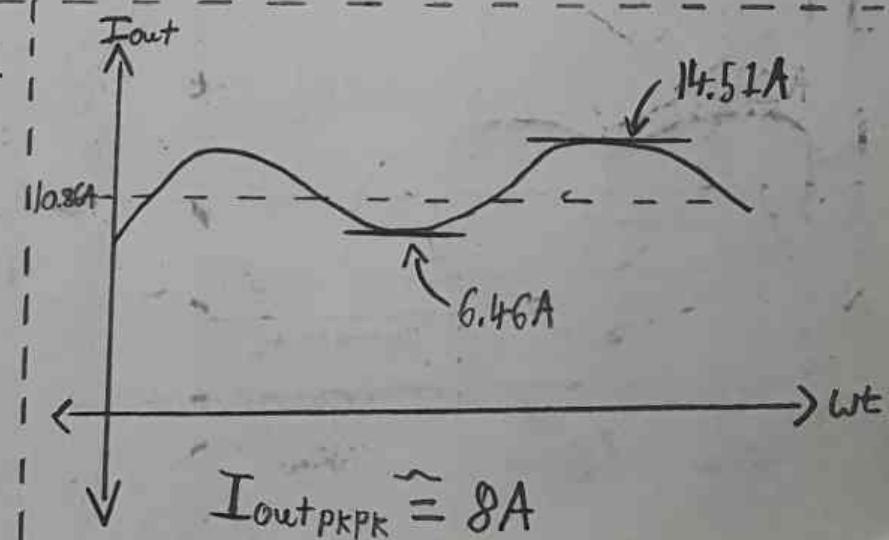

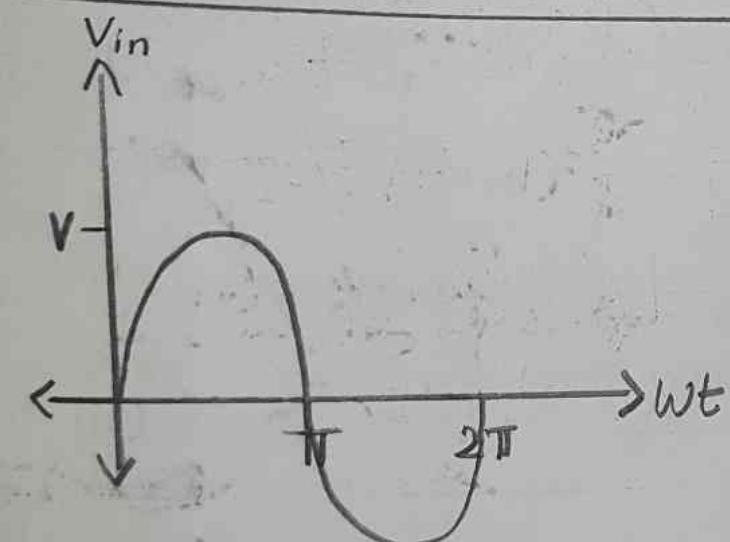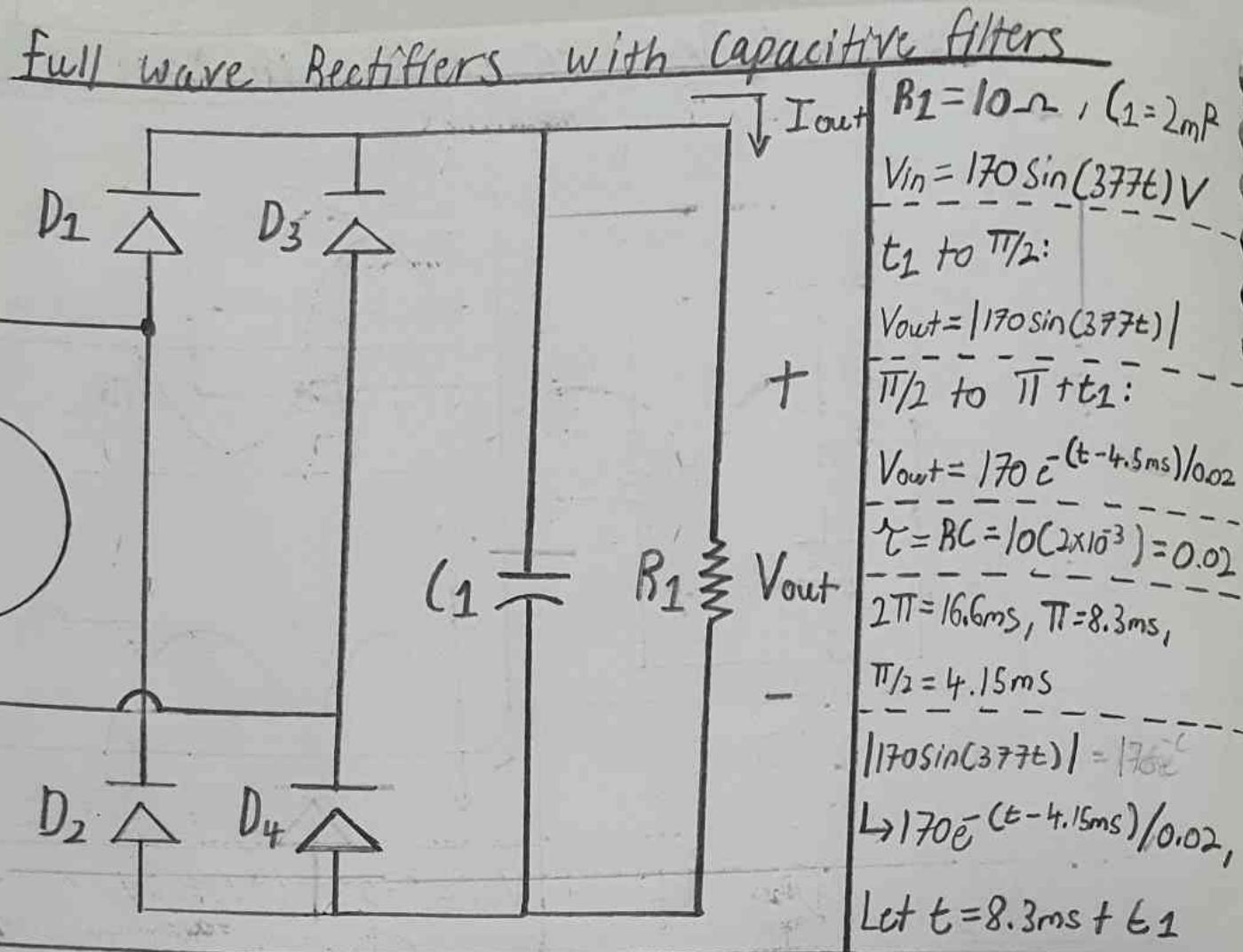


$$\Rightarrow t_1 = 2.2\text{ms}$$

$$\langle V_{out} \rangle = \frac{1}{16.6 \times 10^{-3}} \left[\int_{2.2\text{ms}}^{4.15\text{ms}} 170 \sin(377t) dt + \int_{4.15\text{ms}}^{10.5\text{ms}} 170 e^{-(t-4.15ms)/0.02} dt \right]$$



Sine wave Integral
 Decaying exponential function integral
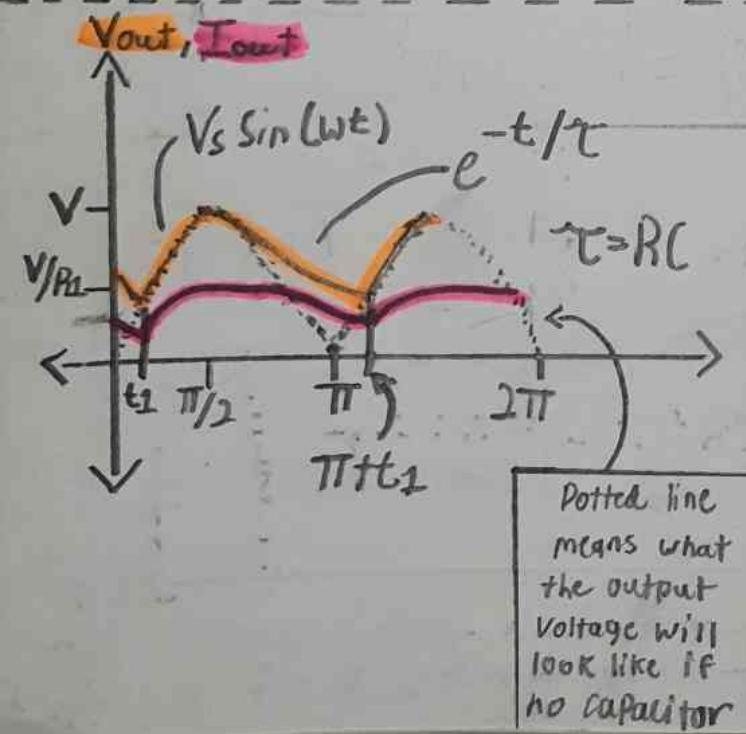
$$\langle V_{out} \rangle = 0.869(170)V = 147.35V$$



Half wave Rectifiers with Resistive Load ::

- 3 Phase Rectifiers

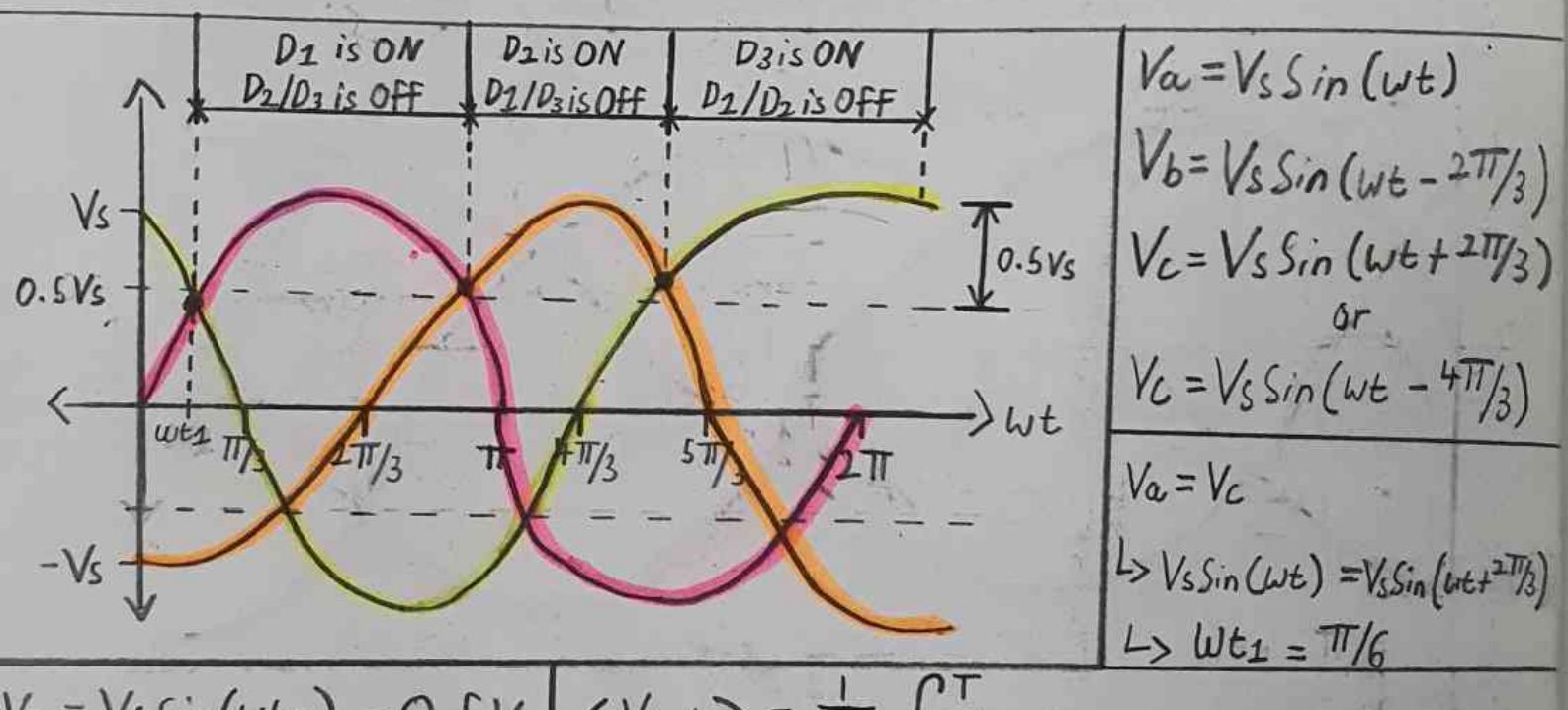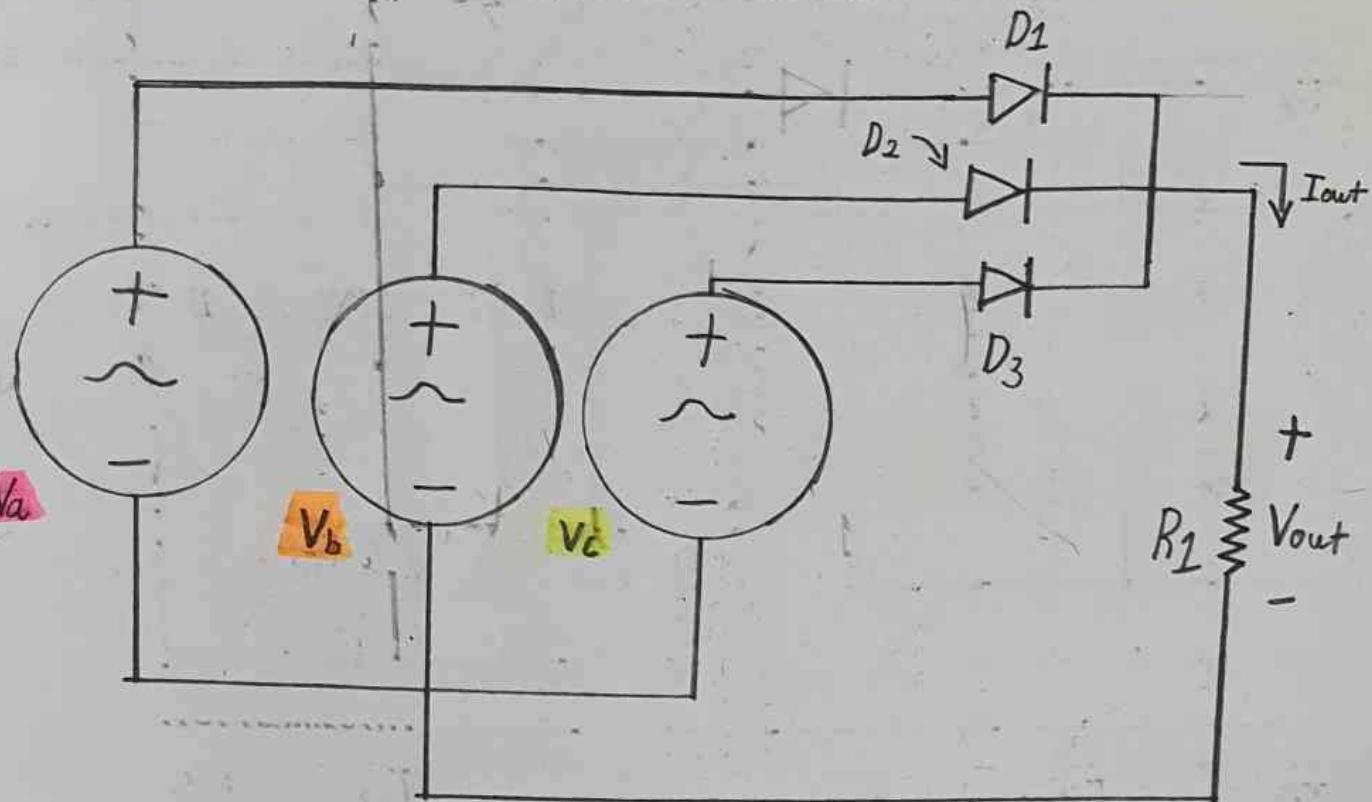

$$V_a = V_s \sin(\omega t_1) = 0.5V_s \quad \langle V_{out} \rangle = \frac{1}{\omega T} \int_0^T V_{out} d\omega t$$



$$\langle V_{out} \rangle = \frac{1}{2\pi} \left[\int_0^{\omega t_1} V_s \sin(\omega t + 2\pi/3) d\omega t + \int_{\pi/6}^{2\pi/3 + \pi/6} V_s \sin(\omega t) d\omega t + \right]$$

$$\left[\int_{2\pi/3 + \pi/6}^{4\pi/3 + \pi/6} V_s \sin(\omega t - 2\pi/3) d\omega t + \int_{4\pi/3 + \pi/6}^{2\pi} V_s \sin(\omega t + 2\pi/3) d\omega t \right] \downarrow$$

$$\frac{V_s}{2\pi} (0.36602 + 1.73205 + 1.73205 + 1.36603) \approx 0.82699 V_s = \frac{3\sqrt{3}}{2\pi} V_s$$

Full-Wave Rectifiers with Inductive Load

- 3 Phase Rectifiers

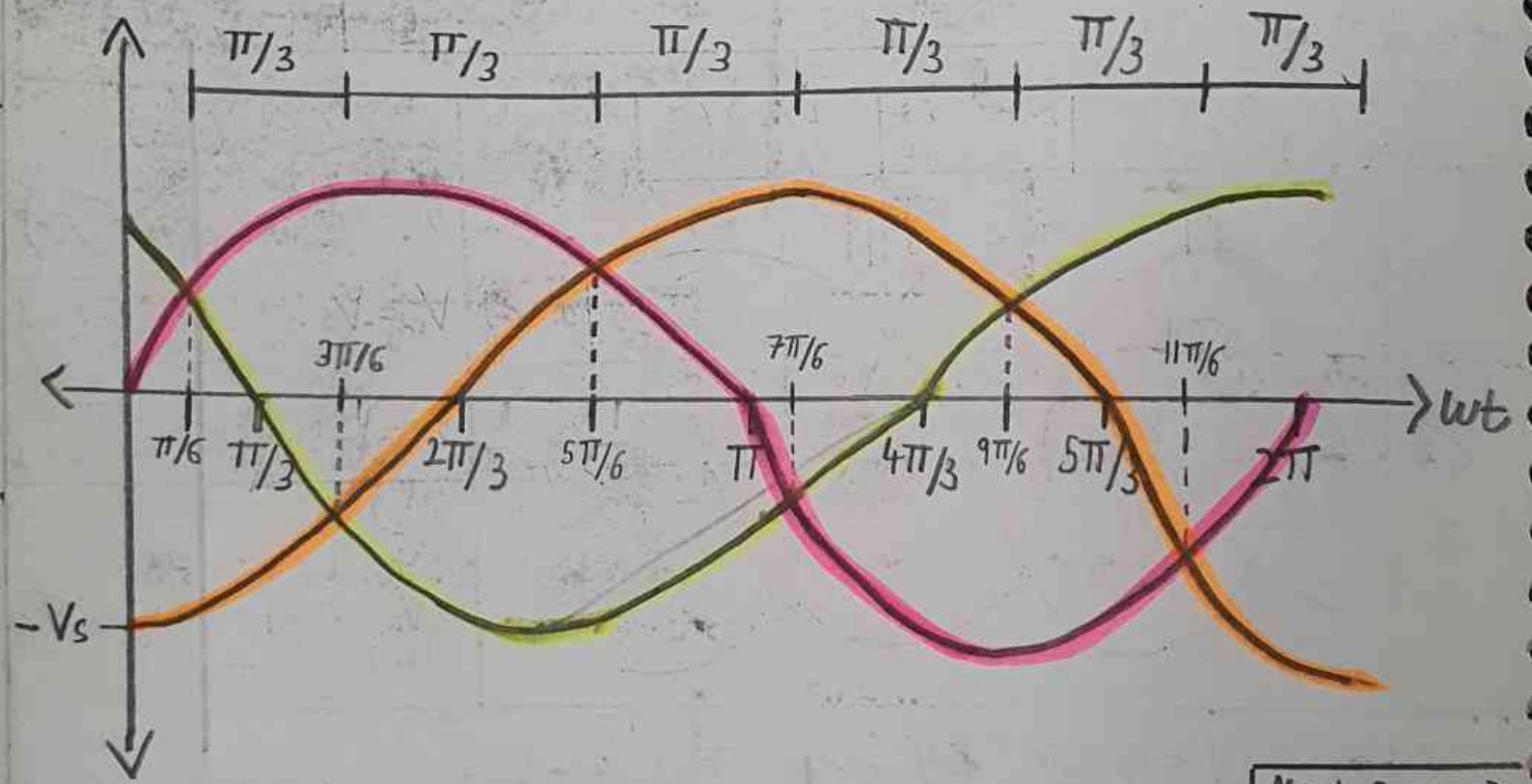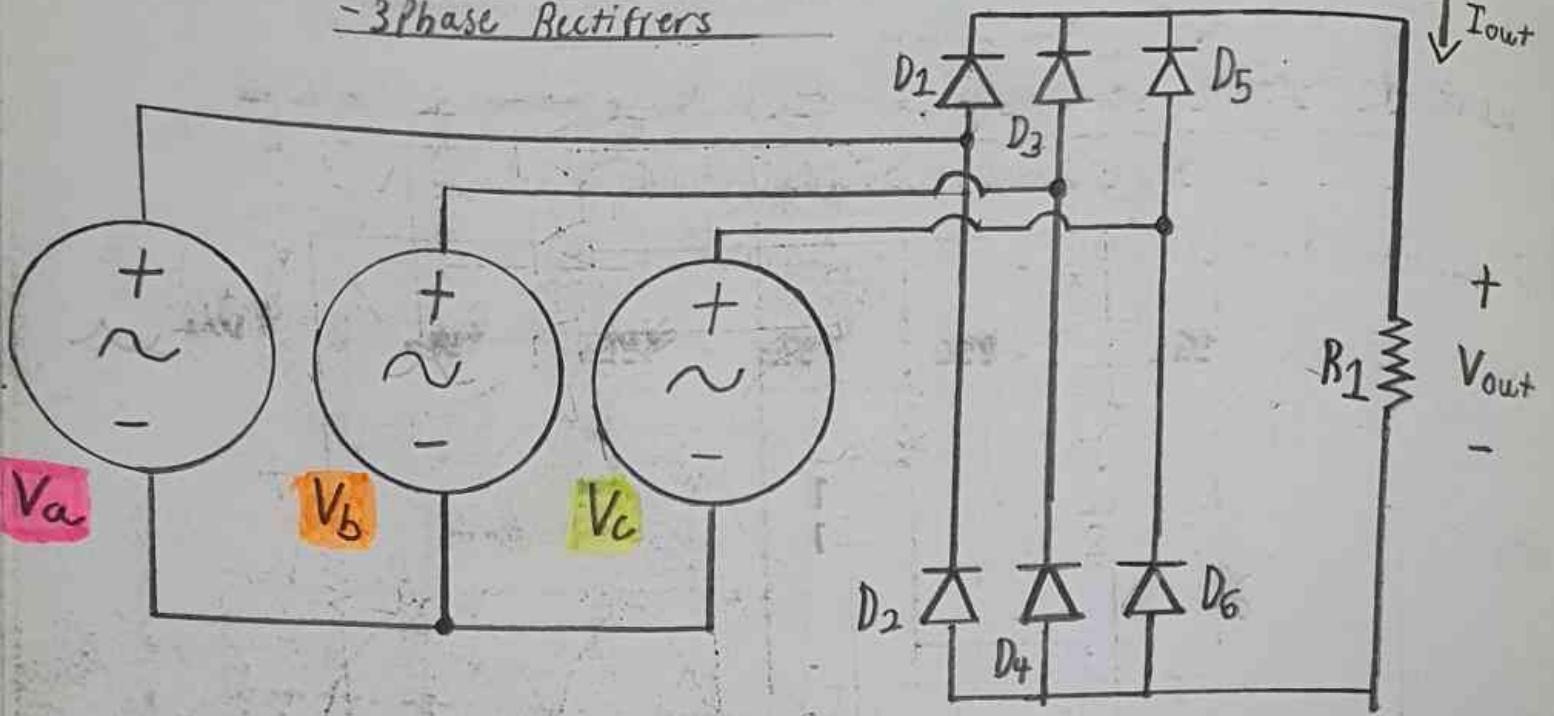


Next Page →

$$V_a = V_s \sin(wt)$$

$$V_b = V_s \sin(wt - 2\pi/3)$$

$$V_c = V_s \sin(wt + 2\pi/3)$$

$0 \text{ to } \pi/6, V_{out} = V_c - V_b, D_4/D_5 \text{ is ON}$ $\pi/6 \text{ to } 3\pi/6, V_{out} = V_a - V_b, D_1/D_4 \text{ is ON}$ $3\pi/6 \text{ to } 5\pi/6, V_{out} = V_a - V_c, D_1/D_6 \text{ is ON}$ $5\pi/6 \text{ to } 7\pi/6, V_{out} = V_b - V_c, D_3/D_6 \text{ is ON}$ $7\pi/6 \text{ to } 9\pi/6, V_{out} = V_b - V_a, D_3/D_2 \text{ is ON}$ $9\pi/6 \text{ to } 11\pi/6, V_{out} = V_c - V_a, D_5/D_2 \text{ is ON}$	$11\pi/6 \text{ to } 2\pi, V_{out} = V_c - V_b, D_5/D_4 \text{ is ON}$
--	--

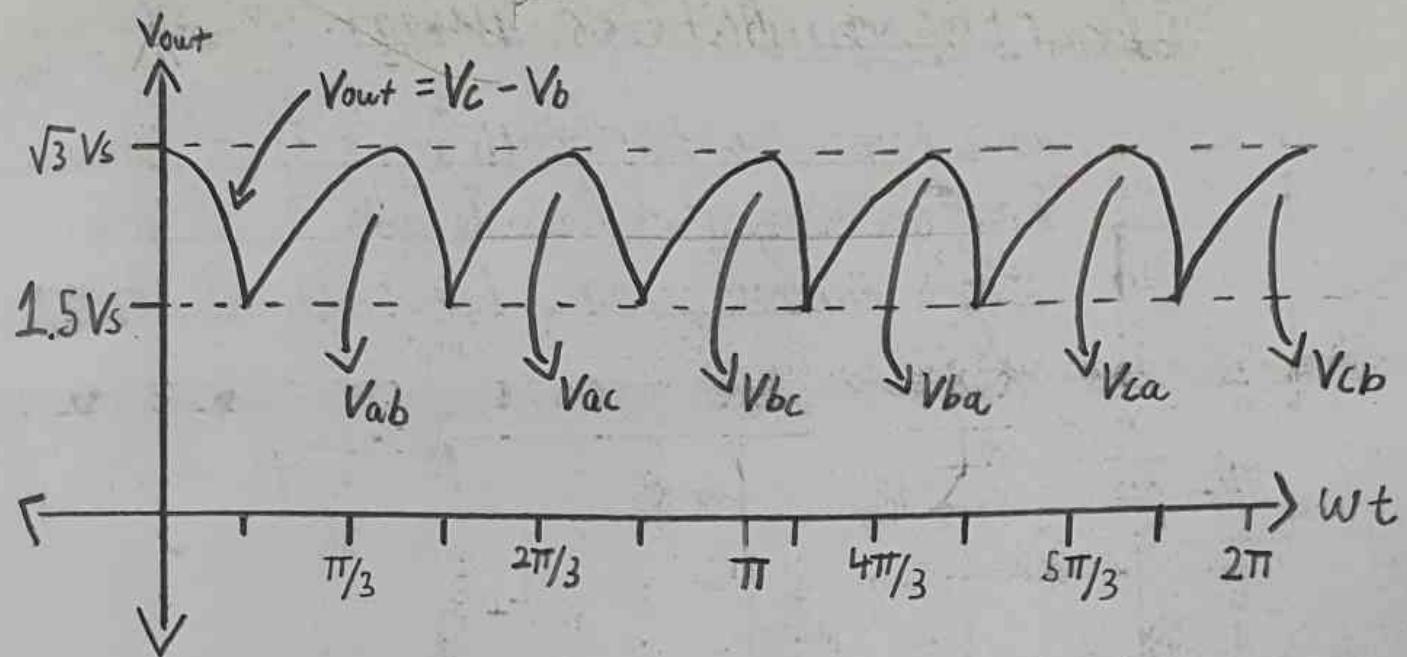

$$V_b = V_s \sin(wt - 2\pi/3)$$

$$V_c = V_s \sin(wt + 2\pi/3)$$

$$V_{ab} = \sqrt{3} V_s \sin(wt + \pi/6)$$

$$V_{ac} = \sqrt{3} V_s \sin(wt - \pi/6)$$

$$V_{bc} = \sqrt{3} V_s \sin(wt - 3\pi/6)$$

$$V_{ca} = \sqrt{3} V_s \sin(wt - 5\pi/6)$$

$$V_{cb} = \sqrt{3} V_s \sin(wt + 3\pi/6)$$

$$V_{out} = V_c - V_b = \sqrt{3} V_s \sin(wt + 3\pi/6)$$

$$wt = \pi/6 \quad \text{Peak Voltage}$$

$$V_{ba} = \sqrt{3} V_s \sin(wt - 5\pi/6) \quad \text{minimum Voltage}$$


$$V_{out} = \sqrt{3} V_s \sin(\pi/6 + 3\pi/6) = 1.5V_s$$

$$\langle V_{out} \rangle = \frac{1}{2\pi} \left[\int_0^{\pi/6} V_{cb} dt + \int_{\pi/6}^{3\pi/6} V_{ab} dt + \int_{3\pi/6}^{5\pi/6} V_{ac} dt + \int_{5\pi/6}^{7\pi/6} V_{bc} dt + \right.$$

$$+ \int_{7\pi/6}^{9\pi/6} V_{ba} dt + \int_{9\pi/6}^{11\pi/6} V_{ca} dt + \left. \int_{11\pi/6}^{2\pi} V_{cb} dt \right] = \frac{3\sqrt{3}}{\pi} V_s \approx 1.65399 V_s$$

A Single - Phase Rectifier Design

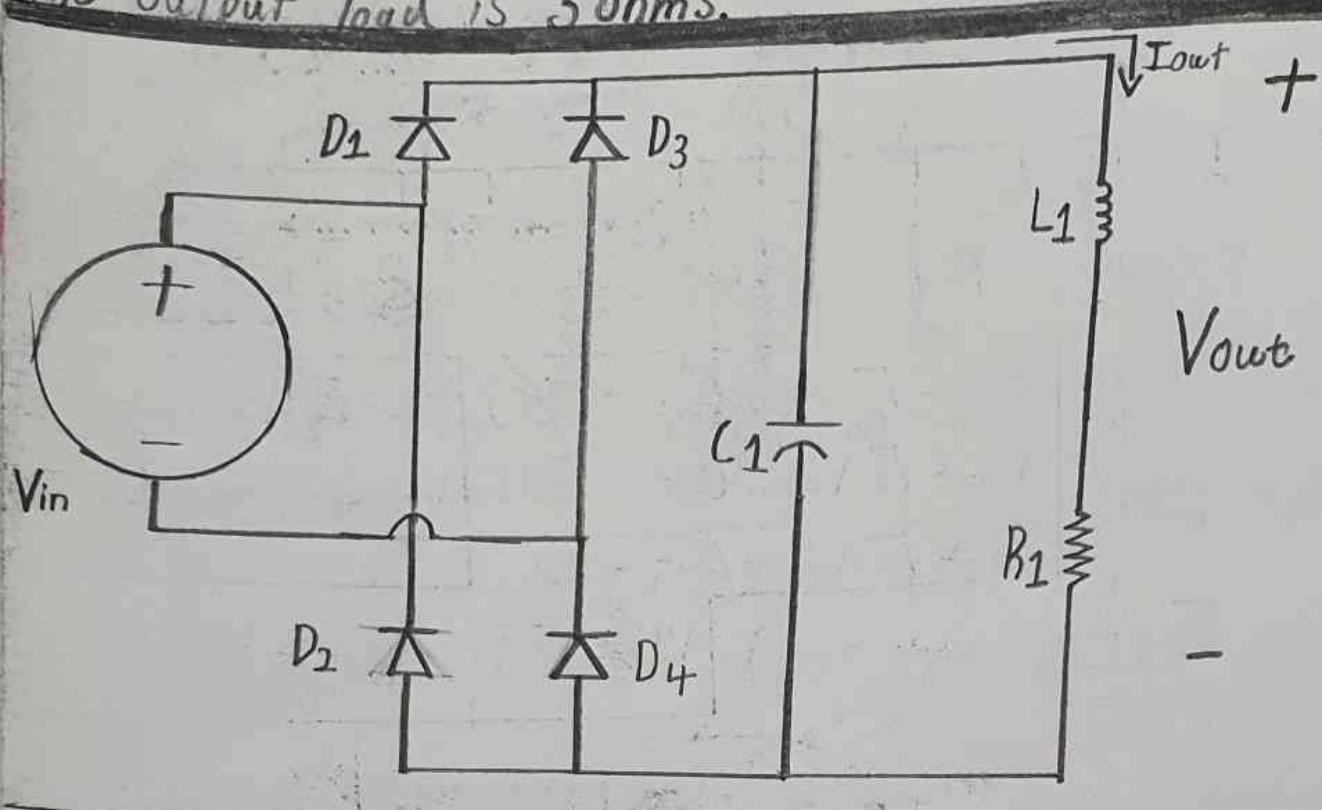Challenge - Design a single phase rectifier with an input voltage of 230V_{rms} at 50Hz an output voltage ripple lower than 20V_{pkpk}, and an output current ripple lower than 2A_{pkpk} the output load is 5 ohms.




$$V_{in} = 230 \text{ Vrms at } 50 \text{ Hz}$$

$$\text{Peak Voltage} = 230\sqrt{2} = 325.269 \text{ V}$$

$$\text{Radiane} = 2\pi (50\text{Hz}) = 314.159 \text{ radians/second}$$
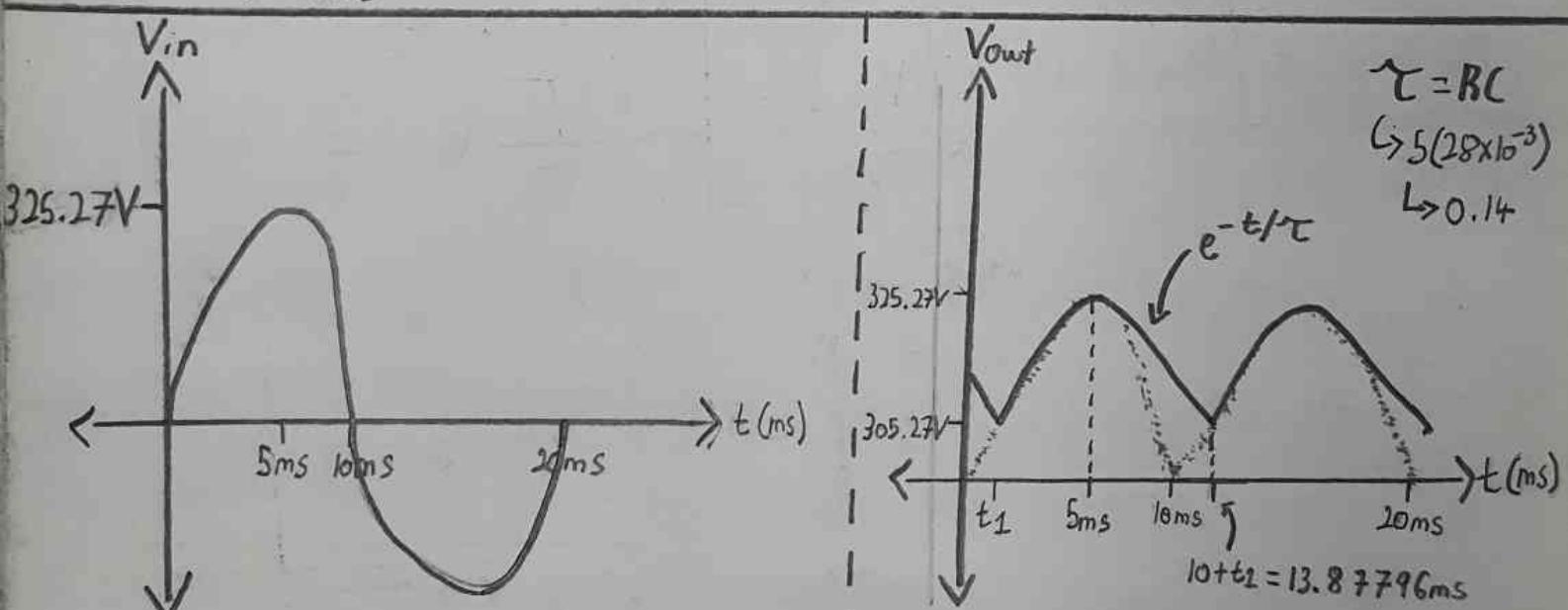
$$T = \frac{1}{50\text{Hz}} = 20 \text{ ms}$$



$$V_{out} = 325.269 \sin(314.159t), V = 305.269V$$

$$\hookrightarrow t_1 = 3.87796ms$$

$$325.269 e^{-(t-5 \times 10^{-3})/5C} = 305.269V, t = 13.8779ms \rightarrow C = 27.980 \mu F$$

$$\hookrightarrow 28 \mu F$$

$$V_{out}(t) = \begin{cases} 325.269 \sin(314.159t)V, 3.87796ms \text{ to } 5.0ms \\ 325.269 e^{-(t-5 \times 10^{-3})/0.14}, 5.0ms \text{ to } 13.87796ms \end{cases}$$



$$V_L = L \frac{di}{dt}$$

$$V_{out} = V_L + I_{out} R = L \frac{dI_{out}}{dt} + I_{out} R$$


↗
fourier Series, find coefficient

$$\frac{dI_{out}}{dt} = \frac{V_{out} - 5I_{out}}{L}, L_1 = 10mH$$

The Ideal DC to DC Converter

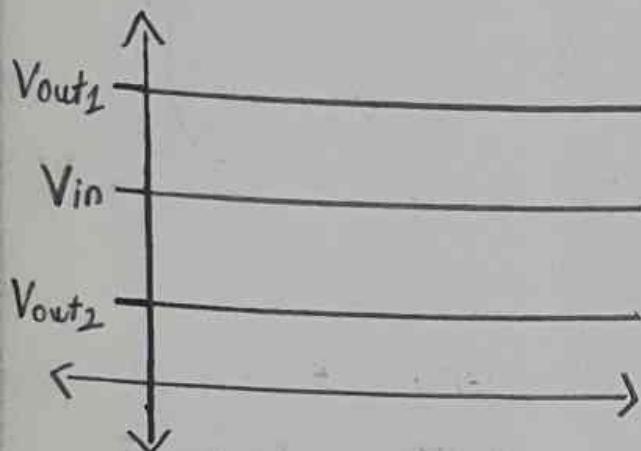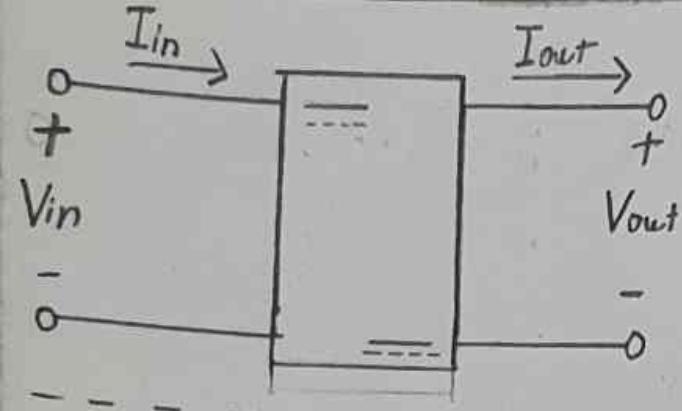

$$V_{out\text{pkpk}} = 0$$

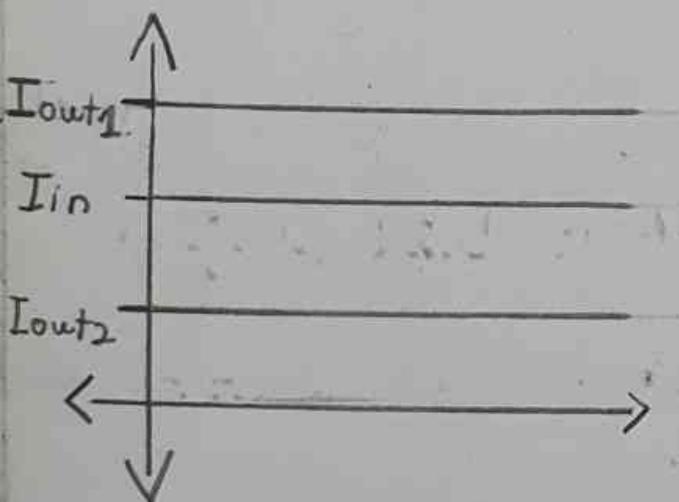

$$I_{out\text{pkpk}} = 0A$$


$$P_{in} = P_{out}$$

$$P = IV$$

A diagram showing the derivation of the current formula. It features a curved arrow pointing from the $P = IV$ equation to the formula $I = \frac{P}{V}$. The formula is written as $I = \frac{P}{V}$, where P is above the fraction line and V is below the fraction line.

Review of the Power BJT and the Power MOSFET


BJT:

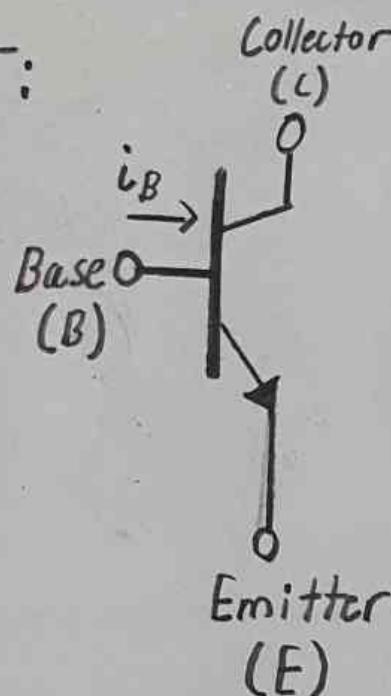

When $i_B > 0A$.




When $i_B = 0$

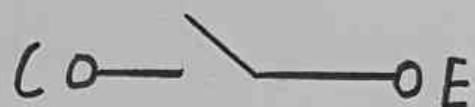

Note: BJT is a current controlled switch.

MOSFET:

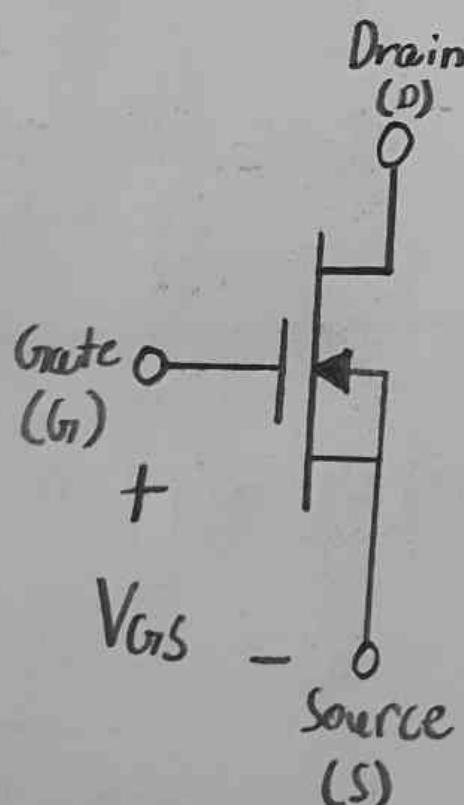

When $V_{GS} > 0V$





When $V_{GS} = 0V$



Note: Mosfet is a voltage controlled switch.

The Basic DC Chopper

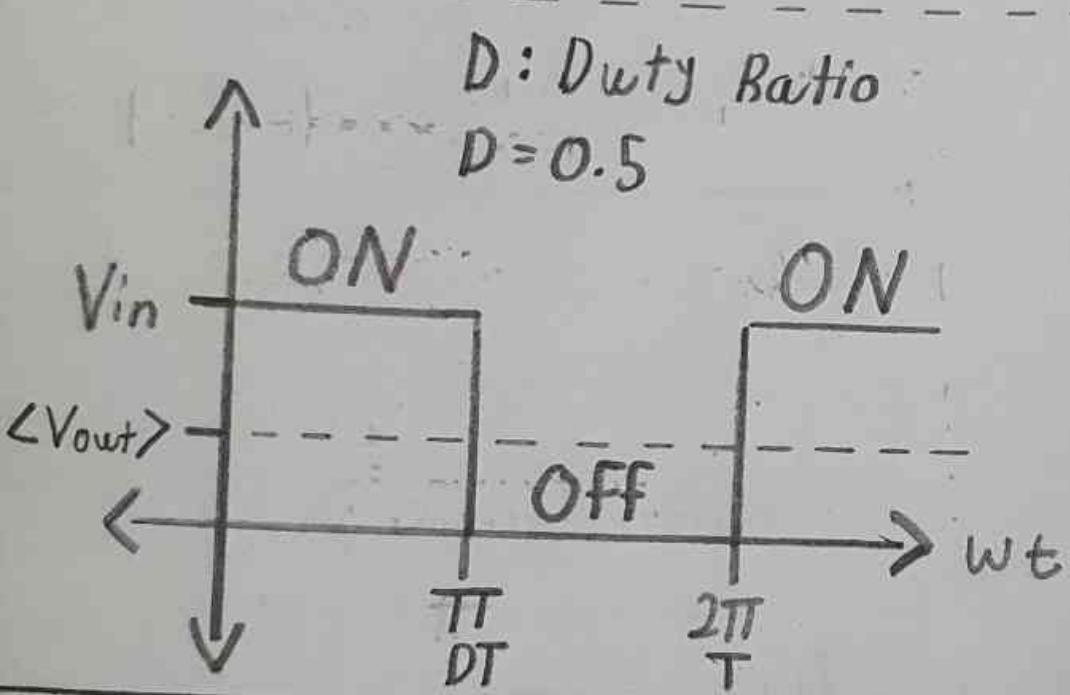
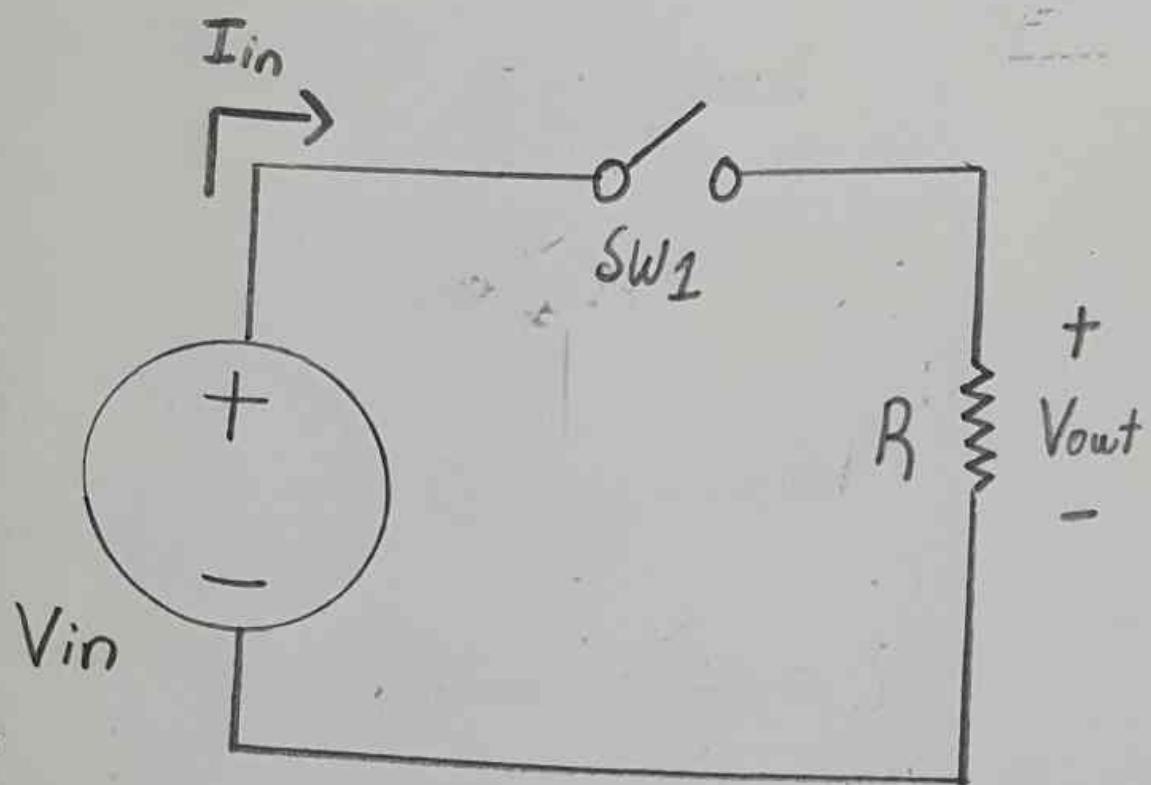


$$\langle V_{out} \rangle = \frac{1}{2\pi} \int_0^{\pi} V_{in} dwt = \frac{1}{2\pi} \left[V_{in}(\pi) - V_{in}(0) \right]$$

$$\hookrightarrow \frac{V_{in}(\pi)}{2\pi} = \frac{V_{in}}{2}$$

$$\hookrightarrow \langle V_{out} \rangle = DV_{in}$$

Buck (Step-Down) Converters

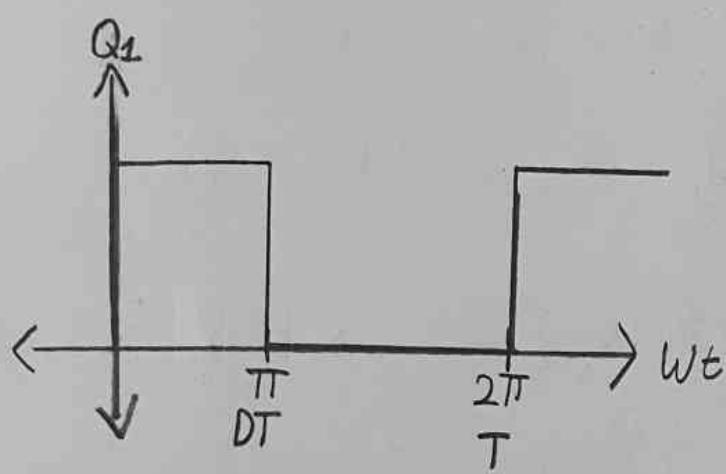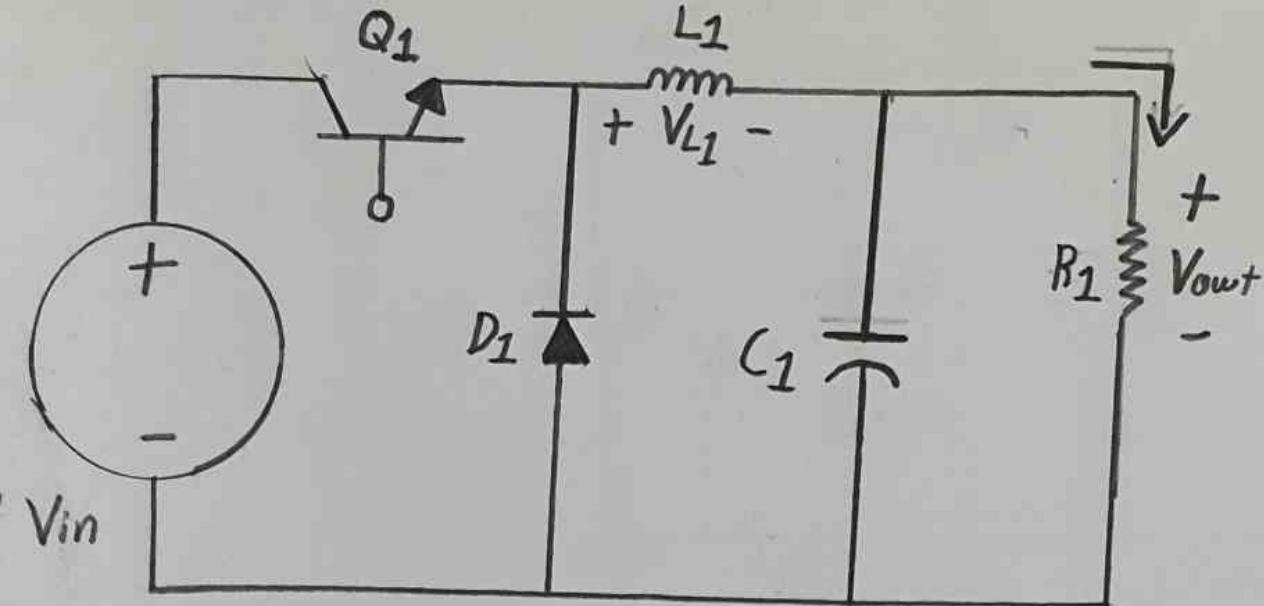

$$\begin{aligned}
 & DT(V_{in} - V_{out+}) + (T - DT)(-V_{out}) = 0 \\
 \hookrightarrow & DT(V_{in} - V_{out+}) + (1 - D)T(-V_{out}) = 0 \\
 \hookrightarrow & DV_{in} - DV_{out+} - V_{out+} + DV_{out+} = 0 \\
 \hookrightarrow & \boxed{V_{out+} = DV_{in}}
 \end{aligned}$$

State 1 0 to π :

Q_1 is ON, D_1 is OFF

$$-V_{in} + V_{L1} + V_{out+} = 0$$



$$\hookrightarrow V_{L1} = V_{in} - V_{out+}$$

State 2 π to 2π :

Q_1 is OFF, D_1 is ON

$$V_{L1} + V_{out+} = 0 \rightarrow V_{L1} = -V_{out+}$$

Boost (Step - UP) Converters

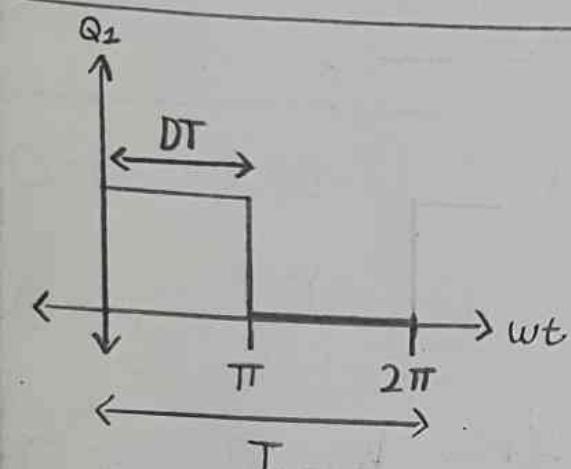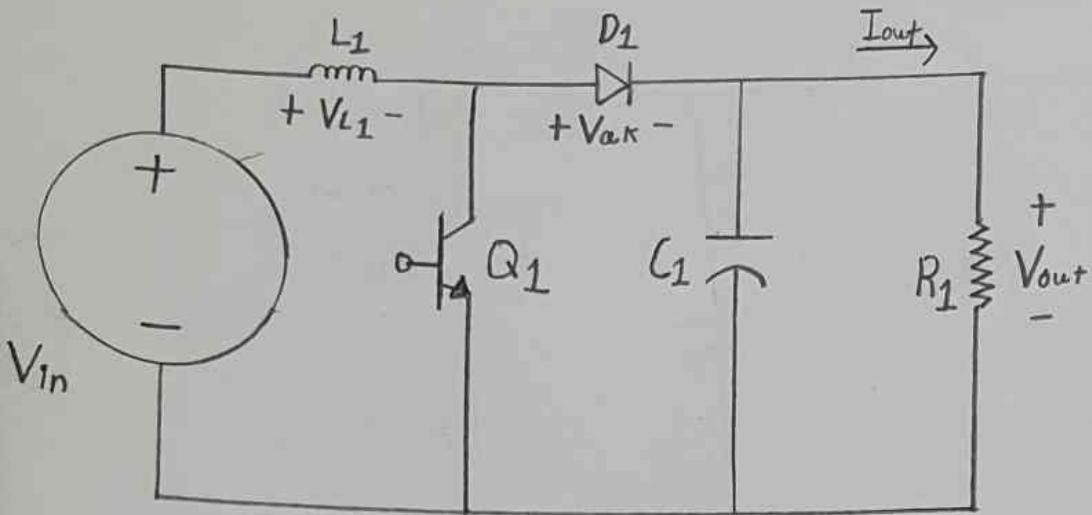

State 1:

Q_1 is ON and D_1 is OFF

$$-V_{in} + V_{L1} = 0 \rightarrow V_{L1} = V_{in}$$

State 2:

Q_1 is OFF and D_1 is ON

$$-V_{in} + V_{L1} + V_{out+} \rightarrow V_{L1} = V_{in} - V_{out+}$$

Energy discharged
from Inductor
 L_1 during
State 2.

Energy Stored
in inductor
 L_1 during
State 1

$$\left[\frac{DT(V_{in})}{L_1} \right] + \left[\frac{(1-D)\tau(V_{in} - V_{out+})}{L_1} \right] = 0$$

$$\hookrightarrow DV_{in} + V_{in} - V_{out+} - DV_{in} + DV_{out+} = 0$$

$$\hookrightarrow V_{in} + V_{out+}(D-1) = 0$$

$$\hookrightarrow V_{in} = V_{out+}(1-D) \rightarrow \frac{V_{out+}}{V_{in}} = \frac{1}{1-D} \rightarrow V_{out+} = \frac{V_{in}}{1-D}$$

Examples : $V_{out+} = V_{in}/0.9 = 1.1V_{in}$, $V_{out+} = V_{in}/0.1 = 10V_{in}$